

**CONTENTS**

	Page
<b>CHAPTER I</b>	
ALTERNATING CURRENT AND VOLTAGE	1
1. General Field of Use of Alternating Current	1
2. Sine Waves	3
3. Cycle : Frequency	6
4. Commercial Frequencies	8
5. Alternating-current Ampere	9
6. Equation of Sine Wave of Current	12
7. Equation of the Current Squared Wave	13
8. Scalars and Vectors	14
9. Ohm ; Volt	16
10. Phase Relations	16
11. Addition of Currents	18
12. Vector Representation of Alternation Quantities	19
13. Vector Addition of Sine Waves	21
<b>CHAPTER II</b>	
ALTERNATING-CURRENT CIRCUITS	24
14. Alternating-current Power; Voltage and Current in Phase	24
15. Alternating-current Power; Voltage and Current in Quadrature	26
16. Alternating-current Power; Voltage and Current Differ in Phase by Angle $\theta$	27
17. Circuit Containing Resistance Only	28
18. Circuit Containing Inductance Only	29
19. Circuit Containing Capacitance Only	32
20. Circuit Containing Resistance and Inductance in Series	35
21. Power	37
22. Circuit Containing Resistance and Capacitance in Series	38
23. Circuit Containing Resistance, Inductance, and Capacitance in Series	40
24. Resonance in a Series Circuit	42
25. Resonance Characteristics of Series Circuits	44
26. Parallel Circuits	46
27. Resonance in Parallel Circuit	47
28. Polygon of Voltages ; Three Voltages	49
29. Polygon of Voltages ; Four Voltages	52
30. Polygon of Currents	55
31. Effective Resistance	55
32. Energy and Quadrature Currents	56
33. Reactive Volt-amperes	58
34. Maximum Power in a Series Circuit	59
<b>CHAPTER III</b>	
COMPLEX QUANTITIES	61
35. Rectangular Notation of Complex Quantities	61
36. Rectangular Vectors	63
37. Addition and Subtraction of Rectangular Vectors	63
38. Reciprocals of Rectangular Vectors	64
39. Multiplication of Rectangular Vectors	65
40. Division of Rectangular Vectors	65
41. Polar Notation	66
42. Addition of Polar Vectors	66
43. Multiplication of Polar Vectors	67
44. Reciprocals of Polar Vectors	67

45. Division of Polar Vectors	68
46. Powers and Roots of Polar Vectors	68
47. Operators for Rotation of Vectors	68
48. Exponential Vectors	69
Application of Complex Quantities to Alternating Currents	70
49. Simple Series Circuits	70
50. Power Determination	72
51. The Parallel Circuit	74
52. The Series-parallel Circuit	77
53. Equivalent Parallel Impedance	79
54. Solution of Series-parallel Circuit with Polar Vectors	80

#### CHAPTER IV

ALTERNATING-CURRENT INSTRUMENTS AND MEASUREMENTS	82
55. Siemens Dynamometer	82
56. Indicating Electrodynamicometer	83
57. Electrodynamicometer Voltmeter	84
58. Inclined-coil Voltmeters	85
59. Dynamometer Ammeters	86
60. Wattmeter	86
61. Wattmeter Connections	88
62. Wattmeter Ratings	90
63. Polyphase Wattmeter	90
64. Wattmeter Calibration	92
Iron-vane Instruments	93
65. Voltmeters	93
66. Ammeters	94
67. Hot-wire Instruments	95
68. Alternating –current Watthour Meter	95
69. Calibration and Adjustment of the Induction Watthour Meter	99
70. Frequency Indicators	100
71. Power-factor Indicators	101
72. Synchroscope	103
73. Oscillograph	105
74. Impedance Bridge	108

#### CHAPTER V

POLYPHASE SYSTEMS	110
75. Reasons for Use of Polyphase Systems	110
76. Double-subscript Notation	111
77. Generation of Three-phase Voltage	115
78. Y-connection	117
79. Power in Y-system	118
80. Delta Connection	120
81. Power in Delta System	123
Methods of Measuring Power in Three-phase System	123
82. Three-wattmeter Method	123
83. Two-wattmeter Method	125
Two-phase Systems	130
84. Two-phase and Four-phase (Sometimes Called Quarterphase) Systems	130
85. Measurement of Power in Two-phase Systems	134
86. Addition of Loads by the Kilovolt-ampere Method	134
87. Applications of Complex Algebra to Polyphase Circuits	136

#### CHAPTER VI

THE ALTERNATOR	141
88. Rotating-field Type	141
Alternator Windings	142
89. General Principles	142
90. Single-phase Windings	143

91. Two-phase Windings	146
92. Two-phase Windings	148
Three-phase Windings	149
93. Full-pitch Windings	149
94. Fractional-pitch Windings	151
Alternator Construction	154
95. Types of Alternators	154
96. Stator or Armature	154
97. Slots	157
98. Ventilation	158
99. Rotating-field Structure	160
Alternator Electromotive Forces and Outputs	163
100. Generated Electromotive Force	163
101. Wave Shape	167
102. Magnetomotive Force of Distributed Field Windings	169
103. Phasing Alternator Windings	170
104. Rating of Alternators	172

## CHAPTER VII

ALTERNATOR REGULATION AND OPERATION	173
105. Alternator Regulation	173
106. Armature Reactance	174
107. Armature Resistance	176
Single-phase Armature Reaction	177
108. Current and Electromotive Force in Phase	177
109. Current in Quadrature Lagging	180
110. Current in Quadrature Leading	181
111. Current Lags by Angle $\theta$	182
112. Polyphase Armature Reaction	182
113. Armature Impedance Drop	184
114. Alternator Regulation	189
115. Space and Time Vectors	190
116. General Method	194
117. Synchronous-impedance Method, or Electromotive-force Method	196
118. Determination of Synchronous Reactance	197
119. Three-phase Application	200
120. Regulation of a Y-connected Generator	202
121. Regulation of a Delta-connected Generator	204
122. Magnetomotive-force Method	205
123. American Institute of Electrical Engineers Method	209
124. Efficiencies of Alternators	211
125. Tirrill Regulator	214
126. Parallel Operation of Alternators	215
127. Synchronizing Power	218
128. Reactive Power	219
129. Synchronizing	221
130. Hunting of Alternators	223

## CHAPTER VIII

THE TRANSFORMER	225
131. Transformer Principle	225
132. Induced electromotive Force	226
133. Ampere-turns	229
134. Leakage Reactance	231
135. Transformer Vector Diagram	233
136. Simplified Diagram	236
137. Equivalent Resistance and Reactance	237
138. Open-circuit Test	240
139. Short-circuit Test	243
140. Regulation	245

141. Efficiency	246
142. Commercial Transformers	249
143. All-day Efficiency	250
144. Core-type Transformer	250
145. Shell-type Transformer	252
146. Type H Transformer	252
147. Cooling of Transformers	253
148. Breathing of Transformers	257
149. Three-phase Transformers	258
150. Auto-transformers	261
151. Phasing Transformer Windings	266
152. Three-phase Transformer Connections	267
153. V-connection	269
154. V-connection and Single-phase Load	270
155. Scott or T-connection	272
156. Tap Changing under Load	275
157. Constant-current Transformers	276
Instrument Transformers	279
158. Electrical Measurements at High Voltages	279
159. Potential Transformers	279
160. Current Transformers	280

## CHAPTER IX

THE INDUCTION MOTOR	284
161. Principle	284
162. Alternating-current Rotating Field	286
163. Rotating Fields in Two-phase Drum-wound Machines	290
164. Rotating Fields in Three-phase Drum-wound Machines	292
165. Synchronous Speed ; Slip	294
166. Rotor Frequency and Induced Electromotive Force	295
167. Alternating-current Torque	296
168. Stator and Slots	301
169. Squirrel-cage Motor	303
170. Operating Characteristics of Squirrel-cage Motor	304
171. Torque Characteristics of Squirrel-cage Motor	306
172. Double-squirrel-cage Rotors	310
173. Starting Squirrel-cage Motors	312
174. Wound-rotor Induction Motor	316
175. Induction-motor Air-gap	320
176. Equivalent Circuit of Induction Motor	320
177. Induction-motor Vector Diagram	324
178. Circle Diagram	326
179. Speed Control of Induction Motors	330
180. Induction Generator	334
181. Measurement of Slip	338
182. Induction Regulator	341

## CHAPTER X

SINGLE-PHASE MOTORS	344
183. Series Motor	344
184. Commutating Poles	349
185. Series-motor Vector Diagram	350
186. Repulsion Motor	352
187. Single-phase Induction Motor	357
188. Reactions in a Single-phase Induction Motor	359
189. Operation of Polyphase Motor as Single-phase Motor	362
Starting Single-phase Induction Motors	362
190. Split-phase Methods	362
191. Capacitor Motor	363
192. Repulsion-motor Start	365

193. Induction Motor as Phase Converter	367
---	-----

## CHAPTER XI

THE SYNCHRONOUS MOTOR	371
194. Synchronous Motor	371
195. Principles of Operation	371
196. Effect of Loading Synchronous Motor	372
197. Effect of Increasing Field Excitation	376
198. Effect of Decreasing the Field Excitation	378
199. Excitation in constant-potential System	380
200. Interlocking Action of Salient Poles	381
201. Synchronous-motor Vector Diagram	382
202. Synchronous-motor V-curves	385
203. Synchronous-motor Excitation Diagram	388
204. Amortisseur or Damper windings	389
205. Starting the Synchronous Motor	391
Starting Synchronous Motor under Load	395
206. High-starting-torque Motors	395
207. Supersynchronous Motor ; Clutches	396
208. Synchronous Condenser	397
209. Power-factor Correction with Synchronous Condenser	398
210. Synchronous Motor as Corrector of Power Factor	400
211. Kilowatt and Kilovar Method	402
212. Synchronous Motor as Regulator of Voltage	403
213. Industrial Applications of Synchronous Motor	406
214. Frequency Converters	408
215. Synchronous Motors of Very Small Size	409

## CHAPTER XII

THE SYNCHRONOUS CONVERTER	412
216. Methods for Obtaining Direct Current from Alternating Current	412
217. Principle of Synchronous Converter	413
218. Polyphase Converters	414
219. Voltage Ratios in Single-phase Synchronous Converter	416
220. Voltage Ratios in Polyphase Synchronous Converter	417
221. Current Ratios in Synchronous Converter	418
222. Conductor Currents in Armature of Converter	422
223. Effect of Number of Phases and of Power Factor on Output of Synchronous Converter	426
224. Effect of Power Factor on Converter Rating	426
225. Armature Reaction in Converter	427
226. Voltage Control	429
227. Efficiency	434
228. Experimental Determination of Voltage and Current Relations in Converter	435
229. Synchronous-converter Connections	437
230. Inverter Synchronous Converter	439
231. Starting Synchronous Converter from Alternating-current side	440
232. Methods of Obtaining Correct Polarity	443
233. Starting Synchronous Converter by Means of an Auxiliary Motor	445
234. Starting Synchronous Converter from the direct-current Side	445
235. Parallel Operation of Synchronous Converters	446
236. Converter Dampers	447
237. Three-wire Converter	448

## CHAPTER XIII

TRANSMISSION OF POWER BY ALTERNATING CURRENT	450
238. Transmission Systems	450
239. Transmission-line Reactance, Single-phase	453
240. Transmission-line Reactance, Three-phase	455
241. Transmission-line Capacitance, Single-phase	457

242. Transmission-line Capacitance, Three-phase	459
243. Three-phase System ; Conductors Spaced Unsymmetrically	461
244. Single-phase Line Calculations	461
245. Three-phase Line Calculations	464
246. Lines Having Considerable Capacitance	466
247. Solution by Complex Quantities for Lines having Considerable Capacitance	468
248. Corona	470
249. Corona Power	472
Lighting and Transients	473
250. Lightning	473
251. Lightning and Surge Protection	476
252. Multigap Arrester	477
253. Horn Gaps	478
254. Aluminum – cell Arrester	479
255. Oxide-film Arrester	479
256. Pellet Type	480
257. SV Autovalve Lightning Arrester	481
258. Thyrite	481
259. Lightning – arrester Connections	482
Transmission Line Construction	484
260. Pin-type Insulators	484
261. Suspension-type Insulators	485
262. Transmission Structures	486
Substations and Distribution	488
263. Transformer Substations	488
264. Distribution Circuits	488
265. Three-wire Systems	491
266. Motor-generator and Synchronous-converter Substations	492
267. Oil Circuit-breakers	493
268. Chamber-type Circuit-breakers	494
269. De-ion Grid Circuit-breaker	495
270. Automatic Substations	497
271. Outdoor Substations	497

#### CHAPTER XIV

VACUUM TUBES	499
273. Electrons	499
274. Emission	500
275. Critical Velocity	500
276. Richardson’s Law	501
277. Thermionic Efficiency	502
278. Space Charge	502
279. Two-electrode Tube	502
280. Space-charge Saturation	503
281. Child’s Three-halves Power Law	505
282. Edison Effect	505
283. Fleming Valve	506
284. Full-wave Rectification	507
285. Rectifier Tubes	508
286. X-ray Tubes	508
287. Three-electrode Tube	509
288. Static Characteristics of Three-electrode Tube	510
289. Tube Coefficients	512
290. Other Static Characteristics	514
291. Measurement of Tube Coefficients	515
292. Three-electrode Receiving Tubes	518
293. Amplification	518
294. Dynamic Characteristics	519
295. Power and Efficiency	520
296. Voltage Amplification	522

297.Measurement of Voltage Amplification	525
298.Four-electrode Tubes	526
299.Five-electrode Tubes	528
300.Multi-electrode Tubes	529
301.Regeneration	530
Oscillators	531
302.Oscillation	531
303.Power Tubes	536
Modulation	536
304.Modulation	536
305.Heising Constant-current Method	539
Detection	540
306.Rectification with Two-electrode Tube	540
307.Detection with Three-electrode Tube with Polarized Grid	542
308.Detection with Three-electrode Tube with Grid Resistance	543
309.Detection and Regeneration	544
310.Heterodyne or Beat Reception	544
Receivers	547
311.Receiving Circuits	547
312.Tuned Radiofrequency Receiver	550
313.Superheterodyne Receiver	550

## CHAPTER XV

RECTIFIERS	551
314.Half-and Full-wave Rectification	552
315.Mechanical Rectifiers	553
316.Electrolytic Rectifiers	554
317.Copper-oxide Rectifier	554
318.Hot-cathode Rectification	555
319.Hot-cathode Gaseous Rectifiers	558
Mercury-arc Rectifiers	560
320.Mercury Arc	560
321.Operation of Single-phase Rectifiers	561
322.Voltages and Currents with Resistance Load	562
323.Battery Load	564
324.Anode Inductance	565
325.Smoothing Inductance	567
326.Single-phase Glass-tube Rectifier	568
327.Three-phase Rectifier	570
328.Six-phase Rectifier and Anode Inductance	572
329.Voltage and Current Ripple	575
330.Average Direct-current Electromotive Force	576
Grid-controlled Gaseous Rectifiers and Inverters	577
331.Hot-cathode Thyatron	577
332.General Electric Thyatron	578
333.Grid Control	579
334.Methods of Grid Control	581
335.Thyatron as Rectifier	583
Thyatron as Inverter	584
336.Simple Inverter Action	584
337.Inverter Circuit	586
338.Ratings of Thyatrons	587
339.Power Rectifiers with Grid Control	588
340.Connections for Grid Control	590
341.Grid Control in Power Rectifiers	592
342.Backfiring	593
343.Efficiencies of Rectifiers	593
344.Advantages of Mercury-arc Rectifiers	594
345.Rectification and Inversion for Power Transmission	595

