
Contents

1 Amplification 1

Objectives	1
Introduction	1
Basic Amplifiers	2
Basic Amplifier Concepts, 2	Basic Amplifier Characteristics, 3
Amplifier Calculations	5
Ideal Amplifiers, 5	Practical Amplifiers, 6
Ideal Amplifier	8
Feedback	9
Feedback Calculations, 10	Advantages of Feedback, 11
Operational Amplifiers	12
Practical Operational Amplifier	14
General Amplifier Characteristics, 14	Amplifier Analysis, 14
Operational Amplifier Types	16
Summary	17
Questions	18
Problems	18

2 DC Specifications and Circuits 20

Objectives	20
Introduction	20
Gain Specifications	21
Open-Loop Gain, 21	Difference-Mode Gain, 23
Common-Mode Gain, 24	
Input and Output Resistance Characteristics	25
Error Sources	26
Input Offset Voltage, 26	Input Bias and Offset Currents, 26
Other Specifications	27
Basic Operational Amplifier Circuits	28
Voltage Follower, 28	Noninverting Amplifier, 32
Inverting Amplifier, 35	
Summary	38
Questions	39
Problems	40

3 DC Applications 42

Objectives	42
Introduction	42

Temperature Measurement	43
Thermistors, 43	Thermocouples, 43
Solid-State Temperature Transducers, 45	An Electronic
Thermometer, 48	Modern Temperature Transducers, 50
Meters	51
Increasing Meter Input Resistance, 51	Improving Meter Voltage Sensitivity, 52
Current-to-Voltage Converters, 54	
Voltage Regulation	55
Manual Control, 58	Simple Transistorized Regulator, 60
Op Amp Voltage Regulators, 61	
Increasing Regulator Current Capability, 65	Error Sources, 67
Shunt Regulation	68
Switched-Mode Regulators	71
Integrated Circuit Voltage Regulators	76
Summary	80
Questions	80
Problems	82

— 4 AC Specifications and Circuits 84

Objectives	84
Introduction	84
Basic AC Characteristics	85
Frequency Response (Gain versus Frequency), 85	
Phase Response (Phase versus Frequency), 87	Slew Rate, 89
Feedback and Stability Considerations	94
Frequency Response, 94	Phase Response, 97
Composite Response, 100	Stability, 103
Frequency Compensation	106
Summary	111
Questions	112
Problems	113

— 5 Audio Applications 115

Objectives	115
Introduction	115
Basic Audio Amplifier Concepts	116
General Characteristics of Audio Amplifiers, 116	
Typical Circuit Configurations, 117	Single-Supply Operation, 117
Noise in Audio Amplifiers, 120	
Audio Circuits in General	122
Offset Problems, 122	Compensated Operational Amplifiers, 122
Uncompensated Operational Amplifiers, 127	
Typical Audio Amplifiers	130
Block Diagram, 130	Preamplifiers, 132
Equalizer Amplifiers, 133	Tone Control, 136
Audio Op Amps, 140	Power Op Amps, 143

Summary 148 Questions 149 Problems

—— 6 *High-Frequency Amplifiers* 152

Objectives 152

Introduction 152

Ultrasonics 153

 Applications, 153 Op Amps for Ultrasonics, 155

Narrow-Band Amplifiers 156

 Spectrum Diagrams, 156 Radio Frequency

 Amplification, 159

Wide-Band Amplifiers 162

Pulse Components 163

Video Amplifiers 165

 Requirements for Video Amplifiers, 165 Video Op Amps, 166

Noise 174

Automatic Gain Control (AGC) 174

 Typical IF Amplifiers with AGC, 175 Other

 Applications, 177

Summary 178 Questions 179 Problems 180

—— 7 *Filter Basics* 181

Objectives 181

Introduction 181

Filter Fundamentals 182

 Filter Classifications, 182 Filter Graphs and

 Calculations, 183

Passive Filters 184

 Low-Pass Filters, 185 High-Pass Filters, 188

 Band-Pass Filters, 190 Band-Reject Filters, 191

 Miscellaneous Filter Facts, 191

Simple Active Filters 194

 First-Order Filter Fundamentals, 194 Active Filters without

 Feedback, 195 Active Filters with Feedback, 197

 Active First-Order Band-Pass Filters, 198

Summary 200 Questions 200 Problems 201

—— 8 *Advanced Filter Circuit* 201

Objectives 203

Introduction 203

Second-Order Filters 204

 Sallen-Key (VCVS) Filters, 204 Multiple-Feedback

 Second-Order Filters 212

Band-Pass Filters	213
Wide-Band Filters, 214	Multiple-Feedback Band-Pass Filters, 216
State-Variable Filters	219
General Characteristics of State-Variable Filters, 219	Typical State-Variable Filter, 219
Biquadratic Filters	223
General Characteristics of Biquadratic Filters, 223	Typical Biquadratic Filter, 225
Band-Reject, or Notch, Filters	227
Multiple-Feedback Notch Filter, 227	Biquad Notch Filter, 229
State-Variable Notch Filter, 229	
Miscellaneous Filters	231
High-Order Filters	232
General Characteristics of High-Order Filters, 232	
Third-Order High-Pass Filter, 234	Fourth-Order Low-Pass Filter, 235
Switched-Capacitor Filter	236
Summary	239
Questions	240
Problems	241

— 9 Oscillators 243

Objectives	243
Introduction	243
Sinusoidal (Sine Wave) Generators	245
Phase Shift Oscillator, 245	Wien Bridge Oscillator, 247
Twin-T Oscillator, 250	Quadrature Oscillators, 252
LC Oscillators, 254	
Nonsinusoidal Waveform Generators	258
Basic Fundamentals, 258	Square Wave Oscillators, 260
Pulse Generator, 265	
Waveform Generator	269
Summary	271
Questions	272
Problems	273

— 10 Mathematical Operations 275

Objectives	275
Introduction	275
Summing Circuits	276
Addition, 276	Multiplication, 280
Averaging, 280	Subtracting, 281
Applications of Summing Circuits, 282	
Integration	284
Concepts of Integration, 284	Practical Integrator, 286
Integrator Frequency Response, 289	

Differentiation	289	
Practical Differentiator,	290	Differentiator Frequency Response, 292
Logarithmic Amplifiers	292	
Concepts of Logarithmic Amplifiers,	293	Logarithmic Amplifier Applications, 295
Other Mathematical Circuits	298	
Summary	301	Questions 302 Problems 303

— 11 *Special-Purpose OP Amps and Linear ICs* 304

Objectives	304
Introduction	304
Comparators	305
Zero-Crossing Detector,	305
Window Comparator,	308
Level Detector,	307
Comparator Applications,	309
Instrumentation Amplifiers	311
Concepts of Instrumentation Amplifiers,	311
Instrumentation Amplifier Applications,	315
Current Difference Amplifiers	316
Transconductance Amplifiers	319
Programmable Amplifiers	321
Op-Amp-Related Integrated Circuits	323
Sample-and-Hold Circuits,	323
Subsystem,	325
Timer ICs,	327
Analog Signal-Processing	
Summary	333
Questions	334

— 12 *Using OP Amps with Semiconductor Devices* 335

Objectives	335
Introduction	335
Diodes and Op Amps	336
Precision Diode,	336
Circuits,	339
Absolute-Value Detectors,	341
Zener Diode Applications,	344
FET Applications	345
Voltage-Variable Resistors,	345
Gain Control,	346
Oscillators,	346
FET Switches,	348
Bipolar Transistor Applications	350
Power Switches,	350
Current Drivers,	352
Audio Applications,	353
Power Control Devices	353
Summary	357
Questions	357

13 D/A and A/D Converters 359

- Objectives 359
- Introduction 359
- D/A Conversion 360
 - Concepts, 360 Weighted Resistor D/A Converters, 362
 - R-2R D/A Converter, 365 A Typical D/A Converter, 368
- A/D Conversion 370
 - Concepts, 370 Integrating A/D Converter, 371
 - Tracking, or Counter, A/D Converter, 372 Successive-Approximation A/D Converter, 374 Parallel, or Flash, A/D Converter, 376 Some Typical A/D Converters, 376
- Applications of D/A and A/D Converters 379
- Summary 381 Questions 382 Problems 383

14 Phase-Locked Loops 384

- Objectives 384
- Introduction 384
- The Phase Detector 387
- Amplifiers and Low-Pass Filters 393
- Voltage-Controlled Oscillators 393
- A Typical PLL 396
- Applications 398
 - Frequency-Shift Keying, 398 FM Demodulation, 401
 - Tone Detectors, 402
 - Frequency Synthesis, 405
- Summary 408 Questions 409 Problems

15 Applications 410

- Introduction 410
- Thermometer 410
- Tone Detector 413
 - Tone Detector Circuit Operation, 414 Troubleshooting the Tone Detector, 414
- Level Sensor 415
 - Level Sensor Circuit Operation, 416 Troubleshooting the Level Sensor, 418
- Voltage-Controlled Oscillator 418
 - VCO Circuit Operation, 419 Troubleshooting a VCO, 421
- Current-Controlled Oscillator 422
- Function Generators 423
 - Function Generator Block Diagram, 423 Integrator Operation, 424 Square and Triangular Wave

Output, 426	Sawtooth Wave Output, 427	Pulse and Sine
Wave Output, 427	Triangular-to-Sine Wave	
Conversion, 428	LSI Function Generator, 429	
Absolute-Value Circuit	430	
Digital Audio	432	
Summary	434	Questions 435 Problems 436

Appendix A: Data Sheets 437

Appendix B: Basic Formulas

Appendix C: Sample Computer Programs 482

Glossary 487

Bibliography 503

Answers to Selected Problems

Index 509