

# Contents

## PREFACE

xvii

## 1

### PRACTICAL TRANSISTOR CIRCUIT THEORY

1

- 1.1 Iterated Circuits
- 1.2 Symbols
- 1.3 Feedback
- 1.4 The Miller Effect
- 1.5 Transistors
- 1.6 The transistor gain-impedance relation
- 1.7 Ohm's law and dc current-voltage relations
- 1.8 Collector power dissipation
- 1.9 Transistor power ratings and heat sinks
- 1.10 The decibel, or dB
- 1.11 The Transistor Current Gain  $\beta$

## 2

### SINGLE-STAGE AMPLIFIERS

16

- 2.1 Single-stage amplifiers
- 2.2 Applications using a single transistor

- 2.3 Threshold-sensitive circuits
- 2.4 Collector feedback amplifiers
- 2.5 The emitter feedback amplifier
- 2.6 A typical emitter feedback stage
- 2.7 High-gain single-stage amplifiers
- 2.8 CE stage with  $Q$ -point adjustment for large signal applications
- 2.9 Combined collection and emitter feedback
- 2.10 High gain CE stage with gain control
- 2.11 Universal single-stage amplifier
- 2.12 Oscilloscope preamplifier
- 2.13 Common-collector amplifiers
- 2.14 High input impedance CC stage
- 2.15 CC stage for driving a low-impedance load
- 2.16 CC-relay amplifiers
- 2.17 Complementary emitter followers

# 3

## **TWO-STAGE TRANSISTOR AMPLIFIERS**

38

- 3.1 Two-stage capacitor-coupled amplifier
- 3.2 Two-stage direct-coupled amplifier with feedback
- 3.3 Direct-coupled amplifiers with series feedback
- 3.4 High-input impedance CE-CE amplifiers with feedback
- 3.5 High-gain, general-purpose, two-stage amplifier
- 3.6 General-purpose line amplifier (audio)
- 3.7 High-gain audio-frequency amplifiers
- 3.8 High-gain emitter-feedback amplifiers
- 3.9 Two-stage combined feedback amplifier
- 3.10 Emitter-coupled two-stage amplifier
- 3.11 CE-CE high-gain pair amplifier
- 3.12 CE-CB cascode pair amplifier
- 3.13 The Darlington CC-CC amplifier
- 3.14 Darlington pair for power loads
- 3.15 CE collector feedback pairs
- 3.16 Phase inverters
- 3.17 Low-impedance phase inverter

**4****FIELD-EFFECT TRANSISTOR AMPLIFIERS**

59

- 4.1 RC-coupled FET stages
- 4.2 Single-stage RC-coupled FET amplifiers
- 4.3 High-gain FET stages
- 4.4 FET-transistor amplifiers
- 4.5 Oscilloscope preamplifier
- 4.6 High-impedance remote pickup
- 4.7 Low-impedance remote pickup
- 4.8 Low-power dc preamplifier
- 4.9 Two and three-stage FET transistor amplifiers
- 4.10 FET-transistor pair amplifier for low-impedance loads
- 4.11 Temperature compensated FET transistor amplifier
- 4.12 Broadband direct-coupled amplifier
- 4.13 FET with bootstrapped input
- 4.14 FET transistor dc amplifier
- 4.15 FET millivoltmeter

**5****MOS FET AMPLIFIERS**

77

- 5.1 Biasing single-stage MOS amplifiers
- 5.2 Two-stage resistance-coupled MOS-FET amplifiers
- 5.3 A wide-band MOS amplifier
- 5.4 High-gain three-stage MOS-FET amplifiers
- 5.5 High-gain low-noise low-drift dc amplifiers
- 5.6 MOS FET electrometer or picoammeter
- 5.7 MOS FET high-frequency amplifiers
- 5.8 MOS FET's in RF and UHF amplifiers

**6****POWER SUPPLIES AND REGULATORS**

87

- 6.1 Ac power supplies
- 6.2 Half-wave rectifiers

- 6.3      Bridge rectifiers
- 6.4      Voltage doublers
- 6.5      Regulated voltage doublers
- 6.6      Regulated power supply for integrated circuits
- 6.7      Typical low-power 30-V dc power supply
- 6.8      Line-operated power supply for a 2-W amplifier
- 6.9      Zener-diode regulators
- 6.10     Regulator for low-power 9-V equipment  
with a 12-V battery
- 6.11     Transistors as Zener diodes
- 6.12     Low-impedance regulator
- 6.13     Shunt transistor regulators
- 6.14     Series transistor regulators
- 6.15     Low-power voltage regulator
- 6.16     One-ampere voltage regulators
- 6.17     Current limiters
- 6.18     Fifteen-ampere short-circuit-protected voltage regulator
- 6.19     Capacitance multipliers
- 6.20     Replacing filter capacitors with Zener diodes
- 6.21     Battery power supplies

## 7

### LOW-NOISE AMPLIFIERS AND PREAMPLIFIERS

- 7.1      Noise in circuit components
- 7.2      Low-noise audio amplifiers
- 7.3      Low-noise collector feedback amplifier
- 7.4      Low-impedance, low-noise amplifiers
- 7.5      JFET high-impedance low-noise amplifiers
- 7.6      Nonblocking amplifier
- 7.7      Low-noise op-amp preamplifiers
- 7.8      Phonograph preamplifier
- 7.9      Transistor phonograph preamplifier

## 8

### AUDIO POWER AMPLIFIERS

- 8.1      Low-power class-A amplifiers
- 8.2      Pocket-radio audio amplifiers

- 8.3 Low-power line-to-line class-A amplifiers
- 8.4 Single-side class-A 2-W amplifier
- 8.5 Line-operated 1-W audio amplifiers
- 8.6 Transformer-coupled 4-W amplifiers
- 8.7 Power pairs
- 8.8 Push-pull 2-W amplifiers
- 8.9 Class-B 2-W amplifier and driver stage
- 8.10 Single-ended class-B 10-W amplifier
- 8.11 Complementary-symmetry amplifiers
- 8.12 Complementary-symmetry op-amp power amplifiers
- 8.13 Low-power complementary-symmetry amplifiers
- 8.14 A 20-W quasi-complementary-symmetry amplifier

**9****LINEAR INTEGRATED CIRCUITS**

144

- 9.1 Basic IC circuits
- 9.2 Signal addition and subtraction
- 9.3 Instrument amplifier
- 9.4 IC integrators
- 9.5 Analog computers
- 9.6 IC amplifier with a single power supply
- 9.7 IC amplifier for low-impedance loads
- 9.8 RC coupled IC amplifier
- 9.9 Bridge amplifiers
- 9.10 High-accuracy bridge amplifier
- 9.11 Resistance-indicating amplifier
- 9.12 IC feedback switch

**10****FILTERS**

160

- 10.1 Resistance-capacitance filters
- 10.2 Amplifier interstage coupling capacitors
- 10.3 Active filters
- 10.4 Miller-feedback filters
- 10.5 Practical low-pass filter
- 10.6 An IC low-pass filter
- 10.7 Active filters (higher order)
- 10.8 Filter types and nomenclature

- 10.9 Active high-pass filters
- 10.10 Active low-pass filters
- 10.11 CE stage filters
- 10.12 Butterworth filters
- 10.13 Butterworth 3-pole filters with equal capacitors
- 10.14 Chebyshev filters
- 10.15 Bessel filters
- 10.16 Op amps in active filters
- 10.17 Active filters using ICs
- 10.18 High-pass filters
- 10.19 Band-pass filters
- 10.20 Band-pass filters using op amps
- 10.21 Band-reject filters
- 10.22 Active band-reject filters

## 11

### TUNED AMPLIFIERS

195

- 11.1 Tuned circuits and the Q-factor
- 11.2 Tuned audio-frequency amplifiers
- 11.3 Twin-T tuned amplifiers
- 11.4 Narrow-band high-Q tuned amplifiers
- 11.5 Low-impedance tuned CB-CE amplifiers
- 11.6 Tuned-amplifier gain limitations
- 11.7 Tuned IF amplifiers
- 11.8 Tuned amplifier example
- 11.9 UHF tuned amplifiers
- 11.10 JFET tuned RF amplifiers
- 11.11 JFET UHF amplifiers

## 12

### VIDEO AMPLIFIERS

209

- 12.1 Video CB amplifier
- 12.2 Video CC amplifier
- 12.3 Video line-to-line amplifiers
- 12.4 Video iterated stage
- 12.5 Single-stage CRT video driver
- 12.6 Direct-coupled high-frequency amplifiers

- 12.7 High-impedance video amplifiers
- 12.8 CE-CE medium-frequency amplifier
- 12.9 High-voltage video amplifiers
- 12.10 Integrated-circuit video amplifiers
- 12.11 MOS-FET video amplifier
- 12.12 Compensating techniques

## 13

### DIODE CIRCUITS AND APPLICATIONS

225

- 13.1 Diode switches
- 13.2 Diode switches in dc power supplies
- 13.3 Spark and noise suppressors
- 13.4 Diode meter protection
- 13.5 Preventing transistor breakdown
- 13.6 Diode switches in low-level circuits
- 13.7 Diode steering circuits
- 13.8 Diode modulators and choppers
- 13.9 Diode AM modulator
- 13.10 Diode detectors
- 13.11 UHF diode voltmeter
- 13.12 Diode mixers
- 13.13 Varactor diode tuning
- 13.14 Diode clipping circuits
- 13.15 Base clipper (noise suppressor)
- 13.16 Low-level limiter and noise suppressor
- 13.17 Ignition noise suppressors
- 13.18 Diode clamp
- 13.19 Diode gate

## 14

### OSCILLATORS AND INVERTERS

250

- 14.1 Sinusoidal oscillators
- 14.2 Resonant circuit oscillators
- 14.3 Tuned emitter and tuned collector oscillators
- 14.4 Tuned-circuit power oscillators
- 14.5 Crystal oscillators
- 14.6 Phase-shift oscillators
- 14.7 Stepped low-frequency phase-shift oscillator

- 14.8 Twin-T R-C oscillators
- 14.9 Wien bridge oscillator
- 14.10 Nonsinusoidal oscillators
- 14.11 Multivibrators
- 14.12 Ringing converter or flyback oscillator
- 14.13 Blocking oscillators
- 14.14 Variable-frequency pulse oscillator
- 14.15 Inverters
- 14.16 Converters
- 14.17 High-voltage converters
- 14.18 UHF oscillators
- 14.19 Parasitic oscillations and feedback instability

## 15

### SPECIAL-PURPOSE CIRCUITS—AF AND AGC

280

- 15.1 An inexpensive hearing aid or intercom
- 15.2 Tone controls
- 15.3 Feedback tone control
- 15.4 Low-distortion AF mixer
- 15.5 A 7-W high-fidelity amplifier
- 15.6 Power amplifier with IC driver
- 15.7 Audio crossover network
- 15.8 Automatic gain-control amplifiers
- 15.9 Gain-control circuits
- 15.10 Audio AGC amplifiers
- 15.11 Instrument AGC amplifiers
- 15.12 Radio-frequency AGC amplifiers
- 15.13 IC amplifiers with AGC

## 16

### TRANSISTOR SWITCHING CIRCUITS

302

- 16.1 Transistor switches and relays
- 16.2 Switching amplifiers
- 16.3 All-purpose latch-up switch
- 16.4 Transistor SCR equivalent
- 16.5 Transistor breakdown pair
- 16.6 Temperature- or light-operated switch

- 16.7 A burglar and fire alarm
- 16.8 Flashlight-operated TV sound switch
- 16.9 Switching inverters
- 16.10 Flip-flops
- 16.11 Multivibrators
- 16.12 Monostable multivibrators
- 16.13 Schmitt triggers
- 16.14 Transistor and FET gates
- 16.15 MOS-FET choppers

# 17

## **LABORATORY INSTRUMENTS AND METHODS**

- 17.1 Laboratory instruments
- 17.2 Laboratory techniques
- 17.3 Volt-ohmmeters
- 17.4 Signal attenuators
- 17.5 Breadboards
- 17.6 Transistor testing
- 17.7 Transistor current-gain meters
- 17.8 Laboratory power supplies
- 17.9 Auxilliary power supply
- 17.10 Voltage regulators and current limiters
- 17.11 Inexpensive shop meter
- 17.12 High-frequency RF voltmeters
- 17.13 Linear AC voltmeter
- 17.14 Laboratory voltage standards

## **ANNOTATED BIBLIOGRAPHY**

343

## **APPENDIX**

- Transistors
- Junction field-effect transistors
- Insulated-gate field-effect transistors
- Miscellaneous semiconductor devices
- Zener diodes—400 mW and 1W
- Signal and rectifier diodes
- Semiconductor interchangeability
- Composition resistor values

- Standard resistance multiples**
- RMA resistor color code**
- Color code examples**
- Decibel formulas and tables**
- A practical decibel table**
- Frequency classifications**
- Thermal resistances**
- Maximum recommended temperatures**
- Reactance-Frequency Chart**

**INDEX**