

Contents

	Preface	vii
	Acknowledgments	ix
	Abbreviations	xix
1	Simple Meters for Current and Voltage	1
	1.1 Operating Principle of Simple Meters, 1	
	1.2 Multipliers and Shunts, 2	
	1.3 Measuring Internal Resistance of Meters, 6	
	1.4 Meter Resistor Specifications, 8	
	1.5 Ohms-per-Volt Rating, 9	
	1.6 Resistance Rating of Current Meters, 11	
	1.7 Multirange Voltmeters, 11	
	1.8 Multirange Current Meters, 13	
	1.9 D-C Volt-Milliammeter, 14	
	1.10 Very-High-Resistance D-C Voltmeter, 15	
	1.11 Meter Rectifiers for Alternating Current, 16	
	1.12 Crystal Meters, 19	
	1.13 A-C/D-C Multimeter, 20	
	1.14 D-C Millivoltmeter, 22	
	1.15 Thermocouple Meter, 22	
	1.16 Electrodynamometer Meter, 23	
	1.17 Calibration of Simple Meters, 24	
2	Ohmmeters and Volt-Ohm-Milliammeters	31
	2.1 Ohmmeter Operating Principle, 31.	
	2.2 Use of Voltmeter without Setting Zero, 33	
	2.3 Series-Connected Versus Shunt-Connected Ohmmeter, 33	

- 2.4 Potentiometer-Type Ohmmeter, 34
- 2.5 Measuring Resistance with Current Meter, 35
- 2.6 Simple Volt-Ohmmeter, 36
- 2.7 Ohmmeter Calibration, 37
- 2.8 Volt-Ohm-Milliammeter, 38
- 2.9 Typical Commercial VOM, 38
- 2.10 Calibration of VOM's, 42
- 2.11 Multimeter Operating Instructions, 43

3 Electronic Voltmeters

46

- 3.1 Features of the VTVM, 46
- 3.2 VTVM Types, 47
- 3.3 Battery-Operated Diode VTVM, 54
- 3.4 A-C Operation of a Diode VTVM, 56
- 3.5 Center-Zero D-C VTVM, 56
- 3.6 Resistance Measurement with VTVM, 58
- 3.7 Commercial Electronic Volt-Ohmmeter, 59
- 3.8 Laboratory-Type A-C VTVM, 64
- 3.9 Accessories for VTVM's, 64
- 3.10 Calibration Procedure for VTVM's, 68
- 3.11 Accuracy of VTVM's, 68
- 3.12 VTVM Operating Instructions, 69
- 3.13 Solid-State Voltmeters, 70

4 Power Meters

74

- 4.1 Voltmeter-Ammeter Method, 74
- 4.2 Basic Wattmeter, 74
- 4.3 Checking Power Drain of Electronic Equipment, 75
- 4.4 Simple Checking of A-F Power, 75
- 4.5 Audio Output Power Meter, 76
- 4.6 Electronic A-F Wattmeter, 79
- 4.7 Checking R-F Power, 80
- 4.8 Photoelectric R-F Wattmeter, 81
- 4.9 Measurement of R-F Power with Slotted Line, 82
- 4.10 Calorimetric Power Meter, 83
- 4.11 Decibel Power-Level Scales, 84

5 Impedance Checkers 86

- 5.1 Scope of Instrumentation, 86
- 5.2 Bridge-Type Impedance Meter, 86
- 5.3 Impedance Measurement by Voltmeter-Ammeter Method, 88
- 5.4 A-F Impedance Measurement with Simple T Network, 89
- 5.5 R-F Impedance Measurement with Simple T Network, 90
- 5.6 Checking Circuit for R-F Impedance of Transmission Line, 92
- 5.7 Transmission Line as R-F Impedance-Measuring Device, 92

6 Capacitance Checkers 95

- 6.1 Simple Capacitor Checker, 95
- 6.2 Compact Capacitor Bridge, 98
- 6.3 Commercial Service-Type Capacitance-Resistance Bridge, 99
- 6.4 Substitution Method for Small Capacitances, 101
- 6.5 Capacitance Checking with Grid-Dip Oscillator, 102
- 6.6 Simple Capacitance Meter, 103
- 6.7 Laboratory-Type Direct-Reading Capacitance Meter, 104
- 6.8 Transistorized Multivibrator-Type Capacitance Meter, 106
- 6.9 Substitution Capacitance Meter with Tunnel Diode Oscillator, 109
- 6.10 Substitution Capacitors, 110

7 Inductance Checkers 112

- 7.1 Inductance Bridge Assembled from Laboratory Parts, 112
- 7.2 Coil Checker with Capacitors as Standards, 114
- 7.3 Resonant L Meter, 115
- 7.4 Checking Inductance with Grid-Dip Oscillator, 118

- 7.5 Combination Inductance Bridge, 119
- 7.6 Professional Inductance-Capacitance Meter, 120
- 7.7 Substitution Inductors, 122

8 Special-Purpose Bridges and Accessories 124

- 8.1 Precision Resistance Bridge, 124
- 8.2 Skeleton-Type *L-C-R* Bridge, 126
- 8.3 Rheostat-Type Skeleton *R-C-L* Bridge, 132
- 8.4 Configuration and Ranges of the Impedance Bridge, 134
- 8.5 Bridge Oscillator, 136
- 8.6 High-Gain Null Detector, 138
- 8.7 Null Detector with Peaked Amplifier, 139
- 8.8 Sharply Tuned Bridge Amplifier, 140
- 8.9 Oscilloscope as Null Detector, 142

9 Oscilloscopes and Applications 145

- 9.1 Basic Oscilloscope, 145
- 9.2 Wide-Band Service-Type Oscilloscope, 146
- 9.3 Professional Laboratory Oscilloscopes, 149
- 9.4 Electronic Switch, 151
- 9.5 Servicing Radio Receivers with Oscilloscope, 153
- 9.6 Television-Receiver Checking with Oscilloscope, 157
- 9.7 Checking Transmitter Modulation with Oscilloscope, 161
- 9.8 Frequency Checking with Oscilloscope, 163
- 9.9 Phase Checking with Oscilloscope, 163
- 9.10 Voltage Calibration of Oscilloscope Screen, 164
- 9.11 Oscilloscope Voltage Calibrator, 165
- 9.12 Recording from Oscilloscope Screen, 167

10 R-F Test Oscillators and Signal Generators 169

- 10.1 Professional Laboratory-Type R-F Signal Generator, 169
- 10.2 Service-Type R-F Signal Generator, 171
- 10.3 TV-FM Sweep Signal Generator, 173

- 10.4 Visual Alignment with Signal Generator, 176
- 10.5 TV Linearity-Pattern Generator, 177
- 10.6 External Modulator for Signal Generators, 179
- 10.7 Audio Extractor for Signal Generators, 180
- 10.8 Calibration of Signal Generators, 181

11 Audio Test Oscillators 184

- 11.1 Simple Single-Frequency Audio Oscillators, 184
- 11.2 Transistorized Phase-Shift Oscillator, 186
- 11.3 Principle of the RC-Tuned Variable-Frequency Oscillator, 187
- 11.4 Professional Audio Oscillator, 187
- 11.5 Commercial Sine- and Square-Wave Generator, 190
- 11.6 Calibration of Audio Oscillators, 192

12 Frequency-Measuring Devices for Radio Frequencies 196

- 12.1 Wide-Range Absorption Wavemeters, 196
- 12.2 Grid-Dip Oscillator, 199
- 12.3 Tunnel Diode Dip Meter, 199
- 12.4 Lecher Frame for Frequency Measurements, 201
- 12.5 Direct-Reading Microwave Frequency Meter, 202
- 12.6 Slotted Line as Microwave Frequency Meter, 203
- 12.7 Self-Excited Dual-Frequency Standard, 204
- 12.8 Crystal-Type Secondary Frequency Standard, 206
- 12.9 Heterodyne Frequency Meter, 208

13 Frequency-Measuring Devices for Audio Frequencies 211

- 13.1 Bridge-Type AF Meter, 211
- 13.2 Parallel-T AF Meter, 214
- 13.3 Electronic AF Meter, 216
- 13.4 Frequency Checking with Oscilloscope, 219

- 14 Audio-Amplifier Testing Devices 220**
- 14.1 A-F Signal Tracers, 220
 - 14.2 Distortion Meter, 223
 - 14.3 Tunable Professional Distortion Meter, 228
 - 14.4 Wave Analyzer, 232
 - 14.5 Square-Wave Generator, 238
 - 14.6 Use of Square Waves in Audio-Amplifier Testing, 238
 - 14.7 Intermodulation Measurements, 240
 - 14.8 Checking Frequency Response, 243
 - 14.9 Checking Gain, 243
 - 14.10 Checking Power Output, 244
 - 14.11 Commercial A-F Microvolter, 244
- 15 R-F Signal Tracers 247**
- 15.1 High-Gain R-F Signal Tracer, 247
 - 15.2 Sensitive AF-RF Signal Tracer with Visual and Aural Indication, 248
 - 15.3 Transistorized Signal Tracer, 250
 - 15.4 Tuned R-F Signal Tracer, 251
 - 15.5 R-F VTVM as Signal Tracer, 252
 - 15.6 Oscilloscope as R-F Signal Tracer, 252
 - 15.7 Signal Injectors for Rapid Trouble-Shooting, 253
- 16 Tube and Semiconductor Testers 255**
- 16.1 Static Characteristics of Tubes, 255
 - 16.2 Dynamic Characteristics of Tubes, 257
 - 16.3 Emission Testing of Tubes, 258
 - 16.4 Transconductance Testing of Tubes, 259
 - 16.5 Power-Output Testing of Tubes, 260
 - 16.6 Commercial Tube Tester, 260
 - 16.7 Static Characteristics of Semiconductor Diodes, 262
 - 16.8 Semiconductor Rectifier Tester, 264
 - 16.9 Rectifier D-C Tests, 265
 - 16.10 Transistor Testers, 265
 - 16.11 Commercial Transistor Tester, 267
 - 16.12 In-Circuit Transistor Tester, 268

17	Miscellaneous Instruments	273
17.1	<i>Q</i> Meter for Coil Testing, 273	
17.2	Professional Wide-Range <i>Q</i> Meter, 279	
17.3	Field Strength Meters, 282	
17.4	Modulation Monitor, 285	
	Index	291