

Contents

Foreword
 Preface
 Author's Preface

NOTE ON JOB CONTENT

Each of the jobs described below is set up in the following manner:

Objectives—The objectives of the job are enumerated and clearly stated.

Materials Required—All the materials, including test equipment and components required to do the job, are enumerated.

Introductory Information—The theory and basic principles involved in the job are clearly stated.

Procedure—A detailed step-by-step procedure is given for doing the job.

Questions—The conclusions which the student has reached are brought out by a series of pertinent questions.

JOB 1	CHARACTERISTICS OF A GASEOUS RECTIFIER	1
	Ionization in a Gaseous Rectifier. Arc Drop. Cold-cathode Gaseous Tubes—Glow Tubes. Rectifier with Resistive Load. Rectifier with <i>RL</i> load. Oscilloscope in Industrial Electronics.	
JOB 2	THYRATRON CHARACTERISTICS	7
	Thyratron Operation. Ionization Potential. Grid-control Characteristic. Negative- and Positive-grid Thyratron.	
JOB 3	RECTIFICATION CHARACTERISTICS OF A THYRATRON	11
	Thyratron Used as a Rectifier. The Control Locus. Determining Firing Delay Angle and Delay Time. D-C Amplitude Control of Firing Point.	
JOB 4	PHASE-SHIFT BRIDGE CIRCUIT	20
	<i>LR</i> Phase-shift Bridge Circuit. <i>RC</i> Phase-shift Bridge Circuit. Phase Relations.	
JOB 5	PHASE-SHIFT CONTROL OF A THYRATRON	25
	Phase Conditions for Control. Effect of Varying Phase of Control Voltage on Firing Point. Effect of Varying Amplitude of A-C Control Voltage on Firing Point.	
JOB 6	PHASE-SHIFT AND D-C AMPLITUDE CONTROL OF A THYRATRON	31
	Effect of Combining D-C Amplitude and Phase-shift Control on Firing Point of a Thyratron.	
JOB 7	CONTROL OF BIPHASE HALF-WAVE THYRATRON RECTIFIER	36
	Biphase System. Phase-shift Control of Biphase Half-wave Rectifier. Phase-shift and Amplitude Control.	
JOB 8	CHARACTERISTICS OF PHOTOTUBES	40
	Photoemission. Phototube Characteristics. Phototube Applications. Photo Circuit. Forward and Reverse Connection. Phototube Amplifiers. Experimental Techniques.	

JOB 9	RELAYS Function and Operation. Open- and Closed-circuit Relay System. D-C Light-sensitive Relay.	48
JOB 10	PHOTOELECTRIC RELAY FROM AN A-C SOURCE Circuit Operation. Forward and Reverse Connections.	53
JOB 11	TIMING CIRCUITS Measuring Time in Electronics. RC Charging Circuit. RC and RL Time Constants. Experimental Techniques in Observing Capacitor Charge and Discharge.	57
JOB 12	TIME-DELAY RELAY D-C-operated Time-delay Relays. A-C-operated Time-delay Relays.	64
JOB 13	ELECTRONIC TIMER Circuit Operation of Commercial Timer. Connections for Various Methods of Operation. Timer Ranges. Trouble Shooting.	69
JOB 14	ELECTRONIC RESISTANCE-SENSITIVE RELAY Normal Operation. Time Delay. Reverse Operation. Commercial Applications.	75
JOB 15	TRANSISTOR TIME-DELAY RELAY Transistor-operated Relay. Time-delay Relay. Precautions in Working with Transistors.	80
JOB 16	PHOTOTRANSISTOR AS A CONTROL DEVICE Characteristics of a Phototransistor. Phototransistor Relay.	84
JOB 17	CHARACTERISTICS OF A SATURABLE REACTOR Characteristics. Saturable Reactor Used in a Phase-shifting Network.	87
JOB 18	APPLICATIONS OF A SATURABLE REACTOR Phase-shift Control of a Thyatron by a Saturable Reactor. Saturable Reactor Used in a Light-dimming Circuit.	93
JOB 19	THE PEAKING TRANSFORMER Characteristics of a Peaking Transformer. Use of a Peaking Transformer.	98
JOB 20	THREE-PHASE HALF-WAVE RECTIFIER Phase and Amplitude Relations in a Three-phase System. Three-phase Half-wave Rectifier without a Transformer. Three-phase Half-wave Rectifier with Transformer.	102
JOB 21	THREE-PHASE FULL-WAVE BRIDGE RECTIFIER Six-phase Half-wave Rectifier. Three-phase Full-wave Bridge Rectifier. Phase-shift Control of a Polyphase Rectifier. Waveforms.	107
JOB 22	D-C SHUNT-MOTOR OPERATION Characteristics of a D-C Shunt Motor. Varying Speed of a D-C Shunt Motor. Measuring Counter-EMF of a Motor. Dynamic Braking. Reversing Direction of Rotation.	113
JOB 23	THYRATRON CONTROL OF THE SPEED OF A D-C MOTOR D-C Voltage for the Motor Windings. Controlling Motor Speed by Grid Control of a Thyatron. Motor-control Circuit.	118
JOB 24	AUTOMATIC CONTROL OF MOTOR SPEED Automatic-speed-control System (A-S-C). Elementary A-S-C Circuit. Practical A-S-C Circuit.	122
JOB 25	A COMMERCIAL ELECTRONIC MOTOR CONTROL FOR FRACTIONAL-HORSEPOWER D-C SHUNT MOTORS A Commercial Motor-control Unit. Safety Time-delay Relay. Shunt Field D-C Source. Armature D-C Source. Control Box Circuit.	127
JOB 26	REGULATED ELECTRONIC POWER SUPPLIES A Simple Voltage Regulator. Ballast-tube Regulator. VR-tube Regulator. Vacuum-tube Regulators. Characteristics of a Regulated Supply.	133
JOB 27	THE SUPERHETERODYNE RECEIVER PART I: THE I-F AMPLIFIER How a Superheterodyne Receiver Works. The I-F Amplifiers. Alignment of I-F Amplifiers.	138

JOB 28	THE SUPERHETERODYNE RECEIVER PART II: THE PENTAGRID CONVERTER	142
	Pentagrid Converter in a Radio Receiver. Loop and Ferri-loop Antenna. Automatic Volume Control. Experimental Superhet Receiver. Alignment Procedure.	
JOB 29	RADIO CONTROL SYSTEM	147
	System Block Diagram. Transmitter of a Radio-controlled Door Opener. Receiver of a Radio-controlled Door Opener. Operation of Balanced Detector. Experimental Radio-control Circuit.	
JOB 30	-tone SIGNALING CONTROL SYSTEM	153
	A Tone Signaling System. Commercial Tone-operated Receiver. Selective Amplifier. Experimental Tone-operated Receiver.	
JOB 31	COMPUTER FUNDAMENTALS	158
	Computer Orientation. Stored-program Concept. Basic Diode Logic Circuits. AND Circuit. OR Circuit. Combined AND-OR Circuits.	
JOB 32	LOGIC INVERTER	164
	D-C Inverter.	
JOB 33	BINARY ADDITION AND COMPUTER ADDERS	166
	Two-state Nature of Computer Components. Binary Arithmetic. Binary Half Adder. Truth Table. Full Adder.	
JOB 34	TRIGGERS	171
	Use in Computers. Trigger Operation. Trigger Speed. Reset. D-C Input. Negative-shift Input. Binary Input. Outputs. Experimental Circuit.	
JOB 35	COUNTERS	176
	Use in Computers. Binary-input Trigger Used as Counter. Modified Binary Counter. Binary-coded-decimal Counter Used as an Accumulator.	
JOB 36	TRANSISTOR COMPUTER CIRCUITS	180
	Vacuum Tubes Versus Transistors in Computers. Transistor Mode of Operation.	
JOB 37	THE SYNCHRO GENERATOR AND MOTOR	183
	Transmitting Angular Motion of a Shaft. Synchro Generator and Receiver. Synchros Used for Remote Indicator System. Rotor Connections. Aligning Synchro Generator at Electrical Zero.	
JOB 38	DIFFERENTIAL SYNCHRO	190
	Characteristics. Differential Synchro Generator (<i>DG</i>) Connected for Subtraction. Differential Synchro System for Addition. Differential Synchro Motor (<i>DM</i>). <i>DM</i> Connections to Show Sum or Difference of Two Generator Inputs. Zeroing the <i>DG</i> .	
JOB 39	THE SYNCHRO CONTROL TRANSFORMER AND ITS USE IN SERVOMECHANISMS	197
	Delivering Power to a Load. The Control Transformer (<i>CT</i>) Characteristics. Block Diagram Servo System. Zeroing the <i>CT</i> .	