

# Contents

---

<b>PREFACE</b>	<b>xiii</b>
<b>SURVEY OF ELECTRONICS</b>	<b>1</b>
<b>CHAPTER 1 ELECTRICITY</b>	<b>11</b>
1-1 Negative and Positive Polarities	11
1-2 Electrons and Protons in the Atom	12
1-3 Structure of the Atom	14
1-4 The Coulomb Unit of Charge	17
1-5 The Volt Unit of Potential Difference	20
1-6 Charge in Motion Is Current	22
1-7 Resistance Is Opposition to Current	27
1-8 The Closed Circuit	28
1-9 Direct Current (DC) and Alternating Current (AC)	31
1-10 Sources of Electricity	33
<b>CHAPTER 2 OHM'S LAW</b>	<b>39</b>
2-1 The Current $I = V/R$	39
2-2 The Voltage $V = IR$	41
2-3 The Resistance $R = V/I$	41
2-4 Practical Units	42
2-5 Multiple and Submultiple Units	43
2-6 The Linear Proportion between $V$ and $I$	43
2-7 Power	45
2-8 Power Dissipation in Resistance	47
2-9 Electric Shock	49
<b>CHAPTER 3 SERIES CIRCUITS</b>	<b>54</b>
3-1 Why $I$ Is the Same in All Parts of a Series Circuit	54
3-2 Total $R$ Equals the Sum of All Series Resistances	56
3-3 Series $IR$ Voltage Drops	58
3-4 The Sum of Series $IR$ Drops Equals the Applied $V_T$	59
3-5 Polarity of $IR$ Voltage Drops	61
3-6 Polarities to Chassis Ground	62
3-7 Total Power in a Series Circuit	63
3-8 Series-Aiding and Series-Opposing Voltages	64
3-9 Analyzing Series Circuits	64
3-10 Effect of an Open Circuit in a Series Path	67

<b>CHAPTER 4 PARALLEL CIRCUITS</b>	<b>74</b>
4-1 The Applied Voltage $V_A$ is the Same across Parallel Branches	74
4-2 Each Branch $I$ Equals $V_A/R$	75
4-3 The Main-Line $I_T$ Equals the Sum of the Branch Currents	76
4-4 Resistances in Parallel	78
4-5 Conductances in Parallel	82
4-6 Total Power in Parallel Circuits	83
4-7 Analyzing Parallel Circuits	84
4-8 Effect of an Open Branch in Parallel Circuits	84
4-9 Effect of a Short Circuit across Parallel Branches	85
<b>CHAPTER 5 SERIES-PARALLEL CIRCUITS</b>	<b>91</b>
5-1 Finding $R_T$ for Series-Parallel Resistances	91
5-2 Resistance Strings in Parallel	92
5-3 Resistance Banks in Series	94
5-4 Resistance Banks and Strings in Series-Parallel	95
5-5 Analyzing Series-Parallel Circuits	97
5-6 Wheatstone Bridge	100
5-7 Chassis-Ground Connections	101
5-8 Voltages Measured to Chassis Ground	102
5-9 Opens and Shorts in Series-Parallel Circuits	104
<b>REVIEW OF CHAPTERS 1 TO 5</b>	<b>113</b>
<b>CHAPTER 6 VOLTAGE DIVIDERS AND CURRENT DIVIDERS</b>	<b>116</b>
6-1 Series Voltage Dividers	116
6-2 Current Divider with Two Parallel Resistances	118
6-3 Current Division by Parallel Conductances	119
6-4 Series Voltage Divider with Parallel Load Current	120
6-5 Design of a Loaded Voltage Divider	122
<b>CHAPTER 7 DIRECT-CURRENT METERS</b>	<b>126</b>
7-1 Moving-Coil Meter	126
7-2 Measurement of Current	129
7-3 Meter Shunts	131
7-4 The Ayrton or Universal Shunt	133
7-5 Voltmeters	135
7-6 Loading Effect of a Voltmeter	140
7-7 Ohmmeters	142

7-8	Multimeters	147
7-9	Digital Meters	150
7-10	Meter Applications	151
7-11	Checking Continuity with the Ohmmeter	153
<b>REVIEW OF CHAPTERS 6 AND 7</b>		<b>159</b>
<b>CHAPTER 8 KIRCHHOFF'S LAWS</b>		<b>161</b>
8-1	Kirchhoff's Current Law	161
8-2	Kirchhoff's Voltage Law	163
8-3	Method of Branch Currents	164
8-4	Node-Voltage Analysis	167
8-5	Method of Mesh Currents	169
<b>CHAPTER 9 NETWORK THEOREMS</b>		<b>175</b>
9-1	Superposition	175
9-2	Thevenin's Theorem	177
9-3	Thevenizing a Circuit with Two Voltage Sources	180
9-4	Thevenizing a Bridge Circuit	182
9-5	Norton's Theorem	184
9-6	Thevenin-Norton Conversions	187
9-7	Conversion of Voltage and Current Sources	189
9-8	Millman's Theorem	191
9-9	T and $\pi$ Networks	193
<b>REVIEW OF CHAPTERS 8 AND 9</b>		<b>201</b>
<b>CHAPTER 10 CONDUCTORS AND INSULATORS</b>		<b>203</b>
10-1	Function of the Conductor	203
10-2	Standard Wire Gage Sizes	204
10-3	Types of Wire Conductors	206
10-4	Printed Wiring	207
10-5	Switches	208
10-6	Fuses	210
10-7	Pilot Lamps	212
10-8	Wire Resistance	212
10-9	Temperature Coefficient of Resistance	214
10-10	Ion Current in Liquids and Gases	216
10-11	Electrons and Hole Charges in Semiconductors	218
10-12	Insulators	219
<b>CHAPTER 11 RESISTORS</b>		<b>225</b>
11-1	Resistor Types	225
11-2	Variable Resistors	227

11-3	Potentiometers and Rheostats	228
11-4	Resistor Color Coding	230
11-5	Power Rating of Resistors	232
11-6	Choosing the Resistor for a Circuit	232
11-7	Series and Parallel Combinations of Resistors	233
11-8	Resistor Troubles	234
<b>CHAPTER 12</b>	<b>BATTERIES</b>	<b>240</b>
12-1	Functions of Batteries	240
12-2	The Voltaic Cell	241
12-3	Carbon-Zinc Dry Cell	243
12-4	Series and Parallel Cells	245
12-5	Lead-Acid Wet Cell	247
12-6	Types of Electromotive Cells	250
12-7	Internal Resistance of a Generator	252
12-8	Matching a Load Resistance to the Generator	257
<b>REVIEW OF CHAPTERS 10 TO 12</b>		<b>263</b>
<b>CHAPTER 13</b>	<b>MAGNETISM</b>	<b>265</b>
13-1	The Magnetic Field	265
13-2	Magnetic Flux $\phi$	267
13-3	Flux Density $B$	268
13-4	Induction by the Magnetic Field	270
13-5	Air Gap of a Magnet	271
13-6	Types of Magnets	272
13-7	Ferrites	275
13-8	Magnetic Shielding	275
13-9	The Hall Effect	276
<b>CHAPTER 14</b>	<b>MAGNETIC UNITS</b>	<b>280</b>
14-1	Ampere-turns ( $NI$ )	280
14-2	Field Intensity ( $H$ )	281
14-3	Permeability ( $\mu$ )	282
14-4	$B$ - $H$ Magnetization Curve	284
14-5	Magnetic Hysteresis	285
14-6	Ohm's Law for Magnetic Circuits	287
14-7	Relations between Magnetic Units	288
14-8	Comparison of Magnetic and Electric Fields	289
<b>CHAPTER 15</b>	<b>ELECTROMAGNETIC INDUCTION</b>	<b>294</b>
15-1	Magnetic Field around an Electrical Current	294
15-2	Magnetic Polarity of a Coil	296

15-3	Motor Action between Two Magnetic Fields	298
15-4	Induced Current	300
15-5	Lenz' Law	301
15-6	Generating an Induced Voltage	302
15-7	Faraday's Law of Induced Voltage	303
<b>CHAPTER 16</b>	<b>ALTERNATING VOLTAGE AND CURRENT</b>	<b>310</b>
16-1	Alternating-Voltage Generator	311
16-2	The Sine Wave	314
16-3	Alternating Current	316
16-4	Voltage and Current Values for a Sine Wave	317
16-5	Frequency	319
16-6	Period	321
16-7	Wavelength	322
16-8	Phase Angle	323
16-9	The Time Factor in Frequency and Phase	327
16-10	AC Circuits with Resistance	327
16-11	Nonsinusoidal AC Waveforms	329
16-12	Harmonic Frequencies	331
<b>CHAPTER 17</b>	<b>THE 60-Hz AC POWER LINE</b>	<b>337</b>
17-1	Advantages of 120-V 60-Hz AC Power	337
17-2	Motors and Generators	338
17-3	Fluorescent Lighting	340
17-4	Residential Wiring	341
17-5	Three-Phase Power	344
<b>REVIEW OF CHAPTERS 13 TO 17</b>		<b>348</b>
<b>CHAPTER 18</b>	<b>INDUCTANCE</b>	<b>352</b>
18-1	Induction by Alternating Current	352
18-2	Self-inductance	354
18-3	Self-induced Voltage $v_L$	356
18-4	How $v_L$ Opposes a Change in Current	356
18-5	Mutual Inductance	358
18-6	Transformers	360
18-7	Core Losses	366
18-8	Types of Cores	367
18-9	Variable Inductance	368
18-10	Inductances in Series or Parallel	369
18-11	Stray Inductance	371
18-12	Energy in Magnetic Field of Inductance	372
18-13	Troubles in Coils	372

<b>CHAPTER 19</b>	<b>INDUCTIVE REACTANCE</b>	<b>379</b>
19-1	How $X_L$ Reduces the Amount of $I$	379
19-2	$X_L = 2\pi fL$	381
19-3	Series or Parallel Inductive Reactances	384
19-4	Ohm's Law Applied to $X_L$	385
19-5	Applications of $X_L$ for Different Frequencies	385
19-6	Waveshape of $v_L$ Induced by Sine-Wave Current	386
<b>CHAPTER 20</b>	<b>INDUCTIVE CIRCUITS</b>	<b>394</b>
20-1	Sine-Wave $i_L$ Lags $v_L$ by $90^\circ$	394
20-2	$X_L$ and $R$ in Series	395
20-3	Impedance ( $Z$ )	398
20-4	$X_L$ and $R$ in Parallel	400
20-5	$Q$ of a Coil	403
20-6	AF and RF Chokes	405
20-7	The General Case of Inductive Voltage	407
20-8	Calculating the $L/R$ Time Constant	408
<b>REVIEW OF CHAPTERS 18 TO 20</b>		<b>415</b>
<b>CHAPTER 21</b>	<b>CAPACITANCE</b>	<b>418</b>
21-1	How Charge Is Stored in the Dielectric	418
21-2	Charging and Discharging a Capacitor	420
21-3	The Farad Unit of Capacitance	422
21-4	Typical Capacitors	424
21-5	Capacitor Color Coding	429
21-6	Parallel Capacitances	430
21-7	Series Capacitances	430
21-8	Stray Capacitive and Inductive Effects	431
21-9	Energy in Electrostatic Field of Capacitance	434
21-10	Troubles in Capacitors	434
<b>CHAPTER 22</b>	<b>CAPACITIVE REACTANCE</b>	<b>442</b>
22-1	Alternating Current in a Capacitive Circuit	442
22-2	$X_C = 1/(2\pi fC)$	444
22-3	Series or Parallel Capacitive Reactances	446
22-4	Ohm's Law Applied to $X_C$	447
22-5	Applications of Capacitive Reactance	448
22-6	Sine-Wave Charge and Discharge Current	448
<b>CHAPTER 23</b>	<b>CAPACITIVE CIRCUITS</b>	<b>457</b>
23-1	Sine-Wave $v_C$ Lags $i_C$ by $90^\circ$	457
23-2	$X_C$ and $R$ in Series	458
23-3	$X_C$ and $R$ in Parallel	461

23-4	RF and AF Coupling Capacitors	463
23-5	Capacitive Voltage Dividers	464
23-6	The General Case of Capacitive Current $i_C$	465
23-7	Calculating the RC Time Constant	466
<b>CHAPTER 24</b>	<b>RC AND L/R TIME CONSTANTS</b>	<b>472</b>
24-1	Response of Resistance Alone	472
24-2	L/R Time Constant	473
24-3	High Voltage Produced by Opening RL Circuit	474
24-4	RC Time Constant	476
24-5	RC Charge and Discharge Curves	479
24-6	High Current Produced by Short-circuiting RC Circuit	479
24-7	RC Waveshapes	481
24-8	Long and Short Time Constants	483
24-9	Charge and Discharge with Short RC Time Constant	483
24-10	Long Time Constant for RC Coupling Circuit	484
24-11	Universal Time Constant Graph	486
24-12	Comparison of Reactance and Time Constant	488
<b>REVIEW OF CHAPTERS 21 TO 24</b>		<b>494</b>
<b>CHAPTER 25</b>	<b>ALTERNATING-CURRENT CIRCUITS</b>	<b>498</b>
25-1	AC Circuits with Resistance but No Reactance	498
25-2	Circuits with $X_L$ Alone	499
25-3	Circuits with $X_C$ Alone	501
25-4	Opposite Reactances Cancel	501
25-5	Series Reactance and Resistance	503
25-6	Parallel Reactance and Resistance	505
25-7	Series-Parallel Reactance and Resistance	507
25-8	Real Power	507
25-9	AC Meters	510
25-10	Wattmeters	510
25-11	Summary of Types of Ohms in AC Circuits	511
25-12	Summary of Types of Phasors in AC Circuits	512
<b>CHAPTER 26</b>	<b>COMPLEX NUMBERS FOR AC CIRCUITS</b>	<b>519</b>
26-1	Positive and Negative Numbers	519
26-2	The $j$ Operator	520

26-3	Definition of a Complex Number	521
26-4	How Complex Numbers Are Applied to AC Circuits	522
26-5	Impedance in Complex Form	523
26-6	Operations with Complex Numbers	524
26-7	Magnitude and Angle of a Complex Number	526
26-8	Polar Form of Complex Numbers	527
26-9	Converting Polar to Rectangular Form	528
26-10	Complex Numbers in Series AC Circuits	530
26-11	Complex Numbers in Parallel AC Circuits	532
26-12	Combining Two Complex Branch Impedances	533
26-13	Combining Complex Branch Currents	534
26-14	Parallel Circuit with Three Complex Branches	535

**CHAPTER 27 RESONANCE 541**

27-1	The Resonance Effect	541
27-2	Series Resonance	542
27-3	Parallel Resonance	546
27-4	The Resonant Frequency $f_r = 1/(2\pi\sqrt{LC})$	550
27-5	Q Magnification Factor of Resonant Circuit	552
27-6	Bandwidth of Resonant Circuit	555
27-7	Tuning	558
27-8	Mistuning	560
27-9	Analysis of Parallel Resonant Circuits	561
27-10	Damping of Parallel Resonant Circuits	563
27-11	Choosing $L$ and $C$ for a Resonant Circuit	564

**CHAPTER 28 FILTERS 570**

28-1	Examples of Filtering	570
28-2	Direct Current Combined with Alternating Current	571
28-3	Transformer Coupling	574
28-4	Capacitive Coupling	575
28-5	Bypass Capacitors	577
28-6	Filter Circuits	580
28-7	Low-pass Filters	581
28-8	High-pass Filters	582
28-9	Resonant Filters	584
28-10	Interference Filters	586

**REVIEW OF CHAPTERS 25 TO 28 593**

**CHAPTER 29 VACUUM TUBES 597**

29-1	Rectifiers, Amplifiers, and Oscillators	598
29-2	Construction of Tubes	599



29-3	Diodes	600
29-4	Plate Current	602
29-5	Diode Rectifier Circuit	602
29-6	Triodes	604
29-7	How a Triode Amplifies the Control-Grid Voltage	606
29-8	Triode Characteristics	608
29-9	Tube Parameters	609
29-10	Tetrodes	610
29-11	Pentodes	612
29-12	Tube Types	614
29-13	The Cathode-Ray Tube (CRT)	616
29-14	Troubles in Vacuum Tubes	617
<b>CHAPTER 30</b>	<b>SEMICONDUCTOR DIODES AND TRANSISTORS</b>	<b>624</b>
30-1	Types of Semiconductor Devices	625
30-2	Characteristics of Semiconductors	626
30-3	N-type and P-type Doping	627
30-4	Current in Semiconductors	629
30-5	The PN Junction	630
30-6	Diode Rectifier Circuits	633
30-7	Transistors	636
30-8	Transistor Amplifier Circuits	639
30-9	The CE Amplifier Circuit	642
30-10	Collector Characteristic Curves	645
30-11	Load-Line Analysis	647
30-12	Bias Stabilization	651
30-13	Field-Effect Transistor (FET)	652
30-14	Silicon Controlled Rectifier (SCR)	655
30-15	Types of Transistors	657
30-16	Special-Purpose Diodes	659
30-17	Transistor Troubles	660
<b>REVIEW OF CHAPTERS 29 AND 30</b>		<b>669</b>
<b>CHAPTER 31</b>	<b>INTEGRATED CIRCUITS</b>	<b>673</b>
31-1	Types of Integrated Circuits	673
31-2	Production of Integrated Circuits	675
31-3	Integrated Components	676
31-4	The Differential Amplifier	679
31-5	Linear IC Applications	681
<b>CHAPTER 32</b>	<b>DIGITAL ELECTRONICS</b>	<b>685</b>
32-1	Binary Numbers	685
32-2	Binary Arithmetic	688

32-3	Symbolic Logic for Switching Circuits	689
32-4	Truth Tables	691
32-5	Basic Logic Circuits	693
32-6	Diode Gate Circuits	694
32-7	Diode-Transistor Logic (DTL)	695
32-8	Transistor-Transistor Logic (TTL)	698
32-9	Multivibrator (MV) Circuits	700
32-10	Flip-flop Circuits	701
32-11	Counters	704
<b>REVIEW OF CHAPTERS 31 AND 32</b>		<b>711</b>
<b>BIBLIOGRAPHY</b>		<b>713</b>
<b>APPENDIX A</b>	<b>ELECTRONIC FREQUENCY SPECTRUM</b>	<b>717</b>
<b>APPENDIX B</b>	<b>FCC FREQUENCY ALLOCATIONS FROM 30 kHz TO 300,000 MHz</b>	<b>719</b>
<b>APPENDIX C</b>	<b>ALPHABETICAL LISTING OF THE CHEMICAL ELEMENTS</b>	<b>721</b>
<b>APPENDIX D</b>	<b>PHYSICS UNITS</b>	<b>724</b>
<b>APPENDIX E</b>	<b>TRIGONOMETRIC FUNCTIONS</b>	<b>728</b>
<b>APPENDIX F</b>	<b>ELECTRICAL SYMBOLS AND ABBREVIATIONS</b>	<b>732</b>
<b>APPENDIX G</b>	<b>COLOR CODES</b>	<b>735</b>
<b>APPENDIX H</b>	<b>SOLDERING AND TOOLS</b>	<b>741</b>
<b>APPENDIX I</b>	<b>SCHEMATIC SYMBOLS</b>	<b>744</b>
<b>ANSWERS TO SELF-EXAMINATIONS</b>		<b>746</b>
<b>ANSWERS TO ODD-NUMBERED PROBLEMS</b>		<b>751</b>
<b>INDEX</b>		<b>759</b>