

Contents

PREFACE

v

Part ONE: HOW ELECTRONICS COMPONENTS WORK

1

1. FUNDAMENTALS AND BASIC CONCEPTS

3

- 1.1 Constitution of Matter. 1.2 Electrical Quantities. 1.3 D-C Circuits. 1.4 Magnetism. 1.5 Sources of Electricity. 1.6 Alternating Current. 1.7 Inductance. 1.8 Capacitance. 1.9 A-C Circuits. 1.10 Transients and the R-C Circuit. 1.11 Transients and the R-L Circuit. 1.12 Transients and the A-C Circuit. 1.13 Nonsinusoidal Waves. 1.14 Nonsinusoidal Transient Circuits. Summary. Questions.

2. VACUUM TUBES, GAS TUBES, AND SEMICONDUCTORS

53

- 2.1 Thermionic Emission. 2.2 Diodes. 2.3 Triodes. 2.4 Tetrodes. 2.5 Pentodes. 2.6 Special-Purpose Tubes. 2.7 Gas-Filled Tubes. 2.8 Semiconductor Diodes. 2.9 Transistors. 2.10 Tube Manuals and Semiconductor Guides. Summary. Questions.

3. SENSORY DEVICES

98

- 3.1 Switches. 3.2 Microphones and Pickups. 3.3 Resistive-Wire Sensors. 3.4 Induction Transducers. 3.5 Capacity-Type Sensors. 3.6 Thermocouples. 3.7 Tachometers.

vii

3.8 Photosensitive Devices. 3.9 Vacuum-Tube Transducers.
 3.10 Ion Sensors. 3.11 Camera Tubes. 3.12 Frequency-
 Selection Sensors. 3.13 Input Devices. Summary. Questions.

4. LOAD DEVICES **137**

4.1 Electrical Loads. 4.2 Acoustical Loads. 4.3 Mechanical
 Loads. 4.4 Magnetic Loads. 4.5 Chemical Loads. 4.6 R-F
 and Heat Loads. 4.7 Light Loads. 4.8 X-Ray Loads.
 Summary. Questions.

Part TWO: BASIC CIRCUITS **173**

5. POWER-SUPPLY CIRCUITS **175**

5.1 Half-Wave Rectifiers. 5.2 Full-Wave Rectifiers.
 5.3 Bridge Rectifiers. 5.4 Voltage Doublers. 5.5 Voltage
 Multipliers. 5.6 Capacitance Filters. 5.7 Inductance Filters.
 5.8 L-C Filters. 5.9 R-C Filters. 5.10 Voltage Regulators.
 5.11 Constant-Voltage Transformers. Summary. Questions.

6. SPECIAL RECTIFIER CIRCUITS **201**

6.1 Grid-Controlled Rectifiers. 6.2 Mercury-Pool Rectifiers.
 6.3 Inverters. 6.4 Vibrators. 6.5 Signal Rectification.
 6.6 Diode Detectors. 6.7 Grid-Leak Detectors. 6.8 Plate
 Detectors. 6.9 Regenerative Detectors. 6.10 Heterodyne
 Detectors. 6.11 The Superregenerative Detector. 6.12 Limiter-
 Discriminator FM Detection. 6.13 Ratio Detectors.
 6.14 Quadrature Detectors. Summary. Questions.

7. SWITCHING AND TIMING CIRCUITS **229**

7.1 The Instantaneous Relay. 7.2 Time-Delay Relays.
 7.3 Timers. 7.4 Multivibrator Switching. 7.5 Time-Delay
 Circuits. 7.6 Gating. 7.7 Inverse-Parallel Switching.
 Summary. Questions.

8. AMPLIFIER CIRCUITS **248**

8.1 Classification of Amplifiers. 8.2 Distortion in Amplifiers.
 8.3 Coupling Methods. 8.4 D-C Amplifiers. 8.5 Video
 Amplifiers. 8.6 Hi-Fi Amplifiers. 8.7 Tuned Amplifiers.
 8.8 Feedback in Amplifiers. 8.9 Cathode Followers.
 8.10 Phase Inverters. 8.11 Magnetic Amplifiers. Summary.
 Questions.

9. OSCILLATOR CIRCUITS	290
9.1 Variable-Frequency L-C Oscillators.	9.2 Transit Time in Oscillators.
9.3 Relaxation Oscillators.	9.4 Fixed-Frequency Oscillators.
Summary.	Questions.
10. SPECIAL CIRCUITS	318
10.1 Modulation.	10.2 Frequency Conversion.
10.3 Multiplexing.	10.4 Limiting Circuits.
10.5 Clamping Circuits.	10.6 Peaking Circuits.
10.7 Gating and Counting Circuits.	Summary.
	Questions.
Part THREE: APPLICATIONS	343
11. RECTIFIER APPLICATIONS	347
11.1 Magnetic Chuck.	11.2 Electroplating.
11.3 Battery Charger.	11.4 Battery Charger with Regulator.
11.5 Air Filter.	11.6 A-C Voltage Regulator.
11.7 Laboratory-Type Power Supply.	11.8 Photoflash Unit.
12. CONTROLLED RECTIFIER APPLICATIONS	353
12.1 Machine-Tool Feed Control.	12.2 Magnetic Clutch.
12.3 Variable D-C Power Supply.	12.4 Power Supply Regulated by Amplified Correction Signal.
12.5 Dynamatic Eddy-Current Clutch.	12.6 Transistorized D-C Inverter and Rectifier.
12.7 Solid-State D-C Motor-Speed Control.	12.8 Phototube-Thyratron Speed and Direction Control.
13. INSTANTANEOUS, TIMING, AND SEQUENCE CONTROLS	359
13.1 Machine-Tool Switch.	13.2 Garage-Door Opener.
13.3 Smoke-Detection Control.	13.4 Flame-Failure Control.
13.5 Antenna Switch.	13.6 Headlight-Dimming Circuit.
13.7 Assembly-Line Radioisotope Control.	13.8 Proximity Pickup.
13.9 A-C Time Delay Relay.	13.10 Photocell Time-Delay Control.
13.11 Welding Timer.	13.12 High-Speed-Welder Control.
14. AMPLIFIERS	370
14.1 Intercom System.	14.2 Two-Stage Audio Amplifier.
14.3 Guitar Amplifier.	14.4 High-Fidelity Williamson-Type Amplifier.
14.5 Heart Monitor Pickup.	14.6 Stereophonic Amplifier.

15. RECEIVERS	375
15.1 Carrier-Current Receivers.	15.2 Superregenerative Receiver.
15.3 Regenerative Receiver.	15.4 A-C/D-C Vacuum-Tube Superheterodyne.
15.5 Transistor-Type Superheterodyne.	15.6 Communication Receiver.
15.7 FM Tuner.	15.8 Block Diagram of Black-and-White TV Receiver.
15.9 Block Diagram of Microwave Radar.	15.10 Block Diagram of Radio Telemetry Receiver System.
16. OSCILLATOR APPLICATIONS	383
16.1 Audio Oscillator.	16.2 Crystal Oscillator Standard.
16.3 Carrier-Current Transmitter.	16.4 Amateur CW Transmitter with vfo.
16.5 Amateur AM Transmitter with Crystal Control.	16.6 Block Diagram of FM Transmitter.
16.7 Block Diagram of Filter System Single-Side-Band.	16.8 Block Diagram of Color TV Transmitter.
16.9 Block Diagram of Radio Telemetry Transmitter.	
INDEX	391