

# CONTENTS

---

---

CHAPTER I. DIRECT CURRENT		1
1-1	Voltage	1
1-2	Current	2
1-3	Resistors in Combination	4
1-4	Graphical Description of Source and Load	10
1-5	Current Generators	11
1-6	Conductance	12
1-7	Nonlinear Resistance	12
CHAPTER II. GENERAL DIRECT CURRENT NETWORKS		15
2-1	Network Topology	17
2-2	Electrical Variables	18
2-3	Loop Currents	19
2-4	Mesh Currents	21
2-5	Branch Voltages	22
2-6	Kirchhoff's Voltage Law	23
2-7	Recapitulation	25
2-8	Mesh Analysis	25
2-9	Voltage Sources	25
2-10	Voltage Variables	26
2-11	Node and Branch Currents	29
2-12	Kirchhoff's Current Law	29
CHAPTER III. SIMULTANEOUS EQUATIONS		33
3-1	Triangularization	34
3-2	Determinants	37
3-3	Expansion of Third Order Determinant	38
3-4	Expansion of a Determinant by Minors	39
3-5	Complete Expansion	41
3-6	Cofactors	44
3-7	Cramer's Rule	45

CHAPTER IV. GENERAL NETWORK PROPERTIES		48
4-1	Thevenin's Theorem . . . . .	48
4-2	Wheatstone Bridge . . . . .	50
4-3	Conjugacy . . . . .	52
4-4	Two-Port Networks . . . . .	53
4-5	Equivalent T . . . . .	55
4-6	Two-Port Description . . . . .	57
4-7	Equivalent II Network . . . . .	58
4-8	Transformation between T and II . . . . .	59
4-9	Black-Box Variables . . . . .	60
4-10	Input and Output Resistance . . . . .	61
4-11	Image Impedances . . . . .	63
4-12	Attenuators . . . . .	64
CHAPTER V. CAPACITANCE		67
5-1	Conductors and Dielectrics . . . . .	67
5-2	Capacitance . . . . .	68
5-3	Capacitance Networks . . . . .	70
5-4	Interelectrode Capacitance . . . . .	71
5-5	Charging and Discharging . . . . .	73
5-6	Current Generator . . . . .	77
5-7	Sinusoidal Voltage . . . . .	77
CHAPTER VI. INDUCTANCE		79
6-1	Magnetic Flux . . . . .	79
6-2	Energy Storage . . . . .	80
6-3	Inductance Networks . . . . .	81
6-4	"Charge" and "Discharge" . . . . .	82
6-5	Mutual Inductance . . . . .	84
6-6	Sinusoidal Current . . . . .	86
CHAPTER VII. SERIES-TUNED CIRCUITS		87
7-1	Natural Oscillations . . . . .	87
7-2	Series Resonance . . . . .	89
7-3	Impedance . . . . .	90
CHAPTER VIII. COMPLEX NUMBERS		93
8-1	Review of Fundamentals . . . . .	93
8-2	Complex Exponentials . . . . .	94
8-3	Graphical Representation . . . . .	94
8-4	Application to Linear Differential Equations . . . . .	95

8-5	Complex Current and Voltage . . . . .	98
8-6	Impedance . . . . .	99
8-7	Series-Parallel Combinations . . . . .	100
8-8	Addition of Currents or Voltages . . . . .	100
8-9	Parallel Resonance . . . . .	101
8-10	Power . . . . .	104
CHAPTER IX. ALTERNATING CURRENT NETWORKS . . . . .		108
9-1	Mutual Inductance . . . . .	110
9-2	Reciprocal Inductances . . . . .	113
9-3	Network Equations . . . . .	113
9-4	Transformer Representation . . . . .	116
9-5	Ideal Transformers . . . . .	117
9-6	Leakage Inductance . . . . .	119
9-7	Practical Transformers . . . . .	122
CHAPTER X. SPECIFIC AC NETWORKS . . . . .		126
10-1	Simple Radio-Frequency Transformers . . . . .	126
10-2	Double-Tuned Transformers . . . . .	128
10-3	Critical Coupling . . . . .	129
10-4	Frequency-Modulation Discriminator . . . . .	133
10-5	Bridge Circuits . . . . .	134
10-6	Bridged-T's . . . . .	136
10-7	Parallel-T . . . . .	139
CHAPTER XI. IMPEDANCE MATCHING . . . . .		143
11-1	Thevenin's Theorem . . . . .	143
11-2	Output Power . . . . .	144
11-3	Matching Sections . . . . .	146
11-4	Matched Impedance Operation . . . . .	148
11-5	Cascaded Sections . . . . .	149
11-6	Mismatch Effects . . . . .	151
11-7	Hyperbolic Functions . . . . .	156
11-8	Logarithmic Expressions . . . . .	158
11-9	Symmetrical Sections . . . . .	159
11-10	Long Chains . . . . .	161
CHAPTER XII. DIODES . . . . .		163
12-1	Nonlinear Circuit Elements . . . . .	163
12-2	Thermionic Diodes . . . . .	164
12-3	Graphical Solutions . . . . .	167

12-4	Rectifiers	168
12-5	Power Supplies	170
CHAPTER XIII. AMPLIFIERS		175
13-1	Thermionic Triodes	175
13-2	Partial Derivatives	178
13-3	Small-Signal Parameters	179
13-4	Basic Amplifier Circuits	180
13-5	Internal Capacitances	182
13-6	Tetrodes and Pentodes	183
13-7	Transistors	185
13-8	Amplifier Configurations	188
13-9	Generalized Amplifiers	190
13-10	Gain	194
13-11	Feedback	196
13-12	Cathode Follower	197
13-13	Uses of Feedback	198
13-14	Transistors	201
CHAPTER XIV. NOISE		203
14-1	Diode Noise	204
14-2	Triode Noise	205
14-3	Thermal Noise	205
14-4	Equivalent Resistance	206
14-5	Noise Addition	207
14-6	Noise Figure	208
14-7	Input Impedance	209
14-8	Cascode Amplifier	211
14-9	Transistor Noise	212
CHAPTER XV. MODULATION, DEMODULATION AND DISTORTION		215
15-1	Nonlinearity	215
15-2	Amplitude Modulation	216
15-3	Demodulation	218
15-4	Frequency Modulation and Phase Modulation	219
15-5	Fourier Series	221
15-6	Truncation of Series	228
15-7	Time Delay	229
15-8	Differentiation and Integration	230
	Problems	232
	Answers	241
	Index	255