

## CONTENTS

	Page
<b>CHAPTER 1. ELEMENTARY CIRCUIT CONCEPTS</b>	<b>1</b>
1-1 Circuit Theory and Its Relation to Field Theory	1
1-2 Consideration of a Simple Circuit at Different Frequencies	2
1-3 Circuit Parameters	4
1-4 The Resistance Parameter	5
1-5 The Inductance Parameter	6
1-6 The Capacitance Parameter	7
1-7 Kirchhoff's Laws	8
 <b>CHAPTER 2. GENERAL CONCEPTS AND DEFINITIONS</b>	 <b>9</b>
2-1 Preliminary Definitions	9
2-2 Generation of Alternating Voltages	10
2-3 Wave Shape	11
2-4 Sinusoidal Waves	12
2-5 Effective Value of Alternating Current	14
2-6 Effective Value of a Sinusoid	17
2-7 Measurement of the Effective Value of Current or Voltage	17
2-8 Average Value of an Alternating Current	22
2-9 Other Sinusoidal Waves	23
 <b>CHAPTER 3. COMPLEX ALGEBRA PHASORS</b>	 <b>26</b>
3-1 Complex Numbers	27
3-2 Development of Sine and Cosine Waves from a Revolving Vector	29
3-3 Addition of Complex Quantities	33
3-4 Subtraction of Complex Quantities	35
3-5 Multiplication of Complex Quantities	36
3-6 Division of Complex Quantities	37
3-7 The Conjugate of a Complex Quantity	39
3-8 Powers of a Complex Quantity	39
3-9 Roots of a Complex Quantity	40
3-10 The Logarithm of a Complex Quantity	41
3-11 Representation of a Constant-direction Vector Varying in Length Sinusoidally with Time	42
3-12 Representation of a Constant-velocity Rotating Time Vector Whose Magnitude Varies Logarithmically with Time	43
 <b>CHAPTER 4. CURRENT, VOLTAGE, POWER, AND ENERGY RELATIONS</b>	 <b>46</b>
4-1 Current Direction and Voltage Polarity	47
4-2 The Pure R Circuit Parameter	47
4-3 The Pure L Circuit Parameter	48
4-4 The Pure C Circuit Parameter	50
4-5 The R and L Circuit	53
4-6 The Mutual and Two-coil Circuit	56
4-7 The R and C Circuit	58
4-8 The R, L, and C Circuit	60
4-9 Power and Energy in an R Circuit	62
4-10 Power and Energy in an L Circuit	63
4-11 Power and Energy in a C Circuit	64
4-12 Power in an R, L, and C Circuit	65
4-13 Power and Energy in a Two-coil Mutual Circuit	66
4-14 Power, Volt-amperes, and Reactive Volt-amperes	67

4-15	Measurement of Power and Energy	71
4-16	Summary	73
<b>CHAPTER 5. USE OF PHASORS IN STEADY-STATE CIRCUIT ANALYSIS</b>		<b>79</b>
5-1	Validity of Using Phasors to Obtain A-C Steady-state Solutions	79
5-2	Significance of Voltage and Current Directions	87
5-3	A-C Steady-state Circuit Analysis	91
5-4	Use of Voltage and Current Phasors in Series-circuit Analysis	91
5-5	Use of Impedances in Series-circuit Analysis	93
5-6	Power-factor Correction in a Series Circuit	94
5-7	Use of Current and Voltage Phasors in Parallel-circuit Analysis	95
5-8	An Equivalent Series Impedance to Replace Impedances in Parallel	97
5-9	An Equivalent Parallel Impedance to Replace a Series Impedance	98
5-10	Conductance, Susceptance, and Admittance	100
5-11	Use of Power and Reactive Volt-amperes in Parallel-circuit Analysis	103
5-12	Power-factor Correction in Parallel Circuits	104
5-13	Use of Kirchhoff's Laws in Network Solutions	105
5-14	Use of Branch Currents in the Mesh Method	107
5-15	Use of Mesh (Loop) Currents in the Mesh Method	109
5-16	The Node Method	111
5-17	Simplified Procedure for the Node Method	112
5-18	Direct Formulation of Mesh Equations with Mutual Coupling	116
<b>CHAPTER 6. SPECIAL AIDS IN CIRCUIT ANALYSIS</b>		<b>129</b>
6-1	The Superposition Principle	129
6-2	The Equivalent Constant-voltage Source (Thevenin's Theorem)	130
6-3	The Equivalent Constant-current Source (Norton's Theorem)	133
6-4	Duals : RLC Parallel and Series Circuits	134
6-5	The Reciprocity Theorem	136
6-6	The Alternate Network Solution	137
6-7	$\Delta$ - and Y- network Equivalents	138
6-8	The Circle Diagram for a Series Circuit	140
6-9	The Circle Diagram for Parallel Circuit	142
6-10	The Series RLC Circuit near Resonance under Steady-state Conditions	143
6-11	The Parallel RLC Circuit near Resonance under Steady-state Conditions	151
6-12	The Parallel Coil-Capacitor Circuit in the Vicinity of Resonance	152
6-13	The Parallel Coil-Capacitor Circuit near Resonance under Steady-state Conditions	152
6-14	Maximum-power Transfer	154
6-15	Power and Reactive Volt-amperes by the Method of Conjugates	156
6-16	A Special Analysis Method for Two-node Networks	157
<b>CHAPTER 7. THREE-PHASE CIRCUIT ANALYSIS</b>		<b>167</b>
7-1	Polyphase Generators	167
7-2	Y-connected Generators	170
7-3	$\Delta$ -Connected Generators	171
7-4	Six-and 12-phase Voltage Systems	172
7-5	Balanced Y Load-Three-wire and Four-wire-No Line Impedances	173
7-6	Unbalanced Y Load-Four-wire-No Line Impedances	174
7-7	Balanced $\Delta$ Load-No Line Impedances	175
7-8	Unbalanced $\Delta$ Load – No Line Impedances	178
7-9	Power, Reactive Volt – amperes, and Power Factor in Three-phase Balanced Systems	179
7-10	Power, Reactive Volt – amperes, Volt – amperes, and Power Factor in Three-phase Unbalanced Systems	181
7-11	Instantaneous Power Flow in a Three-phase Balanced System	182
7-12	Power Measurement in Three-phase Systems	183
7-13	Balanced $\Delta$ and Y Loads in Phase Systems	187
7-14	Unbalanced Y Load – Three – wire with Line Impedances	189
7-15	Unbalanced Y Load – Four – wire with Line Impedances	191

7-16	The Unblanced $\Delta$ Load and Y Generator	192
7-17	The Unblanced Y Load and $\Delta$ Generator	193
7-18	The Unblanced $\Delta$ Load and $\Delta$ Generator	194
7-19	Sequence Indicators	195
7-20	The Method of Symmetrical components and Method of Resolving Three Phasors into Symmetrical Components	198
7-21	Use of the Method of Ymmetrical Components for a Y Generator with Unblanced Vlotages and Balanced Y Load	203
7-22	Use of the Method of Symmetrical Components for a $\Delta$ Generator and Balanced $\Delta$ Load	206
<b>CHAPTER 8. NONSINUSOIDAL PERIODIC WAVES</b>		<b>215</b>
8-1	The Fourier Series	216
8-2	Symmetry	218
8-3	Analytical Evaluation of Constants in a Fourier Series	221
8-4	Graphical Evaluation of Constants in Fourier Series by Numerical Integration	227
8-5	Effective Value of a Nonsinusoidal Current and Voltage	230
8-6	Average Power with Nonsinusoidal Current and Voltage	231
8-7	Volt-amperes with Nonsinusoidal Current and Voltage	232
8-8	Power Factor with Nonsinusoidal Current and Voltage	233
8-9	Circuit Analysis with Nonsinusoidal Current and Voltage (Constant Circuit Parameters)	233
8-10	Introduction of Harmonics Due to Nonlinear Circuit Parameters	236
8-11	Harmonics in a Balanced Three-phase Source	236
<b>CHAPTER 9. TRANSIENT ANALYSIS</b>		<b>247</b>
9-1	The Series RL Circuit with Direct Current Applied	248
9-2	The Series RL Circuit with Alternating Current Applied	252
9-3	The Series RC Circuit with Direct Current Applied	255
9-4	The Series RC Circuit with Alternating Current Applied	259
9-5	Series – parallel Circuits	260
9-6	Circuits Requiring Second – order Differential Equations with Direct Current Applied	262
9-7	Circuit Requiring Second – order Differential Equations with Alternating Current Applied	266
9-8	Series – parallel Circuits Requiring Second – order Differential Equations	266
9-9	Use of the Operator p	268
9-10	Inductively Coupled Circuits	269
9-11	Linear Differential Equations or the nth Order	270
9-12	Circuits in Which the Parameters Are Not Constant	271
<b>CHAPTER 10. MATHEMATICAL ANALOGUES</b>		<b>290</b>
10-1	Electromechanical Analogues	292
10-2	Solution of a Differential Equation by the Use of Analogues	297
10-3	An Electromechanical Device with a Moving Conductor	299
10-4	The D' Arsonval Mechanism	302
<b>INDEX</b>		<b>311</b>