

CONTENTS

		Page
	PART I BASIC CIRCUIT ANALYSIS	
Chapter 1	CIRCUIT ANALYSIS	
1-01	Is circuit analysis important?	3
1-02	How much of the subject will we cover?	4
1-03	Units of measure	5
Chapter 2	BASIC LAWS AND DEFINITIONS	
2-01	The force between charges	9
2-02	The summation of current	10
2-03	The summation of voltage	11
2-04	Ohm's law	13
2-05	Electromagnetic induction	14
2-06	Power as a function of current and voltage	16
2-07	In retrospect	17
Chapter 3	TYPES OF VOLTAGE AND CURRENT VARIATIONS	
3-01	Definition of terms	19
3-02	Direct current and voltage	20
3-03	Alternating current and voltage	21
3-04	Average and rms values	22
3-05	Form factor and crest factor	25
3-06		
Chapter 4	NOTATION	
4-01	The diversity of notation	30
4-02	Let us agree upon the following notation	30
4-03	Relation between indicated polarity and plotted wave	31
4-04	Other notation	32
4-05	Must the student learn this notation?	32
Chapter 5	THE ALGEBRA OF COMPLEX NUMBRES	
5-01	The problem	34
5-02	A solution	35
5-03	Defining the phasor that represents a sine wave	37
5-04	Phasors of rms value	38
5-05	An exception	38
5-06	Mathematical expression of a complex number	38
5-07	The rotational operators	39
5-08	Complex numbers and phasors	41
5-09	The algebra of complex numbers	42
Chapter 6	IMPEDANCE AND ADMITTANCE	
6-01	Imitating an old idea	49
6-02	Impedance	49
6-03	Admittance	51
Chapter 7	CIRCUIT PARAMETERS	
7-01	The function of the parameters	53
7-02	Relating the parameters to the physical composition of the circuit	53
7-03	The parameter resistance	54
7-04	The parameter inductance	57

7-05	The parameter capacitance	60
7-06	In retrospect	62
Chapter 8	THE CALCULATION OF POWER	
8-01	Instantaneous power to a circuit branch	65
8-02	Active and reactive power	67
8-03	Apparent power	68
Chapter 9	APPLICATION OF CURRENT OR VOLTAGE TO A BRANCH COMPOSED OF A SINGLE PARAMETER	
9-01	Background for the problem at hand	74
9-02	Resistance	74
9-03	Inductance	78
9-04	Capacitance	83
9-05	In retrospect	86
Chapter 10	APPLICATION OF CURRENT OR VOLTAGE TO A BRANCH COMPOSED OF PARAMETERS IN SERIES	
10-01	The series connection	89
10-02	Resistance, inductance, and capacitance	89
10-03	In retrospect	93
Chapter 11	APPLICATION OF CURRENT OR VOLTAGE TO PARALLEL BRANCHES COMPOSED OF PARAMETERS IN SERIES	
11-01	The parallel connection	99
11-02	A specific example	99
11-03	In retrospect	105
Chapter 12	EQUIVALENT SERIES AND PARALLEL BRANCHES	
12-01	Parallel-to-series transformation	111
12-02	Series-to-parallel transformation	112
12-03	In retrospect	113
Chapter 13	LOCUS DIAGRAMS	
13-01	Definition and procedure	119
13-02	Use	119
13-03	Current locus diagrams of the series RLC circuit	120
13-04	Voltage locus diagrams of the series RLC circuit	124
13-05	Current locus diagrams for complex impedances in parallel	125
13-06	Voltage locus diagrams for complex impedances in parallel	127
Chapter 14	RESONANCE PHENOMENA	
14-01	General definition	132
14-02	The series RLC circuit	132
14-03	The parallel circuit	139
14-04	A circuit that is resonant at all frequencies	142
14-05	Multiple resonance	143
14-06	In retrospect	144
Chapter 15	ANALYSIS OF CIRCUITS CONTAINING MORE THAN ONE SOURCE OF CURRENT OR VOLTAGE	
15-01	The problem	147
15-02	Rules that apply to all three methods	147
15-03	Direct application of Kirchhoff's laws	149
15-04	The Maxwell loop current method	152
15-05	The node method	155
15-06	In retrospect	158
Chapter 16	MAGNETIC FIELD COUPLING	
16-01	The problem	163

16-02	Magnetic field coupling	163
16-03	Circuit equations for a typical magnetically coupled circuit	164
16-04	Preparation for simplifying the equations of 16-03	165
16-05	Simplification of equations of 16-03	167
16-06	Leakage and coupling coefficients	170
16-07	The air-core transformer	170
16-08	Magnetic coupling between elements conductively connected in series	176
16-09	Magnetic coupling between elements conductively connected in parallel	179

PART II EXTENSION OF BASIC CIRCUIT ANALYSIS

Chapter 17 NONSINUSOIDAL WAVES

17-01	The problem	189
17-02	A solution	189
17-03	Evaluation of the constants	190
17-04	Simplification indigenous to certain types of symmetry	194
17-05	Graphical determination of coefficients	198
17-06	Exponential form of Fourier's series	202
17-07	Average value, rms value, and power	204
17-08	In retrospect	208

Chapter 18 NETWORK SIMPLIFICATIONS AND THEOREMS

18-01	Additional tools	210
18-02	The mesh-to-star transformation	210
18-03	The star-to-mesh transformation	212
18-04	Equivalent potential and current sources	216
18-05	Superposition theorem	219
18-06	Reciprocity theorem	225
18-07	Thevenin's and Norton's theorems	227
18-08	Two-terminal networks and maximum power transfer theorem	230
18-09	Four-terminal networks	233
18-10	More theorems to extend your horizons	237

PART III SPECIALIZATION – POLYPHASE POWER AND COMMUNICATION CIRCUITS

Chapter 19 POLYPHASE CIRCUITS

19-01	Introduction and definitions	249
19-02	Phase voltage in terms of line voltage	250
19-03	Equivalent star-and mesh-connected polyphase sources	252
19-04	Solution of star-generator-star-load networks	252
19-05	Solution of networks with mesh-connected loads	257
19-06	Combined loads	259
19-07	Power in a polyphase network	259
19-08	Measurement of power to a polyphase network	262
19-09	Phase conversion	265
19-10	Determination of phase sequence	266
19-11	Copper required of transmit power	267
19-12	In retrospect	268

Chapter 20 COMMUNICATION CIRCUITS

20-01	Two approximations	277
20-02	Equivalent series and parallel branches	278
20-03	Resonant series circuits	279
20-04	Resonant parallel circuits	285
20-05	Coupled circuits	289
20-06	In retrospect	296

INDEX		299
--------------	--	------------

