

contents

Foreword *vii*

Preface *ix*

General Remarks to the Student *xii*

1 Volts, Amps, Ohms, and Multimeters 1

2 DC Circuits, Thevenin's Theorem,
and Impedance Matching 5

3 DC Null (Comparison) Measurements;
The Potentiometer 9

4	Response of Linear Networks to AC Excitation; Attenuation and Phase-shift Measurements	13
5	Resonant <i>RLC</i> Circuits: The Impedance Concept	17
6	Square-wave (Transient) Response	23
7	Diode Characteristics	29
8	Rectifier Circuits	33
9	Power-supply Filters and Regulators	37
10	Silicon-controlled Rectifiers	43
11	Diode Modulation and Detection	49
12	Triode Tube Amplifiers: Gain and Linearity as Determined by Bias, Signal, Load, and Tube Type	53
13	The Cathode Follower, a Unit-gain Impedance Transformer	63
14	Transistor Characteristics	67
15	Single-stage Transistor Amplifiers	73
16	The DC Differential Amplifier	77
17	Transistor Power Amplifiers	81
18	The Lock-in Amplifier	85

19	Basic Operational-amplifier Circuits	91
20	Analog-computer Solutions of the Damped Harmonic Oscillator	97
21	Operational-amplifier Applications in Control: The Voltage Regulator	103
22	Analog Multiplication	107
23	The Phase-shift Oscillator	113
24	Tuned-circuit Oscillators	117
25	Tunnel-diode Relaxation Oscillator	121
26	Binary Building Blocks; Multivibrators: Bistable, Astable, Monostable	129
27	Binary Numbers; The Binary Counter or Scaler	135
28	Gates	145
29	Flip-flops	151
30	The Logical Design of Gating Networks Using Boolean Algebra	161
31	Digital Measuring Instruments: The Frequency Counter and Digital Voltmeter	169
32	Transmission Lines	177