

# Contents

Preface	vii
<b>1 Transistor Basics</b>	<b>1</b>
1-1. The basic semiconductor	1
1-2. The basic crystal junction (or diode)	3
1-3. The basic two-junction or bipolar transistor	
1-4. Field effect transistors	8
1-5. Unijunction transistors	10
1-6. Basic physical characteristics of transistors	10
1-7. Transistor temperature relationships	13
1-8. Transistor parameter data	21
<b>2 Two-Junction (Bipolar) Transistors</b>	<b>32</b>
2-1. Basic two-junction transistor types	33
2-2. Basic two-junction transistor circuit connections	39
2-3. The basic two-junction amplifier	41
2-4. Rules for labeling, biasing, and polarities in two-junction transistors	42
2-5. Common-emitter amplifier	43
2-6. Common-base amplifier	47
2-7. Common-collector (or emitter-follower) amplifier	

2-8. Using load lines to examine two-junction transistor characteristics	50	
2-9. Two-junction transistor bias networks	51	
2-10. Interpreting two-junction transistor datasheets		63
2-11. Determining two-junction transistor parameters at different frequencies	67	
2-12. Determining two-junction transistor parameters at different temperatures	78	
2-13. Practical two-junction transistor testing		83

### 3 Field Effect Transistors

3-1. Junction field effect transistors (JFET)	99	
3-2. Metal-oxide semiconductor transistors (MOSFET)		102
3-3. Equivalent MOSFET circuit	104	
3-4. FET operating modes	105	
3-5. Practical MOSFETs	107	
3-6. Advantages and disadvantages of FETs		111
3-7. FET operating regions	112	
3-8. Zero-temperature-coefficient point	115	
3-9. Handling MOSFETs	118	
3-10. Protecting MOSFETs	119	
3-11. Triode-connected dual-gate MOSFET		124
3-12. FET characteristics	126	
3-13. Advantages and Limitations of FETs		144
3-14. Temperature coefficient of $I_D$ or $V_{GS}$	149	
3-15. Designing the basic FET stage	150	
3-16. Small-signal analysis of basic FET stage		152
3-17. Test FETs	157	

### 4 Unijunction Transistors

4-1. Operating theory of unijunction transistors		178
4-2. Operation of the PUT	182	
4-3. Structure of unijunction transistors	184	
4-4. Characteristics of unijunction transistors		
4-5. Characteristics of PUT	199	
4-6. Comparison of PUT and UJT characteristics		207
4-7. Basic UJT relaxation oscillator	208	
4-8. Unijunction trigger circuits for gated thyristors		223
4-9. Typical PUT circuits	230	
4-10. Testing unijunction transistors	235	

## 5 Audio-Frequency Considerations for Transistors

- 5-1. How transistor amplifier characteristics affect  
frequency 245
- 5-2. Transistor amplifier coupling techniques 250
- 5-3. Transistor amplifier classifications based on  
operating point 255
- 5-4. UJT regenerative amplifier 260
- 5-5. Basic two-junction transistor amplifier stage 261
- 5-6. Basic FET amplifier stage 265

## 6 Radio-Frequency Considerations for Transistors

- 6-1. Resonant circuits for *RF* amplifiers 271
- 6-2. Basic *RF* amplifier design approaches 276

Index

293