

contents

1 the ideal diode 1

1-1 The ideal diode 1

2 the solid-state junction diode 7

- 2-1 The junction diode 7
- 2-2 Intrinsic conduction 7
- 2-3 Doped semiconductors 8
- 2-4 The *PN* junction 10
- 2-5 Forward bias 12
- 2-6 Reverse bias 13
- 2-7 Barrier capacitance 14
- 2-8 Diffusion capacitance 15

3 diode equivalent circuits 27

3-1 Diode piecewise models 27

4 diode circuit analysis 35

- 4-1 Single-diode circuits 35
- 4-2 Assumed-state analysis 36
- 4-3 Breakpoint analysis 37

5 the junction transistor (transistor action) 53

- 5-1 The controlled current source 53
- 5-2 The junction transistor 54
- 5-3 Transistor current components 55

6 the common-base model 63

- 6-1 The common-base dc model 63
- 6-2 The common-base piecewise model 64

7 the common-emitter model 77

- 7-1 The common-emitter model 77
- 7-1 Piecewise development 78

8 biasing and stabilization 89

8-1 Constant base-current bias 89

- 8-2 Constant emitter-current bias 90
- 8-3 Combination bias 91
- 8-4 Constant collector-voltage biasing 92

9 transistor incremental models 109

- 9-1 The common-base T parameter model 110
- 9-2 The common-emitter T parameter model 110
- 9-3 The h parameters 111
- 9-4 The common-base h parameters 113
- 9-5 The common-emitter h parameters 113

10 transistor high-frequency models 121

- 10-1 The hybrid- π model 121
- 10-2 The Miller effect 122

11 basic transistor amplifiers 129

- 11-1 The common-base amplifier 130
- 11-2 The common-emitter amplifier 131
- 11-3 The emitter-follower amplifier 132
- 11-4 Summary of basic amplifier characteristics 134

12 the field-effect transistor (FET) 147

- 12-1 FET types 147
- 12-2 JFET operation 149
- 12-3 IGFET operation 153

13 FET models 161

- 13-1 FET large-signal models 161
- 13-2 FET small-signal models 166

FET biasing 179

- 14-1 JFET biasing 179
- 14-2 Fixed bias 180
- 14-3 Current-derived self-bias 181
- 14-4 Constant-current bias 184
- 14-5 Zero-temperature-coefficient biasing 185
- 14-6 Miscellaneous biasing methods 186
- 14-7 IGFET biasing 188
- 14-8 The Ohmic region
(voltage-controlled resistor) 191

15 basic FET amplifiers 209

- 15-1 Incremental model review 209
- 15-2 The common-source amplifier 210

- 15-3 The common-drain amplifier
(source follower) 212
- 15-4 The common-gate amplifier 213
- 15-5 High-frequency considerations 214

appendices

A current notation 227

B voltage notation 229

index 231

