

# CONTENTS

- 
- 1** **What Is a Semiconductor?** . . . . . 11  
Current flow in semiconductors—Transistor types and functions  
—Three basic transistor circuits and their signal characteristics  
—Basic transistor circuits combined.
- 
- 2** **Semiconductor Characteristics** . . . . . 17  
Relative size of transistor currents — Self-biasing transistor  
circuits — The effect of temperature — Transistor bias  
stabilization.
- 
- 3** **Determining Semiconductor Characteristics** 24  
Transistor emitter current gain—Base current gain—Voltage  
drops within a circuit—Drawing a transistor circuit's load line  
—Determining a transistor's base current from a load line—  
Changing a transistor circuit's load line — Determining a  
transistor's base voltage—Calculating bias circuits—Transistor  
standardization.
- 
- 4** **Frequency Limitations** . . . . . 35  
Two factors limiting high-frequency response — Causes of  
transistor oscillation at high frequencies—Factors limiting low-  
frequency response—Negative feedback circuits.

<b>5</b>	<b>Field-Effect Transistors</b> . . . . .	<b>44</b>
	Controlling drain current—Biasing the gate—FET pinch-off voltages—Junction FET amplification—Determining an FET circuit's load line—FET frequency response—The effect of temperature on FETs—Junction FET standardization.	
<hr/>		
<b>6</b>	<b>MOS FETs</b> . . . . .	
	Composition of a depletion-type MOS transistor—MOS gate resistances — Depletion-type MOS characteristic curves — A depletion-type MOS common-source circuit—Composition of enhancement-type MOS transistors—Enhancement-type MOS characteristic curves — Enhancement-type MOS common-source circuits—General MOS characteristics.	
<hr/>		
<b>7</b>	<b>The Tunnel Diode</b> . . . . .	
	Tunnel-diode characteristic curves—A simplified tunnel-diode amplifier circuit—Tunnel-diode amplifier output resistance—Tunnel-diode amplifier voltage gain—Tunnel-diode amplifier power gain.	
<hr/>		
<b>8</b>	<b>Tunnel-Diode Applications</b> . . . . .	<b>71</b>
	The tunnel-diode amplifier's input resistance—More tunnel-diode amplifier circuits—Tunnel-diode oscillator circuits—Tunnel-diode switches — Summary of tunnel-diode circuit characteristics.	
<hr/>		
<b>9</b>	<b>Integrated Circuits</b> . . . . .	<b>81</b>
	A variable-current-source amplifier—A constant-current-source amplifier—An unbalanced differential amplifier.	
<hr/>		
<b>10</b>	<b>IC Differential Amplifiers</b> . . . . .	<b>91</b>
	A balanced differential amplifier circuit — The CA3005 integrated circuit.	

## **11** IC Applications in FM Circuits

An IC FM IF strip—A cascode amplifier.

---

## **12** IC Applications in TV . . . . . 12

The IC201 integrated circuit—IC series differential amplifiers  
—IC voltage-regulating transistors.

---

## **13** IC TV Sound Circuits . . . . .

IC negative feedback circuits—Discriminator circuits.

---

## **14** IC Time Constants & Cascade Amplifiers

Capacitor time constants—IC cascade amplifiers.

---

## **15** The Varicap . . . . .

General capacitor characteristics—Diode capacitors—Voltage-current phase angles—Coil impedances.

---

## **16** Varicap Applications . . . . .

Original "varicap" circuits — Series resonant circuits  
Parallel resonant circuits—"Varicap" tuning circuits.

---

## **17** Review of Capacitor & Coil Impedances . . 165

Resonant circuit  $Q$  factors—Tuning receivers—Superheterodyne circuits—FM AFC circuits—TV AFC circuits—AM receiver varicap tuning.

**18** Photo-Sensitive and Photo-Emissive Devices . 180  
Photovoltaic cells — Photoconductive cells — Photodiodes  
—Phototransistors.

---

**19** FET Light-Sensitive Devices . . . . . 188  
PhotoFET transistors—PhotoMOS transistors—Light-emitting  
diodes.

---

**20** Principles of Optics . . . . .  
Basic principles of optic lenses—Basic principles of fiber  
optics.

---

**21** Optic-Electronic Couplers . . . . .  
Incandescent couplers — Luminescent couplers — Contactless  
meter relays—Needleless phono pickup for standard records.

---

**22** Semiconductors for Power Supplies . . . . .  
Unijunction transistor characteristics — Field-effect diodes —  
Zener diodes—Complex diodes—Temperature-compensating  
diodes and thyrectors.

---

**23** More Semiconductors for Power Supplies . . . 230  
Four-layer diode characteristics—SCR diodes—Diacs—Triacs.

---

**24** Constant-Voltage Transformer . . . . . 237  
AC voltage regulation—AC current regulation.

**25** Power Conversion . . . . . 247  
DC-to-AC conversion—AC-to-DC conversion—AC-to-varied  
DC conversion — AC-to-regulated DC conversion — Voltage  
multiplier circuits.

---

**26** Filter & Regulators . . . . . 258  
Filter circuits—DC voltage regulating circuits—DC current  
regulating circuits.

---

Index . . . . . 267