

# CONTENTS

**PREFACE** **xi**

chapter one

**BASIC DESIGN RULES** **1**

- 1-1. *How to use this book* 1
- 1-2. *Interpreting datasheets* 3
- 1-3. *Determining parameters at different frequencies* 7
- 1-4. *Temperature-related design problems* 12
- 1-5. *Using load lines in simplified design* 21
- 1-6. *Basic bias schemes* 23
- 1-7. *Practical design techniques* 34
- 1-8. *Practical transistor mounting techniques* 45

chapter two

**AUDIO AMPLIFIERS** **53**

- 2-1. *Basic audio amplifiers* 53
- 2-2. *Basic audio amplifier with emitter bypass* 58
- 2-3. *Basic audio amplifier with partially bypassed emitter* 59
- 2-4. *Direct coupled voltage amplifier* 61
- 2-5. *Transformerless multistage audio amplifiers* 64
- 2-6. *Examples of transformerless direct-coupled audio amplifiers* 74

- 2-7. *Complementary power amplifiers with short-circuit protection* 83
- 2-8. *Multistage audio amplifier with transformer coupling* 97
- 2-9. *Operating and adjustment controls* 110
- 2-10. *Audio filters* 117
- 2-11. *Audio circuit test procedures* 122
- 2-12. *Frequency response of audio circuits* 122
- 2-13. *Analyzing design problems with test results* 133

chapter three

## **OPERATIONAL AMPLIFIERS WITH INTEGRATED CIRCUITS**

- 3-1. *Basic IC operational amplifier* 138
- 3-2. *Design considerations for frequency response and gain* 148
- 3-3. *Interpreting IC data sheets* 169
- 3-4. *Integrated-circuit operational amplifier* 190
- 3-5. *Integrated-circuit summing amplifier* 194
- 3-6. *Integrated-circuit integration amplifier* 195
- 3-7. *Integrated-circuit differentiation amplifier* 199
- 3-8. *Integrated-circuit narrow bandpass amplifier* 201
- 3-9. *Integrated-circuit wide bandpass amplifier* 202
- 3-10. *Integrated-circuit unity gain amplifier* 204
- 3-11. *Unity gain with fast response* 205
- 3-12. *Integrated-circuit high input impedance amplifier* 208
- 3-13. *Integrated-circuit difference amplifier* 209
- 3-14. *Integrated-circuit voltage-to-current converter* 211
- 3-15. *Integrated-circuit voltage-to-voltage amplifier* 212
- 3-16. *Integrated-circuit low-frequency sine-wave generator* 214
- 3-17. *Operational amplifier test procedures* 216

chapter four

## **RADIO-FREQUENCY CIRCUITS**

- 4-1. *Resonant circuits* 227
- 4-2. *Basic RF amplifier design approaches* 232
- 4-3. *Power amplifiers and multipliers* 247
- 4-4. *Using datasheet graphs to design RF amplifier networks* 257
- 4-5. *Using sampled  $y$ -parameter techniques to design RF networks* 281
- 4-6. *Voltage amplifiers* 290
- 4-7. *Frequency mixers and converters* 295
- 4-8. *Detectors* 299

- 4-9. *Discriminator and ratio detector* 301
- 4-10. *AVC-AGC circuit* 305
- 4-11. *Radio-frequency circuit test procedures* 308

chapter five

## **WAVEFORMING AND WAVESHAPING CIRCUITS 323**

- 5-1. *Basic design considerations for oscillators* 323
- 5-2. *LC and crystal-controlled oscillators* 324
- 5-3. *RC oscillator* 338
- 5-4. *Twin-T RC oscillator* 341
- 5-5. *Blocking oscillator* 343
- 5-6. *Multivibrator* 349
- 5-7. *Modification of square waves* 353
- 5-8. *Modification of sine waves* 357
- 5-9. *Waveforming and waveshaping test procedures*

chapter six

## **POWER-SUPPLY CIRCUITS 367**

- 6-1. *Basic solid-state power supply* 367
- 6-2. *Zener diode regulation* 370
- 6-3. *Extending Zener voltage range* 373
- 6-4. *Extending Zener current range* 375
- 6-5. *Overload protection* 378
- 6-6. *Feedback regulator* 381
- 6-7. *Feedback regulator for input voltage variations*
- 6-8. *Switching regulator* 386
- 6-9. *DC-DC converter* 400
- 6-10. *Power-supply circuit test procedures* 409

## **INDEX**

**421**