

Table of Contents



1.0 Introduction

1.1	Scope of Handbook	1-1
1.2	IC Parameters Applied to Audio	1-1

2.0 Preamplifiers

2.1	Feedback — To Invert or Non-Invert	2-1
2.2	Design Tips on Layout, Ground Loops and Supply Bypassing	2-1
2.3	Noise	2-3
2.4	Audio Rectification — or, "How Come My Phono Detects AM?"	2-11
2.5	Dual Preamplifier Selection	2-12
2.6	LM381	2-13
2.7	LM381A	2-16
2.8	LM387 or LM387A	2-17
2.9	LM382	2-18
2.10	LM1303	2-22
2.11	Phono Preamps and RIAA Equalization	2-23
2.12	Tape Preamps and NAB Equalization	2-28
2.13	Mic Preamps	2-43
2.14	Tone Controls — Passive and Active	2-46
2.15	Scratch, Rumble and Speech Filters	2-55
2.16	Bandpass Active Filters	2-58
2.17	Octave Equalizers	2-59
2.18	Mixers	2-65
2.19	Driving Low Impedance Lines	2-67
2.20	Noiseless Audio Switching	2-68

3.0 AM, FM and FM Stereo

3.1	AM Radio	3-1
3.2	LM3820	3-4
3.3	FM-IF Amplifiers/Detectors	3-7
3.4	LM3089 — Today's Most Popular FM-IF System	3-8
3.5	LM3189	3-13
3.6	FM Stereo Multiplex — LM1310/1800	3-14
3.7	Stereo Blend — LM4500A/LM1870	3-18

4.0 Power Amplifiers

4.1	Inside Power Integrated Circuits	4-1
4.2	Design Tips on Layout, Ground Loops and Supply Bypassing	4-5
4.3	Power Amplifier Selection	4-5
4.4	LM1877/378/379/1896/2887/2896	4-7
4.5	LM380	4-22
4.6	LM384	4-29
4.7	LM386	4-31
4.8	LM389	4-36
4.9	LM388	4-41
4.10	LM390	4-45
4.11	LM383	4-46
4.12	Power Dissipation	4-48
4.13	Boosted Power Amps /LM391/LM2000	4-50
4.14	Heatsinking	4-64

Table of Contents

(continued)



5.0 Floobydust*

5.1	Bi-amplification 5-
5.2	Active Crossover Networks 5-
5.3	Reverb 5-
5.4	Phase Shifter 5-11
5.5	Fuzz 5-1
5.6	Tremolo 5-1
5.7	Acoustic Pickup Preamp 5-1;
5.8	Non-Complementary Noise Reduction 5-1;

6.0 Appendices

A1	Power Supply Design 6-1
A2	Decibel Conversion 6-11
A3	Wye-Delta Transformation 6-11
A4	Standard Building Block Circuits 6-12
A5	Magnetic Phono Cartridge Noise Analysis 6-13
A6	General Purpose Op Amps Useful for Audio 6-16
A7	Feedback Resistors and Amplifier Noise 6-17
A8	Reliability 6-18
A9	Audio-Radio Glossary 6-19

7.0 Index

*“Floobydust” is a contemporary term derived from the archaic Latin *miscellaneus*, whose disputed history probably springs from Greek origins (influenced, of course, by Egyptian linguists) — meaning here “a mixed bag.”

Device Index

LM378 4-7	LM1310 3-14
LM379 4-7	LM1800 3-14
LM380 4-22	LM1818 2-37
LM381 2-13	LM1870 3-20
LM381A 2-16	LM1877 4-7
LM382 2-16	LM1896 4-7
LM383 4-46	LM2000 4-62
LM384 4-26	LM2001 4-62
LM386 4-31	LM2887 4-7
LM387 2-17	LM2896 4-7
LM387A 2-17	LM3089 3-8
LM388 4-41	LM3189 3-13
LM389 4-36	LM3820 3-4
LM390 4-46	LM4500A 3-19
LM391 4-52	MM5837 2-62
LM1011 2-42	LM13600 5-13
LM1303 2-22		