

CONTENTS

Preface, v

CHAPTER 1 VOLT-AMPERE CHARACTERISTICS

- 1-1 Current, 1
- 1-2 The Volt-Ampere Characteristic of a Linear Device, 2
- 1-3 The Volt-Ampere Characteristic of a Nonlinear Device, 5
- 1-4 Determining the Static and Dynamic Resistances of a Nonlinear Device, 6
- 1-5 The Load Line, 8

CHAPTER 2 THE p - n JUNCTION DIODE 16

- 2-1 The Atom and Free Electrons, 16
- 2-2 Crystalline Structures and Covalent Bonds, 17
- 2-3 Electron-Hole Pairs, 18
- 2-4 Impurity Doping, 19
- 2-5 The p - n Junction, 21
- 2-6 Diode Action, 23
- 2-7 Reverse Current, 24
- 2-8 The p - n Diode Characteristic, 25

CHAPTER 3 THE TRANSISTOR 32

- 3-1 Relative Doping and the Depletion Region, 32
- 3-2 The Junction Transistor, 33
- 3-3 Transistor Currents, 34
- 3-4 The Relationship between α and β , 37
- 3-5 The Common-Emitter Configuration, 40
- 3-6 The Common-Emitter Output Characteristics, 42
- 3-7 Transistor Parameters, 45
- 3-8 The Common-Emitter Input Characteristics, 47

	3-9	Temperature Effects, 49	
	3-10	Beta Spread, 50	
	3-11	dc Analysis of the Common-Emitter Configuration, 51	
	3-12	Transistor Ratings, 57	
CHAPTER	4	THE ELEMENTARY TRANSISTOR AMPLIFIER	61
	4-1	Analysis of a Single-Stage Amplifier, 61	
	4-2	Waveforms, 64	
	4-3	Gain, 65	
	4-4	The Function of the Batteries, 70	
	4-5	Current Source, 75	
	4-6	The Small Signal ac Equivalent Circuit: Approximate Model, 78	
	4-7	The Small Signal ac Equivalent Circuit: Exact Model, 82	
	4-8	Applications of the Equivalent Circuit, 88	
CHAPTER	5	dc BIAS CIRCUITS AND STABILITY	99
	5-1	Fixed Bias, 99	
	5-2	Instability of the Q Point, 105	
	5-3	Collector-to-Base Bias, 116	
	5-4	Analysis of the Collector-to-Base Bias Circuit, 121	
	5-5	Thevenin's Theorem, 130	
	5-6	Emitter Bias, 132	
	5-7	Stability Factor, 143	
CHAPTER	6	AMPLIFIERS IN CASCADE	159
	6-1	Capacitor Coupling, 159	
	6-2	ac Analysis of the Capacitor-Coupled Amplifier, 169	
	6-3	The Cascade Connection, 174	
	6-4	Design Factors, 186	
	6-5	Gain of the Cascaded Amplifier, 195	
	6-6	Limitations on Cascading, 198	
	6-7	Direct Coupling the Emitter Bias Circuit, 204	
	6-8	Emitter Bias Circuit: Input Resistance, 206	
	6-9	Emitter Bias Circuit: Output Resistance, 209	
	6-10	Analysis of the Emitter-Biased Amplifier, 212	
	6-11	General Gain Equation, 220	
	6-12	ac Analysis of the Collector-to-Base Bias Circuit, 223	
CHAPTER	7	FEEDBACK AMPLIFIERS	234
	7-1	Relationship between β and r_{11} , 235	
	7-2	Effect of β Variation on Amplifier Gain, 237	
	7-3	Negative ac Feedback: Emitter Bias, 240	
	7-4	General Feedback Theory, 243	
	7-5	Negative ac Feedback: Collector-to-Base Bias, 248	

7-6	Over-All Feedback, 250	
7-7	Maximum Power Transfer, 259	
7-8	Impedance Matching, 263	
7-9	The Emitter-Follower Amplifier, 269	
7-10	The Emitter-Follower as an Impedance Matcher, 273	
7-11	The Emitter-Follower as a Buffer, 279	
CHAPTER 8	FREQUENCY RESPONSE	286
8-1	The Concept of Frequency Response, 286	
8-2	The Decibel, 290	
8-3	The Frequency Plot, 294	
8-4	Low-Frequency Response: Coupling Capacitor, 301	
8-5	Low-Frequency Response: By-Pass Capacitor, 306	
8-6	High-Frequency Response, 311	
8-7	Frequency Response of Multi-Stage Amplifiers, 323	
CHAPTER 9	POWER AMPLIFIERS	328
9-1	Maximum Output Power, 328	
9-2	The Single-Ended Class A Power Amplifier, 333	
9-3	Amplitude Distortion, 343	
9-4	Class A Push-Pull Amplifier, 347	
CHAPTER 10	AMPLIFIER DESIGN	351
10-1	Systems, 352	
10-2	The Statement of the Design Problem, 353	
10-3	Determination of the Circuit Configuration, 354	
10-4	Selection of the Transistor Type: The Specification Sheet, 358	
10-5	The Design of Stage 1, 366	
10-6	The Design of Stage 2, 373	
10-7	The Design of the Follower Stage, 376	
10-8	The Design of the Feedback Loop, 379	
10-9	The Selection of the Resistor Power Ratings, 382	
10-10	The Selection of the Capacitors, 385	
10-11	Troubleshooting the Circuit, 390	
	Index, 399	