

# CONTENTS

---

<b>Preface</b>	<b>iii</b>
<b>List of Symbols</b>	<b>xiii</b>
<b>1 Problems of Circuit Design and Applications</b>	<b>1</b>
The circuit relations problem, 2; The temperature problem, 3; The transistor variability problem, 3; Transistor circuit analysis, 4; Design, 6.	
<b>2 Static Characteristics and Transistor Parameters</b>	<b>8</b>
Transistors as coupled diodes, 8; Transistor static characteristics, 9; The CB $Q$ -point parameters and the static input characteristics, 11; CB static collector characteristics, 13; CE static input characteristics, 14; CE static collector characteristics, 15; CC input-out characteristics, 18; Current transfer and transconductance curves, 18; Symmetrical transistors and inverse alpha, 19; Summary, 19.	
<b>3 The Emitter Diode and Shockley's Relation</b>	<b>21</b>
Semiconductor diode theory, 21; Shockley's relation derived, 25; Implications of Shockley's relation, 26; Silicon transistors—the exceptions, 28; Summary, 29.	
<b>4 Equivalent Circuits, Gain and Impedance Formulas</b>	<b>31</b>
The CB $T$ -equivalent, 31; The CE $T$ -equivalent, 34; The hybrid CB equivalent, 35; The short-circuited $T$ -equivalent, 35; Gain and impedance relations of the CB amplifier, 37; Gain and impedance relations of the CE amplifier, 38; Gain and impedance relations of the CC amplifier, 39; The CE amplifier with external resistors, 41; CE amplifier gain dependence on $R_g$ and $R_E$ , 42; The internal output resistance of the CB and CE amplifiers, 44; The transistor gain-impedance relation, 45; Summary, 47.	
<b>5 Temperature Problems</b>	<b>49</b>
Diode saturation currents, 49; $I_{CBO}$ effects in practical transistors, 51; The $I_{CO}$ equivalent generator, 52; The temperature dependence of $V_{BE}$ , 55; Temperature variation of transistor parameters, 56; Transistor selection for low $I_{CO}$ or high temperature operation, 59; Summary, 60.	

<b>6 Bias and Temperature Instability</b>	<b>61</b>
Transistor biasing and bias temperature problems, 62; Emitter feedback biasing for $I_{CO}$ control, and the S-factor, 62; Emitter feedback biasing: an example, 65; Collector feedback biasing, 69; Collector feedback bias with a Zener diode, 72; Feedback biasing to reduce $V_{BE}$ temperature shift, 72; Feedback biasing and beta changes, 73; Q-point shift with $V_{BE}$ and beta, 74; Summary, 75.	
<b>7 Common-Base Amplifiers</b>	<b>77</b>
CB amplifier characteristics, 77; CB amplifier circuit: an example, 78; The gain-impedance relation with transformers, 79; Temperature effects, 79; Summary, 80.	
<b>8 Common-Emitter Amplifiers</b>	<b>81</b>
CE amplifier characteristics, 81; CE amplifier circuit: an example, 83; Summary, 86.	
<b>9 Common-Collector Amplifiers</b>	<b>87</b>
CC amplifier characteristics, 87; CC amplifier circuits: examples, 88; The CC filter (or impedance reducer), 91; Summary, 93.	
<b>10 Direct-Coupled Pairs</b>	<b>94</b>
Voltage-gain relations, 95; Voltage gain and limited supply voltage, 98; Voltage gain and the emitter currents, 98; The choice between npn or pnp transistors, 100; A direct-coupled pair: an example, 101; The CC-CC or Darlington compound, 104; CC-CC high input impedance amplifiers, 107; Transistor compounds, 109; Parallel-connected and complementary-symmetry compounds, 112; Summary, 113.	
<b>11 Feedback Amplifiers</b>	<b>116</b>
Feedback, 117; Series-current feedback, 118; Loop feedback, 121; Shunt-voltage feedback, 123; Miller feedback, 125; Black-equivalent or series-voltage feedback, 126; Positive feedback, 128; Miller feedback: an example, 129; Shunt feedback to control gain, 130; Black feedback: an example, 131; Double feedback: an example, 132; Amplifier S-factors, 134; Feedback loop stabilization, 134; Summary, 135.	
<b>12 Direct-Coupled Amplifiers</b>	<b>138</b>
Single-sided dc amplifiers, 139; A practical single-sided amplifier, 142; High-impedance dc amplifiers, 143; Drift, 145; The drift equations, 146; The $V_{BE}$ drift, 147; The $I_{CO}$ drift, 148; The alpha drift, 148; The drift of later stages, and residual drifts, 149; Related design problems, 150; Dc chopper amplifiers, 151; Differential dc amplifiers: an example, 152; Summary, 154.	

<b>13 Noise in Transistor Amplifiers</b>	<b>156</b>
Noise, 156; Resistance noise, 156; Shot noise, 158; Excess (or $1/f$ ) noise, 158; High-frequency (or cutoff) noise, 159; Signal-to-noise ratio, 159; Noise factor, 160; Spot noise, 161; Wide-band (or average noise) factors, 161; Transistor noise, 163; Transistor noise representations, 165; Transistor noise calculations, 167; Summary, 168.	
<b>14 The Ebers and Moll Large-Signal Relations</b>	<b>171</b>
The Ebers and Moll relations, 171; Large-signal relations in the cutoff region, 174; Large-signal relations in the active region, 175; Large-signal relations in the saturated ON region, 177; Summary, 179.	
<b>15 Linear Power Amplifiers</b>	<b>181</b>
Power amplifier principles, 182; Single-sided power amplifiers, 182; Power amplifiers for higher frequencies, 184; Class-A power amplifier design, 185; Push-pull Class-B amplifiers, 186; Complementary-symmetry amplifiers, 189; Quasi-complementary-symmetry amplifiers, 191; Driver-stage requirements, 193; Power transistor ratings, 193; Control of $I_{CO}$ effects in power amplifiers, 195; Power-supply requirements, 196; Summary, 197.	
<b>16 The Dissipation of Heat and Thermal Runaway</b>	<b>199</b>
Power dissipation and heat transfer, 199; Thermal resistance calculation, 201; Thermal resistance of solid conductors, 201; Thermal resistance of transistors, 202; Free convection cooling, 204; Forced air and liquid cooling, 205; Thermal runaway, 206; Runaway and heat sinks: an example, 210; Prevention of runaway damage, 212; Thermal capacity and pulse power ratings, 213; Summary 215.	
<b>17 Power Switching Amplifiers and Inverters</b>	<b>217</b>
Large-signal characteristics, 219; Base drive requirements, 221; Base input curves and an equivalent circuit, 222; Base driver transformers, 224; Output transformers, 227; Switching transformer construction, 228; Voltage and current waveforms, 228; Operating frequency and switching power loss, 231; Load diagrams, 232; Switching amplifier performance, 233; Transistor inverters, 234.	
<b>18 Medium-Frequency Amplifiers</b>	<b>238</b>
The hybrid pi-equivalent circuit, 239; The current-gain-bandwidth product, 240; The Miller effect in transistors, 241; Input impedance and series feedback, 243; Series feedback and beta cutoff, 243; Shunt feedback and beta cutoff, 244; Tuned amplifiers and stability problems, 246; Wide-band single-stage amplifier. 247: Summary. 249.	

## CONTENTS

### **19 Tetrode Transistors**

Tetrode biasing, 251; High-frequency tetrodes, 252; Automatic gain-control tetrodes, 253; Power tetrodes, 253; Summary, 255.

### **20 The Field-Effect Transistor**

257

Static characteristics, 257; Dynamic characteristics, 260; An equivalent circuit, 262; Frequency effects, 263; Temperature characteristics, 264; Noise characteristics, 265; FET applications, 267; FET-transistor compounds, 268; FET-amplifier examples, 269; Automatic gain-control amplifier, 273; FET choppers, 274; Summary, 274.

### **21 Insulated-Gate Field-Effect Transistors (MOS)**

Principal characteristics, 277; Static characteristics, 278; Temperature characteristics, 279; Dynamic characteristics, 280; Noise characteristics, 280; Applications, 281; MOS biasing and single-stage amplifiers, 281; Multistage resistance-coupled amplifiers, 283; High-input-impedance, wide-band amplifier, 284; MOS time-delay relay circuit, 285; Summary, 286.

### **Appendices**

- I (A) Characteristics of a Silicon Planar Transistor; NPN Amplifier and Switching Type 2N1613
- (B) Typical Characteristic Curves of Transistor Type 2N1613 288
- II Low-Frequency Transistor Approximations 290
- III Hybrid T-Equivalent Conversions 291
- IV (A) Transistor Gain and Impedance Formulas
- (B) Current Gains and Voltage Gains Versus Load Resistance
- (C) Power Gains Versus Load Resistance
- (D) Input Resistance Versus Load Resistance
- (E) Output Resistance Versus Generator Resistance 292
- V Shea's Gain and Stability Factor Relations
- VI (A) Collector Cutoff Current Versus Temperature
- (B) Thermal Resistance Formulas
- (C) Thermal Resistances, Resistivities, and Thermal Capacities

- (D) Thermal Resistance of Heat Sinks
- (E) Temperature Conversion
- VII (A) Typical Low-Power Transistors
- (B) Typical Power Transistors
- VIII Resistance Noise Chart
- IX Alpha-Beta Table
- X Reactance Chart

**Index****305**