

CONTENTS

Members of the Consultative Committee	page xi
Foreword by O.W. Humphries, C.B.E.	xii
Editor's Preface	1

1. POWER SUPPLIES

1. 1. Low-voltage D.C. Supplies

1. 1. 1. Non-controllable D.C. Low-voltage Power Supply Using Semiconductor Diodes	2
1. 1. 2. Controllable D.C. Power Supply Using Thyristors	4

1. 2. High-voltage D.C. Supplies

1. 2. 1. Variable Heavy-duty D.C. Power Supply Using Thyratrons	8
1. 2. 2. Unstabilized D.C. Supply with Focus and Brilliance Controls for a Cathode Ray Oscillograph Tube	10

1. 3. Transistor Convertors

1. 3. 1. A Low-Power D.C. Convertor Using Transistors	12
---	----

1. 4. Stabilizers

1. 4. 1. D.C. Degenerative Stabilizer Using a Cascode-amplifier Shunt Circuit	14
--	----

2. WAVEFORM GENERATORS

2. 1. Sinusoidal Generators

2. 1. 1. Crystal Oscillators Using Valves	16
2. 1. 2. Franklin Oscillator	23
2. 1. 3. Variable-frequency Wien-bridge Oscillator Using Valves	24
2. 1. 4. 1000 c/s Bridge Source Oscillator Using Transistors	26
2. 1. 5. General Purpose Wide-range R.F. Oscillator	28

2. 2. Sawtooth Generators

2. 2. 1. General-purpose C.R.T. Sweep Circuit	30
2. 2. 2. Linear Current Sweep Generator	32

2. 3. Pulse Generators

- 2. 3. 1. Transistor Blocking Oscillator for Digital Circuits
- 2. 3. 2. Triggered Blocking Oscillator Using Transistors for Large Current Pulse Amplitudes

2. 4. Multivibrators

- 2. 4. 1. Transistor Multivibrators

2. 5. Monostable Trigger Circuits (Flip-flops)

- 2. 5. 1. Monostable Trigger Circuit (Flip-flop) Using Transistors
- 2. 5. 2. General Purpose Monostable Trigger Circuit (Flip-flop) Using Valves

2. 6. Bistable Trigger Circuits (Toggles)

- 2. 6. 1. Bistable Trigger Circuit (Toggle) Using Transistors
- 2. 6. 2. Bistable Trigger Circuit (Toggle) for High-frequency Operation Using Transistors
- 2. 6. 3. A Bistable Trigger Circuit (Toggle) Using a P-N-P and an N-P-N Transistor

2. 7. Step Waveform Generators

- 2. 7. 1. Step Waveform Generator Using Transistors

3. AMPLIFIERS**3. 1. Special Amplifiers**

- 3. 1. 1. Electrometer Amplifier

3. 2. Audio-frequency Amplifiers

- 3. 2. 1. Music-frequency Amplifier Using Transistors
- 3. 2. 2. High-sensitivity General Purpose A.F. Amplifier Using Valves

3. 3. Radio-frequency Amplifiers

- 3. 3. 1. R.F. Voltage Amplifier Using a Valve
- 3. 3. 2. High-gain Broad-band Amplifier Using Transistors

3. 4. Video Frequency Amplifiers

- 3. 4. 1. Wide-band Voltage Amplifier with Differential Input, Using Valves

3. 4. Video Frequency Amplifiers (continued)

3. 4. 2. Wide-band Amplifier with Asymmetrical Input Using Valves	page 69
3. 4. 3. Wide-band Amplifiers with Negative Feedback Using Valves or Transistors	70
3. 5. Automatic Gain Control	
3. 5. 1. Automatic Gain Control Circuit for Oscillator Level Control	75
3. 6. Differential Amplifiers	
3. 6. 1. Differential Valve Amplifiers of High Rejection Ratio	76
3. 7. Cathode-follower Circuits	
3. 7. 1. General-purpose Isolating Cathode-follower Using a Valve	78
3. 7. 2. Cable-driving Cathode-follower	80
3. 7. 3. Cathode-follower for Fast Negative-going Signals	82

4. FREQUENCY CONVERTORS

4. 1. Frequency Adders

4. 1. 1. Frequency Adding Circuit Using Valves	84
--	----

4. 2. Frequency Multipliers

4. 2. 1. Frequency Multiplier Using a Valve	86
4. 2. 2. Frequency Doubler Using a Valve	88

4. 3. Frequency Dividers

4. 3. 1. High-speed Frequency Divider Using a Trochotron	90
4. 3. 2. Medium-speed Frequency Divider Using a Dekatron	92
4. 3. 3. Low-speed Frequency Divider Using Cold-cathode Trigger Tubes	96

5. COUNTERS

5. 1. Unidirectional Counters

5. 1. 1. Counter Circuits Using Transistors	98
5. 1. 2. Ring Counter Using Transistors and Ferrite Cores	104
5. 1. 3. Unidirectional Counters Using Dekatron Tubes	106
5. 1. 4. Unidirectional Counter Using a Trochotron Tube with Transistor Drive	110

5. 2. Bi-directional Counters

5. 2. 1. Bi-directional Ring Counter Using Trigger Tubes page 112

5. 2. 2. Bi-directional Counter Using Dekatron Tubes 114

5. 3. Batch Counters

5. 3. 1. Batch Counter Using Dekatrons

6. MODULATORS**6. 1. Amplitude Modulators**

6. 1. 1. Balanced Modulator Using Symmetrical Transistors

6. 2. Frequency Modulators

6. 2. 1. Frequency Modulator Using a Semiconductor Variable Capacitor 123

6. 2. 2. Frequency Modulated Crystal Oscillator Using Valves 124

6. 3. Phase Modulators

6. 3. 1. Low-amplitude-modulation Phase Modulator, Using Valves

6. 4. Pulse Modulators

6. 4. 1. High Power Pulse Modulators Using Hydrogen Thyratrons

7. DEMODULATORS**7. 1. Frequency Demodulators**

7. 1. 1. Fast-acting Phase-sensitive Detector Using Valves 144

7. 1. 2. Phase Sensitive Detector Using Transistors 146

7. 1. 3. Phase Sensitive Modulator/Demodulator Circuit Using Transistors

8. WAVEFORM MODIFIERS**8. 1. Differentiating and Integrating Circuits**

8. 1. 1. General Survey of Differentiating and Integrating Circuits

8. 2. Schmitt Trigger Circuits

8. 2. 1. General Purpose Schmitt Trigger Circuit Using Valves

8. 2. 2. General Purpose Schmitt Trigger Circuit Using Transistors

9. LIMITERS

9. 1. Diode Limiters

9. 1. 1. Diode Limiters Using Thermionic or Semiconductor Diodes page 157

10. CLAMPS

10. 1. D.C. Restoring Circuits

10. 1. 1. Simple D.C. Restoring Circuit and Basic Clamp Circuits
Using Thermionic or Semiconductor Diodes 160

10. 2. Non-error Predicting Circuits

10. 2. 1. Non-feedback Clamp Using Valves 162

10. 3. Error Predicting Circuits

10. 3. 1. Feedback Clamp Using Valves 166

11. REFERENCE CIRCUITS

11. 1. Direct Voltage Reference Circuits

11. 1. 1. Direct Voltage Reference Circuits Using Gas-filled Valves 170

11. 1. 2. Direct Voltage Reference Circuit Using a Semiconductor
Diode 172

11. 2. Alternating Voltage Reference Circuits

11. 2. 1. Alternating Voltage or Current Reference Circuit Using
a Valve 173

12. LOGIC ELEMENTS

12. 1. Logic Elements in Logic-circuits

12. 1. 1. Logic Elements Using Semiconductor Devices 175

12. 1. 2. High Frequency Logic Elements Using Semiconductor
Devices 178

13. INPUT CIRCUITS FOR TRANSDUCERS**13. 1. Amplitude-sensitive Input Circuits**

- | | |
|--|----------|
| 13. 1. 1. Balanced Microphone Input Circuit Using Transistors | page 180 |
| 13. 1. 2. Approximately-balanced High-input Impedance Circuit
Using Transistors | 182 |

14. INTERVAL TIMERS**14. 1. Relay Timing Circuits**

- | | |
|--|-----|
| 14. 1. 1. Relay Timing Circuit Using a Cold Cathode Tube | 183 |
|--|-----|

15. ELECTROMECHANICAL CONTROL CIRCUITS**15. 1. Transistor Relay Circuits**

- | | |
|---|-----|
| 15. 1. 1. Relay Operation from Short-duration Pulses, Using a
Transistor and a D.C. Supply | 186 |
|---|-----|

15. 2. Photocell-operated Relay Circuits

- | | |
|--|-----|
| 15. 2. 1. Relay Operation Using a Photoconductive Cell | 188 |
|--|-----|

15. 3. Schmitt Trigger Relay

- | | |
|--|-----|
| 15. 3. 1. Adjustable Centre Stable Electronic Relay Using Valves | 191 |
|--|-----|

15. 4. Thyatron Control Circuits

- | | |
|--|-----|
| 15. 4. 1. Variable Speed Control for Small Motors Using a Single
Thyatron | 193 |
|--|-----|

- | | |
|--------------|------------|
| Index | 194 |
|--------------|------------|