

CONTENTS

Preface	1
Chapter 1 Introduction; Semiconductors and Configurations Used	3
1. Semiconductors used.....	4
1.1. Diodes	4
1.2. Thyristors	5
2. Presentation and classification of circuit configurations	8
2.1. Diode (commutating) groups	8
2.2. Supply connection – the three types of circuit	10
3. Basic approach	13
3.1. Analysis of a circuit	13
3.2. Assumptions for a general analysis	14
3.3. Summary of contents.....	15
Bibliographic notes	17
Bibliography	17
Chapter 2 Half-wave Diode Rectifiers	19
1. Voltage analysis	22
1.1. Rectified voltage	22
1.2. Pulse number	24
1.3. Voltage across the diodes	24
2. Current analysis	25
2.1. Current in the diodes	25
2.2. Secondary current and power factor.....	25
2.3. Primary current and power factor	26
3. Commutation: voltage drop under normal operating conditions.....	34
3.1. Commutation: voltage drop due to overlap.....	35
3.2. Other voltage drops	40

4.	Short-circuit operation	43
4.1.	Short-circuit current.....	43
4.2.	Short-circuit ratio.....	44
	Bibliographic notes	46
	Bibliography	47
Chapter 3 Diode Bridge Rectifiers.....		51
1.	Rectifiers with star-connected supply.....	51
1.1.	Voltage analysis.....	52
1.2.	Current analysis.....	55
1.3.	Voltage drop during normal operation	57
1.4.	Short-circuit operation	61
1.5.	Notes on supplying a purely inductive load	64
2.	Bridge rectifiers with mesh-connected supply	66
2.1.	Operation – voltage analysis	69
2.2.	Current analysis.....	72
2.3.	Voltage drop during normal operation	76
2.4.	Short-circuit operation	81
2.5.	Example of a rectifier providing a voltage with high pulse number.....	84
	Bibliographic notes	88
	Bibliography	88
Chapter 4 Combinations of Diode Rectifiers.....		91
1.	Series combinations.....	91
1.1.	General remarks	91
1.2.	Examples	91
2.	Parallel combinations	95
2.1.	General paralleling conditions	96
2.2.	The 'double-star' rectifier	98
2.3.	Parallel combinations giving a 12-pulse rectified voltage	105
	Bibliographic notes	109
	Bibliography	109
Chapter 5 Effect of Diode Rectifiers on the Supply System: Circuit Comparison and Selection.....		111
1.	Line current harmonics.....	112
1.1.	Single-phase AC supply	112
1.2.	Three-phase AC supply.....	114
2.	Circuit comparison and selection	117
2.1.	Comparison criteria	117
2.2.	General comments	118
2.3.	Application to circuit selection	119
3.	Notes on disturbances induced in the supply system.....	122
3.1.	Propagation and effects of harmonic currents	122

3.2. Commutation effects	128
Bibliographic notes	133
Bibliography	134
Chapter 6 Notes on the Effects of the Load Characteristics ...	139
1. Supplying an <i>RL</i> load	140
1.1. Rectified current analysis	141
1.2. Correcting the results of the general analysis	145
2. Supplying an <i>RLE</i> load	148
2.1. Discontinuous conduction; direct calculation	150
2.2. Discontinuous conduction; simplified calculation	155
2.3. Continuous conduction; direct calculation	159
2.4. Continuous conduction; first harmonic method	164
Bibliographic notes	166
Bibliography	167
Chapter 7 Half-wave Thyristor Rectifiers ...	169
1. Voltage analysis	170
1.1. Rectified voltage	170
1.2. Voltage across the thyristors	176
2. Analysis of current and power	178
2.1. Current and power factor values	178
2.2. The various powers – representation	179
3. Analysis of voltage drops	182
3.1. Commutation – voltage drop due to inductance	182
3.2. Other voltage drops	185
3.3. Notes on other commutation effects	186
4. Precautions necessary in the inverter mode	189
4.1. Consequences of a total blocking failure	190
4.2. Commutation failures	191
5. Fully controlled rectifier with <i>RL</i> load	195
5.1. The two conduction modes	196
5.2. Characteristics	199
6. Fully controlled rectifier with <i>RLE</i> load	202
6.1. Rectified voltage variation at low output	202
6.2. Rectified current ripple at high output	212
7. Effects of incorporating a free-wheel diode	215
Bibliographic notes	218
Bibliography	219
Chapter 8 Thyristor Bridge Rectifiers ...	223
1. Fully controlled bridges with star-connected supply	223
1.1. Voltage analysis	224
1.2. Current analysis	226
1.3. Analysis of voltage drops	226

1.4. Notes on the duration of the gate control signals	230
2. Half-controlled bridges with star-connected supply	231
2.1. Rectified voltage	231
2.2. Secondary current and power factor.....	237
2.3. Fundamental and harmonic components of the line currents ...	240
2.4. Notes on the asymmetrical single-phase bridge.....	246
2.5. Voltage drops.....	248
2.6. Effects of the load characteristics.....	250
3. Bridges with mesh-connected supply	253
3.1. Fully controlled bridges	254
3.2. Half-controlled bridges.....	256
Bibliographic notes	261
Bibliography	262
Chapter 9 Thyristor Rectifier Combinations.....	265
1. Series combinations.....	265
1.1. Reversible rectifiers with high pulse number	265
1.2. Reversible rectifier combinations employing sequence control	266
1.3. Non-reversible rectifier combinations employing sequence control	272
2. Parallel combinations	276
2.1. 'Double-star' rectifier.....	276
2.2. Other parallel combinations	279
3. Antiparallel combinations with circulating current.....	280
3.1. Practical circuits	282
3.2. Calculation of the circulating current.....	284
3.3. Characteristics	288
3.4. Varying the circulating current.....	290
3.5. Advantages and disadvantages.....	291
4. Antiparallel combinations without circulating current	293
4.1. Dead-band circuits	293
4.2. Change-over logic circuits	299
Bibliographic notes	300
Bibliography	300
Chapter 10 Comparison of Controlled Rectifiers	303
1. General remarks	303
2. Application to single-phase circuits	304
3. Application to three-phase circuits	305
4. Other AC-DC conversion solutions.....	307
Bibliographic notes	308
Bibliography	309
APPENDICES	315
Appendix A: Single-phase half-wave rectifier	315

Appendix B: Controlled rectifier with free-wheel diode	327
Appendix C: Calculation of rectified voltages and expansion in harmonic series	337
Appendix D: Line current harmonics of three-phase rectifiers	347
NOMENCLATURE	355
INDEX	359