

Contents

Preface xiv

Chapter 1 Semiconductors and the p - n Junction Diode 1

- 1-1. Semiconductors 2
- 1-2. Impure Semiconductors 5
- 1-3. Conduction Processes in Semiconductors 7
- 1-4. The p - n Junction 9
- 1-5. The Metal-Semiconductor Junction 14
- 1-6. The Practical p - n Junction Diode 15
- 1-7. p - n Junction Diode Ratings 19
- 1-8. Space-Charge, Transition, or Barrier Capacitance—Depletion Layer Width 20
- 1-9. Diffusion Capacitance—Charge Control 24
- 1-10. Switching the p - n Junction Diode—High-Frequency Effects 27
- 1-11. Light-Emitting Diodes—LED's 29

Problems 30

Bibliography 32

Chapter 2 The Junction Transistor 33

- 2-1. The Bipolar Junction Transistor 33
- 2-2. Current-Voltage Relations in the Junction Transistor 37
- 2-3. Common-Base Characteristics 38
- 2-4. Common-Emitter Characteristics—Active Region—Amplification 40
- 2-5. Common-Emitter Characteristics—Saturation and Cutoff Regions 46
- 2-6. Transfer Characteristics of the Common-Emitter Transistor Configuration 51
- 2-7. Common-Collector Configuration 53

2-8. Switching Speed and High-Frequency Effects in the Junction Transistor 53
2-9. Ratings of Junction Transistors 58
Problems 59
Bibliography 60

Chapter 3 The Field Effect Transistor 62

3-1. The Junction Field Effect Transistor 62
3-2. Metal-Oxide-Semiconductor FET—MOSFET; The Insulated-Gate FET—IGFET 66
3-3. The FET Amplifier—Dynamic Parameters 71
3-4. Saturation and Cutoff Operation of the FET 77
3-5. Switching Speed and High-Frequency Response of the FET 78
3-6. Ratings of FET's 79
Problems 81
Bibliography 83

Chapter 4 Integrated Circuit Fabrication 84

4-1. Planar Fabrication Processes for Transistors and Integrated Circuits 84
4-2. Monolithic Transistors—Isolation Techniques 89
4-3. Monolithic *p-n* Junction Diodes—Schottky Diodes 92
4-4. Monolithic MOSFET's 94
4-5. Monolithic Resistors and Capacitors 95
Problems 98
Bibliography 98

Chapter 5 Graphical Analysis 99

5-1. Rules for Notation 99
5-2. Biasing Procedures for the FET 100
5-3. Thermal Stabilization of the FET's Operating Point 106
5-4. A Direct Coupled FET Amplifier 109
5-5. FET Inverters—Active Loads—Complementary Symmetry 113
5-6. Basic Transistor Bias Circuits 119
5-7. Stability of the Junction Transistor's Operating Point 126
5-8. Operating Point Stabilization Circuits 130
5-9. A Direct Coupled Transistor Amplifier 134
5-10. The Direct Coupled Cascode Amplifier 140
5-11. Generalized Notation 142
5-12. Frequency Dependent Loads 144
5-13. Nonlinear Distortion 149
Problems 155
Bibliography 163

Chapter 6 Linear Models for Electronic Devices 164

- 6-1. The Low-Frequency Model of the FET—The Common-Source Amplifier 164
- 6-2. The Common-Drain FET Amplifier—The Source Follower 169
- 6-3. The Common-Gate FET Amplifier 173
- 6-4. Low-Frequency Junction Transistor Linear Models—Physical Discussion 175
- 6-5. Low-Frequency h -Parameter Models for the Junction Transistor 176
- 6-6. Analysis of Basic Transistor Amplifier Circuits Using h Parameters 185
- 6-7. High-Frequency Linear Models for the FET 195
- 6-8. Common-Source FET Amplifier—High-Frequency Input Admittance—Miller Effect 198
- 6-9. The Source Follower—High-Frequency Input Admittance 200
- 6-10. High-Frequency Linear Models for the Junction Transistor 203
- 6-11. Determination of Hybrid- π Parameters from Published Data 207
- 6-12. Common-Emitter Amplifier—Input Admittance 211
- Problems 214
- Bibliography 222

Chapter 7 Pulse and Large-Signal Models for Electronic Devices 223

- 7-1. The Ebers-Moll Low-Speed Model for the Junction Transistor 223
- 7-2. Approximate Low-Speed Models for the Junction Transistor 226
- 7-3. Low-Speed Model for the FET 231
- 7-4. Approximate Low-Speed Models for the FET 232
- 7-5. High-Speed Model for the Bipolar Junction Transistor 236
- 7-6. Linear and Piecewise Linear Approximate High-Speed Models for the Junction Transistor 239
- 7-7. High-Speed Model for the FET 241
- Problems 243
- Bibliography 245

Chapter 8 Fundamental Elements of Digital Systems 246

- 8-1. Some Basic Ideas of Digital Circuits 246
- 8-2. Logical Operations 252
- 8-3. The AND Operation 253
- 8-4. The OR Operation 254
- 8-5. The Complement or NOT Operation 256
- 8-6. The NOR Operation 257
- 8-7. The NAND Operation 257
- 8-8. The Exclusive OR—XOR Operation 258
- 8-9. Functionally Complete Sets 259
- 8-10. Some Useful Relations—DeMorgan's Theorem 263

8-11. Some Examples of Gate Circuits	266
8-12. A General Procedure for Expressing Arbitrary Switching Functions—Canonical Forms	269
8-13. Minimization of Switching Functions—Karnaugh Maps	278
8-14. Don't Care Conditions	284
Problems	285
Bibliography	289

Chapter 9 Logic Families 290

9-1. Characteristics of Logic Families	290
9-2. Diode Transistor Logic—DTL	292
9-3. An Improved DTL Circuit	300
9-4. High-Threshold Logic—HTL	303
9-5. Transistor-Transistor Logic—TTL	303
9-6. Wired Logic	310
9-7. Active Pull-up	312
9-8. Resistor-Transistor Logic—RTL	320
9-9. Direct Coupled Transistor Logic—DCTL	323
9-10. Integrated-Injection Logic—I ² L	324
9-11. Schottky-Diode Nonsaturating Logic Circuits	329
9-12. Emitter-Coupled Logic—ECL—Nonsaturating Logic	331
9-13. MOSFET Logic	340
9-14. Complementary Symmetry MOSFET Logic—COSMOS Logic—CMOS Logic	343
9-15. Comparison of Logic Gates	346
9-16. Switching Time Specifications of Logic Gates	348
9-17. Manufacturers' Data	349
Problems	356
Bibliography	360

Chapter 10 Sequential Circuits and Their Design 361

10-1. Flip-Flops—Latches	362
10-2. The <i>R-S</i> Flip-Flop	363
10-3. The <i>J-K</i> Flip-Flop	371
10-4. The <i>T</i> Flip-Flop	372
10-5. The <i>D</i> Flip-Flop	373
10-6. Synchronizing and Triggering of Flip-Flops	374
10-7. Master-Slave Flip-Flops	377
10-8. The ac-Coupled Edge-Triggered Flip-Flop	382
10-9. The Capacitive-Storage Edge-Triggered Flip-Flop	385
10-10. Propagation-Delay Edge-Triggered Flip-Flops	387
10-11. Timing of Master-Slave and Edge-Triggered Flip-Flops	388

- 10-12. Registers 391
- 10-13. The Shift Register 391
- 10-14. More Complex Registers—Serial to Parallel and Parallel to Serial Conversion 395
- 10-15. Analysis Techniques for Synchronous Sequential Circuits 398
- 10-16. Design of Synchronous Sequential Circuits 404
- 10-17. Counters 412
- 10-18. Other Counter Circuits 419
- 10-19. Sequence Detectors and Generators 428
- 10-20. Asynchronous Sequential Circuits—Cycles—Races—Oscillation—Hazards 432
- 10-21. Design of Asynchronous Sequential Circuits 439
- 10-22. Integrated Circuit Implementation of Sequential Circuits 444
- Problems 449
- Bibliography 454

Chapter 11 Memories 455

- 11-1. Random Access Memories—RAM's 456
- 11-2. Bipolar Transistor RAM's 460
- 11-3. Schottky Transistor Memory Cells 466
- 11-4. PL Memory Cells 468
- 11-5. Static MOS RAM's 470
- 11-6. Dynamic MOS RAM's 472
- 11-7. Paralleling of RAM Memory Chips 476
- 11-8. Sequential Memories 480
- 11-9. MOS Sequential Memories 482
- 11-10. The Charge Coupled Device CCD; CCD Sequential Memories 488
- 11-11. Read Only Memories—ROM's 494
- 11-12. The Programmable Logic Array—PLA 498
- 11-13. Magnetic Memories 500
- 11-14. The Magnetic Bubble Memory 502
- 11-15. Manufacturers' Data 509
- Problems 509
- Bibliography 511

Chapter 12 Small-Signal Untuned Amplifiers—Broadband Amplifiers 512

- 12-1. Frequency Distortion 512
- 12-2. Decibel Notation 516
- 12-3. Frequency Response of One Stage in a FET Common-Source Amplifier Cascade 520
 - Factors Affecting the Frequency Response of the One-Stage Common-Source FET Amplifier 532
 - Frequency Response of One Stage in a Junction Transistor Common-Emitter Amplifier Cascade 535

12-6.	Factors Affecting the Frequency Response of the One-Stage Common-Emitter Transistor Amplifier	549
12-7.	Bypass Capacitors	551
12-8.	Source Follower Amplifier	558
12-9.	Emitter Follower Amplifier	561
12-10.	Common-Base Amplifier	568
12-11.	Input and Output in a Cascade of Amplifiers	573
12-12.	Bandwidth of Cascaded Amplifier Stages	575
12-13.	Design of Broadband FET Amplifiers	577
12-14.	Design of Broadband Transistor Amplifiers	585
12-15.	The Cascode Amplifier Pair	596
12-16.	Poles and Zeros	599
12-17.	Transient Response	604
12-18.	Noise—Amplifier Sensitivity	612
	Problems	615
	Bibliography	621

Chapter 13 Operational Amplifier Applications 622

13-1.	The Ideal Operational Amplifier—The Quasi-ideal Operational Amplifier	622
13-2.	The Simple Inverting Amplifier	625
13-3.	Noninverting Amplifier Configurations	630
13-4.	The Differential Amplifier—The Balanced Amplifier	632
13-5.	Output Impedance	634
13-6.	The Summer or Adder Circuit	637
13-7.	The Integrator	640
13-8.	A Simple Analog Computer	644
13-9.	The Differentiator	645
13-10.	The Logarithmic Amplifier	646
13-11.	The Comparator	648
13-12.	The Schmitt Trigger-Regenerative Comparator	652
13-13.	Sample and Hold Circuits	655
13-14.	Digital to Analog Converters	658
13-15.	Analog to Digital Converters	662
	Problems	669
	Bibliography	673

Chapter 14 Operational Amplifier Circuitry—The Practical Operational Amplifier 674

14-1.	The FET Differential Input Stage	674
14-2.	The Junction Transistor—Differential Input Stage	678
14-3.	The Cascode Differential Amplifier	682
14-4.	High-Input Impedance Stages	683

- 14-5. Current Sources 689
- 14-6. Use of Current Sources as Load Impedances 697
- 14-7. Cascaded Differential Amplifiers—dc Stability 704
- 14-8. Output Stages 705
- 14-9. Bias Analysis of a Complete Operational Amplifier 713
- 14-10. The Signal Analysis of a Complete Operational Amplifier 721
- 14-11. The Darlington Transistor—Compound Transistors 723
- 14-12. The Frequency Response of Operational Amplifiers 724
- 14-13. Slewing Rate 729
- 14-14. Common Mode Problems 732
- 14-15. Offset Problems 734
- 14-16. Latch Up 736
- 14-17. Operational Amplifier Specifications 737
- Problems 744
- Bibliography 748

Chapter 15 Untuned Power Amplifiers 749

- 15-1. The Efficiency of Ideal Amplifiers 749
- 15-2. The Single-Ended Amplifier 754
- 15-3. The Loudspeaker as a Load Impedance 761
- 15-4. The Complementary Symmetry Push-Pull Amplifier—Graphical Analysis 762
- 15-5. The Quasicomplementary Symmetry Push-Pull Amplifier 772
- 15-6. Distortion in Push-Pull Amplifiers 778
- 15-7. Design of Push-Pull Amplifiers 780
- 15-8. Push-Pull Amplifier with an Output Transformer 784
- 15-9. Thermal Design—Thermal Stability 787
- Problems 793
- Bibliography 798

Chapter 16 Feedback Amplifiers 799

- 16-1. Some Basic Ideas of Feedback Amplifiers 799
- 16-2. Two Very Simple Feedback Amplifiers 802
- 16-3. The Effect of Feedback on Sensitivity—The Importance of Return Difference and Loop Gain 805
- 16-4. The Effect of Feedback on Nonlinear Distortion 807
- 16-5. The Effect of Feedback on Noise 809
- 16-6. The Effect of Feedback on Impedance Levels 810
- 16-7. The Effect of Feedback on Bandwidth 814
- 16-8. The Feedback Pair 816
- 16-9. Use of Linear Models in General Feedback Amplifier Calculations 820
- 16-10. Oscillation in Feedback Amplifiers 824
- 16-11. The Routh-Hurwitz Test for the Location of the Roots of a Polynomial 826

16-12. The Nyquist Criterion for the Stability of a Feedback Amplifier	830
16-13. Further Discussion of Stability	834
16-14. Gain and Phase Margin	839
16-15. Basic Design of Feedback Amplifiers	841
16-16. Corrective Networks	848
16-17. Analysis and Stabilization of Series-Shunt Feedback Circuits	852
Problems	854
Bibliography	859

Chapter 17 Bandpass Amplifiers 860

17-1. The Ideal Bandpass Amplifier	860
17-2. The Parallel Resonant Circuit	861
17-3. The Single-Tuned Capacitance-Coupled Amplifier	865
17-4. Impedance Level Control Using a Tapped Inductance	872
17-5. Mutual Inductance Coupled Single-Tuned Circuits	875
17-6. Double-Tuned Amplifier Circuits	879
17-7. Neutralization	888
17-8. The Superhetrodyne Principle	889
17-9. Active Filters—The Thomas Biquad	891
17-10. The Delyiannis Active Filter	898
17-11. Butterworth Filter Characteristics	901
17-12. The Chebyshev Filter Characteristic	906
17-13. The Low-Pass—Bandpass Transformation	910
Problems	915
Bibliography	920

Chapter 18 Oscillators 921

18-1. RF Oscillators—Criteria for Oscillation	921
18-2. The RC Phase Shift Oscillator	930
18-3. The Wein Bridge Oscillator	933
18-4. Linear and Nonlinear Operation of Sinusoidal Oscillators	934
18-5. Frequency Stability	937
18-6. Crystal Oscillators	939
18-7. The Transistor Astable Multivibrator	940
18-8. The Comparator Astable Multivibrator	943
18-9. A Voltage-Controlled Oscillator	947
18-10. The One-Shot or Monostable Multivibrator	948
18-11. Integrated Circuit Waveform Generators—Timers	951
18-12. Clipping and Clamping Circuits	951
Problems	955
Bibliography	956

Chapter 19 Microprocessors 957

- 19-1. The Basic Elements of a Digital Computer 957
- 19-2. The Arithmetic Logic Unit 959
- 19-3. Basic Microprocessor Architecture 966
- 19-4. Microprocessor Timing Diagrams and Operation 971
- 19-5. Programming and Interfacing the Microprocessor 973
- Problems 982
- Bibliography 984

Chapter 20 Modulation and Demodulation 985

- 20-1. Amplitude Modulation 985
- 20-2. Methods of Amplitude Modulation 990
- 20-3. Detection of Amplitude Modulated Signals 994
- 20-4. Frequency and Phase Modulation 998
- 20-5. Frequency and Phase Modulating Circuits 1003
- 20-6. Frequency and Phase Modulation Detectors That Use Reactive Components 1007
- 20-7. The Phase Locked Loop 1011
- 20-8. Pulse Modulation 1017
- 20-9. Delta Modulation 1021
- Problems 1023
- Bibliography 1026

Chapter 21 Power Supplies 1027

- 21-1. Rectifiers 1027
- 21-2. The Capacitor Filter 1031
- 21-3. Other Filter Circuits 1036
- 21-4. Output Impedance of Power Supplies 1039
- 21-5. Voltage Regulators 1040
- 21-6. Switching Regulators 1044
- 21-7. SCR's, Diacs, and Triacs 1051
- Problems 1055
- Bibliography 1057

Index 1059