

CONTENTS

Preface	ix
Chapter 1	
INTRODUCTION TO DIGITAL ELECTRONICS	1
1.0 Introduction	
1.1 Logic Functions	2
1.2 Karnaugh Maps	6
1.3 Integrated Circuit Fabrication Technology; Scale of Integration	12
1.4 Properties of Digital Circuits	20
1.5 The Ideal Digital Logic Element	21
1.6 Definition of Noise and Noise Margins	22
1.7 Definition of Transient Characteristics	23
1.8 Computer-Aided Design of Digital Circuits	25
1.9 Diode Logic and the Programmable Logic Array (PLA)	27
1.10 Summary	33
References	33
Problems	33
Chapter 2	
METAL-OXIDE-SEMICONDUCTOR (MOS) TRANSISTOR	37
2.0 Introduction	37
2.1 Alternative MOS Processes	37
2.2 Structure and Operation of the MOS Transistor	39
2.3 Threshold Voltage of the MOS Transistor	43
2.4 Current-Voltage Characteristics	49
2.5 Capacitances of the MOS Transistor	52
2.6 Modeling the MOS Transistor for Circuit Simulation	55
*2.7 Limitations on MOS Transistors	59
2.8 Summary	63
References	63
Demonstrations	64
Problems	65

*Denotes material which may be omitted without loss of continuity.

Chapter 3	
MOS INVERTERS AND GATE CIRCUITS	68
3.0 Introduction	68
3.1 Static NMOS Inverter Analysis	70
3.2 Transistors as Load Devices	73
3.3 Circuit Layout and Capacitances	85
3.4 Switching Time Analysis and Power-Delay Product	94
3.5 Complementary MOS (CMOS) Inverter Analysis	97
3.6 NMOS Gate Circuits	102
3.7 CMOS Gate Circuits	105
*3.8 Dynamic Logic Circuits	108
*3.9 Scaling of MOS Circuits	112
3.10 Summary	114
References	115
Demonstrations	116
Problems	117
 Chapter 4	
SEMICONDUCTOR DIODES	125
4.0 Introduction	125
4.1 <i>pn</i> Junction Diodes	127
4.2 The Equilibrium Barrier Potential	128
4.3 Depletion Region Charge	132
4.4 <i>pn</i> Junction with Forward Bias	138
4.5 <i>pn</i> Junction with Reverse Bias	143
4.6 Diode Switching Transients	144
4.7 Diode Structures	149
4.8 Diode Models for Circuit Simulation	153
4.9 Schottky-Barrier Diode	157
*4.10 Temperature Effects	159
*4.11 Breakdown Diodes	161
4.12 Summary	163
References	163
Demonstrations	164
Problems	165
 Chapter 5	
BIPOLAR JUNCTION TRANSISTOR	170
5.0 The Bipolar Junction Transistor	170
5.1 Transistor Operation in Forward Active Mode	170
5.2 Terminal Currents	177
5.3 Modes of Operation	180

5.4	BJT Model for Circuit Simulation Programs	186
5.5	Summary	193
	References	193
	Demonstrations	194
	Problems	196
Chapter 6		
BIPOLAR TRANSISTOR INVERTER		199
6.0	Introduction	199
6.1	Static Characteristics	199
6.2	Charge-Control Analysis	206
6.3	BJT Inverter Switching Times	228
6.4	Schottky-Clamped Inverter	236
6.5	Comparison with SPICE	238
6.6	Summary	242
	References	243
	Demonstrations	243
	Problems	244
Chapter 7		
BIPOLAR DIGITAL GATE CIRCUITS		248
7.0	Introduction	248
7.1	Resistor-Transistor Logic	249
7.2	Diode-Transistor Logic	251
7.3	Transistor-Transistor Logic	255
7.4	Emitter-Coupled Logic	271
7.5	Integrated Injection Logic	283
7.6	Integrated Schottky Logic	291
*7.7	Interfacing	293
7.8	Summary	298
	References	299
	Demonstrations	299
	Problems	301
Chapter 8		
REGENERATIVE LOGIC CIRCUITS		306
8.0	Introduction	306
8.1	Basic Bistable Circuit	307
8.2	SR Latch	308
8.3	JK Flip-Flop	310
8.4	D Flip-Flop	314
8.5	TTL Circuits	315
8.6	ECL Circuits	316
8.7	I ² L Circuits	319

*Denotes material which may be omitted without loss of continuity

8.8	NMOS Circuits	321
8.9	CMOS Circuits	327
8.10	Summary of Flip-Flop Circuits	329
8.11	Schmitt Trigger	332
8.12	Multivibrator Circuits	337
8.13	IC Timer	345
8.14	Summary	350
	References	351
	Demonstrations	351
	Problems	352
Chapter 9		
SEMICONDUCTOR MEMORIES		359
9.0	Introduction and Definitions	359
9.1	Read-Only Memories	363
9.2	Static Read-Write Memories	378
9.3	Dynamic Read-Write Memories	386
9.4	Serial Memories	394
9.5	Summary	397
	References	397
	Problems	398
Chapter 10		
CIRCUIT DESIGN FOR LSI AND VLSI		400
10.0	Introduction	400
10.1	Gate Arrays	401
10.2	Standard Cells	406
10.3	Programmable Logic Array (PLA)	407
10.4	Microprocessors and Microcomputers	408
10.5	Circuit Design for VLSI	410
10.6	Summary	421
	References	421
	Problems	422
Answers to Exercises		424
Index		431