

CONTENTS

<i>Preface</i>	V
<i>Preface to the English edition</i>	VII
<i>Main symbols and abbreviations</i>	IX
1. <i>Introduction to the problems of integrated circuits</i>	1
2. <i>Principles of integrated-circuit technology</i>	7
2.1 Principles of monolithic planar technology	7
2.2 Thin-film technology	22
2.3 Thick-film technology	26
2.4 Principles of hybrid technologies	27
3. <i>Elements of integrated functional blocks</i>	28
3.1 Resistors	29
3.1.1 Monolithic resistors	33
3.1.2 Thin-film resistors	38
3.1.3 Thick-film resistors	40
3.2 Capacitors	42
3.2.1 Film capacitors	42
3.2.2 Junction capacitors	48
3.3 Diodes	52
3.4 Transistors	54
3.5 Special types of integrated-circuit elements	68
4. <i>Models of transistors and diodes for integrated functional blocks</i>	76
4.1 Linear models of integrated transistors	76
4.1.1 Noise in transistors	83
4.2 Nonlinear models of integrated transistors	85
5. <i>Principles of integrated-circuit design</i>	97
5.1 The idea of functional blocks	97
5.2 Economic aspects	100
5.3 Reliability questions	106
5.4 Basic physical limitations and energy relations of integrated circuits	121
5.5 Parasitic effects	135
5.6 Parameter tolerances	137
5.7 Planarity problems	137
6. <i>Principles of the theory of sensitivities and tolerances</i>	141
6.1 Relation between the circuit functions and their parameters	142

6.2	Basic concepts of the theory of sensitivities and tolerances	148
6.3	Multiparameter sensitivity	155
6.4	Large-change sensitivities and tolerances	164
6.5	Methods of sensitivity determination	170
7.	<i>Theoretical principles of integrated-circuit design</i>	179
7.1	Computer methods of integrated-circuit design	179
7.2	Circuit functions and methods for their approximation	187
7.2.1	Most important types of circuit functions of integrated functional blocks	188
7.2.2	Survey of approximation methods	192
7.3	Analysis of circuit models and systems	197
7.4	Principles of optimization methods used in the design of integrated functional blocks	205
7.4.1	Linear and linearized optimization	208
7.4.2	Nonlinear optimization	212
7.5	Optimization programs and software packages	225
7.5.1	The GOSPEL optimization package	226
7.5.2	The UNOPT and UNMIN optimization packages	227
7.5.3	The SPONA optimization package	228
7.6	Morphological design of integrated-circuit	230
7.7	Application of computer methods in the integrated-circuit production process	243
7.8	Program systems for computer-aided integrated-circuit analysis and synthesis	244
8.	<i>Basic integrated logic functional blocks</i>	248
8.1	Problems of integrated logic circuits and networks	248
8.2	Properties of the main types of integrated logic functional blocks	253
8.3	Integrated functional memory blocks	275
9.	<i>Basic linear integrated functional blocks</i>	281
9.1	Basic types of integrated functional blocks	281
9.2	Integrated amplifiers	285
9.3	Gyrators, converters and mutators	313
9.4	Stabilized power sources	323
9.5	Distributed RC functional blocks	332
9.6	Selective functional blocks	337
9.7	Special linear integrated functional blocks	362
	<i>References</i>	368
	<i>Index</i>	384