

Contents

Preface *xiii*

Chapter	1	Introduction to Linear Integrated Circuits	1
	1-1	General Significance of Linear Integrated Circuits	1
	1-2	Development of Linear Integrated Circuits	2
	1-3	Using a Simple Linear Integrated Circuit	3
	1-4	Types of Linear-Integrated-Circuit Functions	5
	1-5	Types of Linear Integrated Circuits	7
	1-6	Medium-Scale and Large-Scale Integration	7
	1-7	Standardization Tendencies for Linear Integrated Circuits	8
	1-8	Making a Practical Choice of an Industry-Standard OP-AMP Type	9
	1-9	Sequence of Presentation	9
	1-10	Linear Subsystems	9
Chapter	2	General Conditions Governing Linear Integrated Circuit Design	11
	2-1	Monolithic versus Discrete Components	11
	2-2	Monolithic <i>NPN</i> Transistors	12
	2-3	Monolithic Diodes	14
	2-4	Monolithic <i>PNP</i> Transistors	15

	2-5	Monolithic Resistors	16
	2-6	Monolithic Capacitors	17
	2-7	Monolithic Components with No Discrete Counterparts	18
	2-8	Basic Techniques in the Design of Linear Integrated Circuits	19
	2-9	Monolithic versus Hybrid Integrated-Circuit Designs	20
	2-10	Linear-Integrated-Circuit Arrays	20
	2-11	Transistor Arrays	21
	2-12	Monolithic Techniques with Transistor Arrays	25
	2-13	Precautions in Applying Transistor Arrays	28
	2-14	Multiple-Function Linear Integrated Circuits	29
	2-15	Combining Transistor Families on a Single Chip	30
	2-16	Amplifier Arrays	30
	2-17	Advanced Forms of the Monolithic Chip	34
		<i>Questions</i>	34
Chapter	3	Differential Amplifier Stage in Integrated-Circuit Design	37
	3-1	General Elements in Integrated-Circuit Design	37
	3-2	Choice of Differential Amplifier for Integrated-Circuit Input Stage	39
	3-3	Circuit Action of Differential-Amplifier Stage	40
	3-4	Constant-Current Circuit	46
	3-5	Practical Circuit for Single-Ended Stage	47
	3-6	Common-Mode Rejection Ratio	49
	3-7	Input-Stage Variations in Practical Integrated Circuits	50
		<i>Questions</i>	51
		<i>Problems</i>	52
Chapter	4	Operational Amplifier Characteristics	55
	4-1	Basic Requirements for the Operational Amplifier	55
	4-2	Analysis and Practical Example of Operational-Amplifier Action	56
	4-3	Flexible Use of Operational-Amplifier Circuits	60
	4-4	Data Sheet: Type 741 OP-AMP Characteristics	61
	4-5	Major Operational-Amplifier Characteristics	66
	4-6	Comparison Chart of Typical Values of OP-AMP Characteristics	67
	4-7	Interpreting Operational-Amplifier Data Sheets	70
	4-8	Approximate Values of Typical OP-AMP Specifications	71
		<i>Questions</i>	74
		<i>Problems</i>	75
Chapter	5	General Operational Amplifier Applications	77
	5-1	Kinds of Operational Amplifier Applications	77
	5-2	Choice of Operational Amplifier in Typical Applications	78

5-3	Basic Circuit Configurations	78
5-4	Inverting Voltage Amplifier	78
5-5	Noninverting Voltage Amplifier	80
5-6	Voltage Follower (Unity-Gain Amplifier)	82
5-7	Summing Amplifier	83
5-8	Integrating Amplifier	84
5-9	Differentiating Amplifier	86
5-10	Square-Wave Generator (Multivibrator)	88
5-11	Sine-Wave Oscillators	90
5-12	Linear Rectifiers	93
5-13	Peak Detector	95
5-14	Current-to-Voltage Converter	96
5-15	Differential (Instrumentation-Type) Amplifier	97
5-16	Current-Difference (Norton) OP AMP: Single-Supply Operation	101
5-17	Additional OP-AMP and LIC Circuits (BiFET and BiMOS)	104
	<i>Questions</i>	107
	<i>Problems</i>	108

Chapter 6 Testing and Breadboarding Operational Amplifiers 111

6-1	Levels of Testing Linear Integrated Circuits	111
6-2	Basic Laboratory Tests	111
6-3	Voltage Gain (Tests for Open-Loop, Closed-Loop, and Loop Gain)	112
6-4	Input-Resistance Tests	116
6-5	Bandwidth (Estimating and Testing)	119
6-6	Output-Resistance (R_o) Test	121
6-7	Common-Mode Rejection Tests	122
6-8	Input-Offset Error (I_B , I_{io} , and V_{io}) Tests	124
6-9	Improved-Specification Types of OP AMPs	125
6-10	Curve-Tracer Method of Testing Amplifiers	126
6-11	Breadboarding the Integrated-Circuit Package	129
6-12	Automated Linear-Integrated-Circuit Testing	132
6-13	Engineering Evaluation (Semiautomatic) Testing	133
6-14	Quick-Check Test Method for OP AMPs	135
	<i>Questions</i>	137
	<i>Problems</i>	138

Chapter 7 Power Amplifiers: Direct Current and Audio 141

	Power Limitations in Integrated-Circuit Operational Amplifiers	141
7-2	High Output-Current Operational Amplifiers	142
7-3	Power Boosters	142
7-4	Power Operational Amplifier	143

	Audio Power Amplifiers (to 1 or 2 Watts)	146
7-6	Higher-Power Integrated-Circuit Audio Amplifiers	148
	<i>Questions</i>	155
	<i>Problems</i>	156
Chapter 8	Consumer Communication Circuits	157
8-1	Impact of Linear Integrated Circuits on Communication Equipment	157
8-2	Broadcast FM Receiver Circuits	161
8-3	FM-IF Strips	163
8-4	FM Stereo Multiplex Decoders	168
8-5	Broadcast AM Receiver Circuits	171
8-6	Television Applications	176
8-7	Mixers, Modulators, and Multipliers	182
8-8	Phase-Locked Loop	186
	<i>Questions</i>	192
	<i>Problems</i>	192
Chapter 9	Regulators and Control Circuits	193
9-1	Power Control with Monolithic Circuits	193
9-2	Voltage Regulators	194
9-3	Series versus Shunt Regulators	196
9-4	Current Limiting	197
9-5	Representative Example of a Voltage Regulator	197
9-6	Applications of the 723-Type Regulator	200
9-7	Other Regulator Types	207
9-8	Zero-Voltage Switches	214
	<i>Questions</i>	217
	<i>Problems</i>	219
Chapter 10	Digital-Interface Circuits	221
10-1	Differential Voltage Comparators	221
10-2	Operation of Comparator	222
10-3	Comparator Characteristics	223
10-4	Advanced-Performance Comparators	225
10-5	Sense Amplifiers	227
10-6	Analog-to-Digital and Digital-to-Analog Converters	229
10-7	Borderline Linear-Digital Integrated Circuits	236
10-8	Complementary MOS (CMOS) Types	237
	<i>Questions</i>	237
	<i>Problems</i>	238
Chapter 11	Precision and Instrumentation Operational Amplifiers	239
11-1	Major High-Performance Characteristics	239
11-2	Development of Precision Operational Amplifiers	240

-3	Selecting Operational Amplifiers for High-Performance Characteristics	241
11-4	Low-Bias-Current (I_B)-High-Input Impedance (Z_{in}) Types	245
11-5	Low Voltage-Drift Types	245
11-6	Additional High-Performance Features	247
11-7	Wide-Band (High-Slew-Rate) Types	247
11-8	Micropower Types	251
11-9	Instrumentation Amplifier	252
11-10	Representative Instrumentation Amplifier (Monolithic)	261
11-11	Modular Form of Instrumentation Amplifier	264
	<i>Questions</i>	268
	<i>Problems</i>	269
 Chapter 12	Specialized Linear-Integrated-Circuit Applications	271
12-1	Expansion of Linear-Integrated-Circuit Functions	271
12-2	Programmable Amplifiers	272
12-3	Operational Amplifier as a Regulated Voltage Source	272
12-4	Current-Source Application	274
12-5	Active Filter Applications	275
12-6	Gyrators and Q -Factor in Active Filters	285
12-7	Logarithmic Amplifier	289
12-8	Low-Noise and High-Impedance (Electrometer) Applications	294
12-9	Sample-and-Hold Applications	297
12-10	Multiple (Triple and Quad) Operational Amplifiers	299
12-11	Voltage-Controlled Oscillator (VCO) and Waveform Generators	305
12-12	The 555 Timer	312
12-13	Multipliers, Dividers, Squarers, Square Rooters	315
12-14	Digital-Voltmeter System	321
12-15	Sources for Specific Technical Information	324
	<i>Questions</i>	325
	<i>Problems</i>	325
	<i>Bibliography</i>	327
 Appendix	Decibel Conversion Chart	329
 Appendix II	Classification of LIC Groups and Selection Guide for OP AMPS	331
 Appendix III	Cross-Reference List of LICs and Key to Identification of Manufacturers' Types	333

Appendix IV Manufacturers' Addresses 343

Appendix V Answers to Selected Questions and Problems 345

Index 340