

# Contents

<b>Introduction</b>	<b>7</b>
<b>1 Bipolar IC Devices and Operational Amplifiers</b>	<b>9</b>
The Operational Amplifier—Op Amp Input Circuit—Operational Amplifier Symbol—Properties of the Operational Amplifier—Inverting Follower Circuits—Noninverting Followers with Gain—Recapitulation—Unity Gain Noninverting Followers—Differential Amplifiers—Operational Amplifier Problems	
<b>2 Discrete-Device Timers</b>	<b>26</b>
Simple Timers—Relaxation Oscillators—Transistor Monostable Multivibrator	
<b>3 Some TTL and CMOS Devices</b>	<b>35</b>
Interfacing CMOS and TTL—CMOS Timers—TTL Timers—TTL Monostable Chips	
<b>4 Basics of Digital Electronics</b>	<b>47</b>
Logic States—Positive and Negative Logic—Logic Families—Speed vs Power—RTL Devices—DTL Devices—TTL Devices—CMOS Devices—HTL Devices—Gates—TTL and CMOS Examples—Some Experiments in Logic Gates—Flip-Flops—Some Flip-Flop Experiments—Additional Types of Flip-Flop—Experiments in Clocked Flip-Flops—Multivibrators (The Heart of the Timer Circuit)—Digital Counters	
<b>5 The 555 Timer</b>	<b>106</b>
<b>6 Monostable Operation of the 555</b>	<b>109</b>
Example—Some 555 One-Shot Applications and Projects	
<b>7 Astable Operation of the 555</b>	
Example—555 Astable Multivibrator Applications	
<b>8 Exar XR-2240</b>	

<b>9</b>	<b>XR-2240 Projects</b>	<b>161</b>
	Staircase or Ramp Generator—Analog-to-Digital Converter—Digital Sample-and-Hold Circuit—Programmable Astable Multivibrator—Ten-Minute Timer for Amateur Radio ID—Sixty-Second Timer—Three-Minute Egg Timer—Timer Audio Output Circuit—Binary Address Sequence—Programmable Monostable Multivibrator	
<b>10</b>	<b>CMOS Timer Circuits</b>	<b>174</b>
	CMOS 4528 Device—4013 as a One-Shot—Bounceless Pushbuttons—Water Level Detector—Touch-Plate Switches—Astable Multivibrators—Address Sequencer—Two-Phase CMOS Clock—Multiphase Clock—Oscilloscope Dual-Trace Switch	
<b>11</b>	<b>TTL Timers</b>	<b>199</b>
	Two-Phase Digital Clock—Multiphase Digital Clock—Transistor-TTL Clock—TTL Crystal Oscillator—MC4024P TTL Oscillator—MC4024P Crystal Oscillator—MC4024P VCO—60-Hz Clock—One-Second Clock—Sixty-Second Timer—Three-Minute Timer—Shift-Register One-Shot—Autoresetting Shift Register Timer—Interstimulus Timer for Evoked Potentials Studies—Main Control Unit	
<b>12</b>	<b>Retriggerable Timers</b>	<b>220</b>
	Operation—TTL Monostable Multivibrators	
<b>13</b>	<b>Very Long Duration Timers</b>	<b>228</b>
	TTL Long-Duration Timer—Intersil 8250/8260 Long-Duration Timer	
<b>14</b>	<b>Op-Amp Timers</b>	<b>237</b>
	Op-Amp as Comparator—Operational Amplifier Monostable Multivibrator—Operational Amplifier Astable Multivibrators	
	<b>Alarm Projects</b>	<b>246</b>
	Low-Battery Alarm—Automatic Battery Charger—Power Failure Alarm—Low Light Monitor—Low Temperature Alarm—Idiot Lamp Monitor—Burglar Alarm (I)—Burglar Alarm (II)—Burglar Alarm (III)—Burglar Alarm (IV)	
<b>16</b>	<b>Some More Projects</b>	<b>262</b>
	DC-DC Converter—Dice Game—Temperature Monitor—Digital Capacitance Meter—Continuity Tester (Visual)—Aural Continuity Tester (I)—Aural Continuity Tester (II)	
<b>17</b>	<b>And Still More Projects</b>	<b>271</b>
	Sidetone Oscillator—Variable Pulse Generator—Warble Siren—Touch-Plate Switches—Pulse Catcher—Digital Logic Probe—Oscilloscope Calibrator	
	<b>Appendix A Universal Experimenter's Power Supply</b>	<b>284</b>
	<b>Appendix B Interfacing Timer ICs with High-Power Loads</b>	<b>289</b>
	<b>Appendix C Resistors and Capacitors</b>	
	<b>Index</b>	