

CONTENTS

	Preface	vii
1	DIRECT CURRENT CIRCUITS	1
	Introductory Concepts	2
	<i>Potential difference. Current and current density. Ohm's law. Joule's law.</i>	
	Circuit Elements	9
	<i>Resistors. Batteries.</i>	
	Simple Circuits	15
	<i>Series circuits. Parallel circuits. Networks.</i>	
	Circuit Analysis	20
	<i>Kirchhoff's rules. Wheatstone bridge. Potentiometer circuit.</i>	
	Equivalent Circuits	29
	<i>Thévenin's theorem. Norton's theorem. Maximum power transfer</i>	
	Electrical Measurements	35
	<i>D'Arsonval meter. Ammeters and voltmeters. Ohmmeters and multimeters.</i>	
2	ALTERNATING CURRENTS	46
	Sinusoidal Signals	47
	<i>Frequency, amplitude, and phase. RMS value. Power factor.</i>	
	Capacitance	50
	<i>Origin of capacitance. The parallel-plate capacitor. Series and parallel capacitors. RC filter. Differentiating and integrating circuits.</i>	
	Inductance	61
	<i>Origin of inductance. Inductors. RL filter.</i>	
	Transformers	70
	<i>Mutual inductance. Transformer ratio. Transformer construction.</i>	

Complex Waveforms	73
<i>Fourier series. Oscilloscope.</i>	
AC-CIRCUIT ANALYSIS	83
Impedance	84
<i>Reactance. Complex impedance.</i>	
RLC Circuits	88
<i>Series resonance. Parallel resonance. Q factor.</i>	
Bridge Circuits	96
<i>Inductance and capacitance bridge. Wien bridge. Bridged-T filter. Twin-T network.</i>	
Transient Currents	104
<i>Inductive time constant. Capacitive time constant. Ringing. Square-wave response.</i>	
DIODES	117
Practical Rectifiers	118
<i>The vacuum diode. The junction diode.</i>	
Rectifier Circuits	127
<i>Half-wave rectifier. Full-wave rectifier. Bridge rec- tifier. Voltage doubler.</i>	
Filters	132
<i>Capacitor filter. L-section filter. π-section filter.</i>	
Voltage Regulators	139
<i>Zener diodes. VR tubes. Controlled rectifiers.</i>	
Diode Circuits	145
<i>Clippers. Clamps. AC voltmeters. Detectors.</i>	
VACUUM TUBE CIRCUITS	155
Triodes	156
<i>The grid. Plate characteristics. Small signal param- eters. Triode equivalent circuit.</i>	
Pentodes	166
<i>Screen and suppressor grids. Norton equivalent cir- cuit. Other multigrid tubes.</i>	
Grid Bias	172
<i>Cathode bias. Screen bias.</i>	
Special Circuits	175
<i>Cathode follower. Difference amplifier. VTVM. Class A, B, and C amplifiers.</i>	

TRANSISTORS	189
Semiconductors	190
<i>Energy bands. Electrons and holes. Extrinsic semiconductors.</i>	
PN-Junction Devices	197
<i>Energy-band diagram. Parametric diodes. Minority carrier injection.</i>	
Junction Transistors	201
<i>Theory of junction transistors. The T-equivalent circuit. Fabrication of transistors. Hybrid parameters.</i>	
Transistor Circuits	216
<i>Biasing. Common-emitter amplifier. Grounded-base amplifier. The emitter follower. Complementary symmetry.</i>	
Other Semiconductor Devices	228
<i>Field-effect transistors. Silicon controlled rectifiers. Tunnel diodes. Heterojunctions. Injection lasers. Integrated circuits.</i>	
AMPLIFIERS	242
Voltage Amplifiers	243
<i>Cascading. Low-frequency gain. High-frequency gain. Decoupling.</i>	
Power Amplifiers	255
<i>Transformer coupling. Push-pull amplifier.</i>	
Tuned Amplifiers	263
<i>Tuned coupling. Neutralization.</i>	
Noise	268
<i>Nyquist noise. $1/f$ Noise. Noise in tubes and transistors. Stray pickup.</i>	
Special Circuits	277
<i>Cascode amplifier. DC amplifiers. Chopper amplifiers. Lock-in amplifier.</i>	
FEEDBACK AMPLIFIERS	288
Negative Feedback	289
<i>Voltage feedback. Current feedback. Stability.</i>	
Operational Amplifiers	301
<i>Operational feedback. Mathematical operations. Analog computers. Measurement and control.</i>	

Voltage Regulators*Series regulator. Practical circuits.***Servo Amplifiers**

319

*Mechanical feedback. The recording potentiometer.
Servo amplifiers.***9****OSCILLATORS****Positive Feedback**

329

RC Oscillators

330

*Phase-shift oscillator. Wien-bridge oscillator.***Resonant Circuit Oscillators***LC oscillators. Crystal oscillators.***Relaxation Oscillators***Sawtooth generators. Blocking oscillator.***Special Circuits***Converters and inverters. Regenerative and superregenerative detectors.***10****PULSE AND DIGITAL CIRCUITS****Pulse Amplifiers**

358

*Rise time. Tilt. Square-wave testing.***Multivibrators***Astable multivibrators. The binary. Monostable multivibrators.***Waveform Generators***The diode pump. Ramp generators. Pulse regeneration.***Counters**

381

*Binary and decade scalars. The Dekatron counter.
Frequency meters and timers.***Digital Circuits***Binary numbers. Logic gates. The digital computer.
Digital instruments.***11****MEASUREMENT CIRCUITS**

411

Transducers

412

*Mechanical transducers. The pH meter. Ion gauges.
Photocells.*

Transmission Lines and Waveguides	425
<i>Characteristic impedance. Delay time. Reflections and resonance. Waveguides.</i>	
Electrical Measurements	434
<i>Electrometers. Oscilloscopes. The waveform analyzer.</i>	
Recorders	442
<i>Chart recorders. The oscillograph. Magnetic recorders.</i>	
Appendix 1	451
<i>Resistor and capacitor color codes.</i>	
Appendix 2	454
<i>Effective value of complex waveforms.</i>	
Appendix 3	457
<i>Characteristic curves of tubes and transistors.</i>	
Index	465