

# Contents

## Preface xi

## Survey of Electronics 2

- S-1 Development of Electronics 4
- S-2 Wireless Broadcasting 4
- S-3 Radio Broadcast Services 5
- S-4 Applications of Electronics 6
- S-5 Electronic Components 8
- S-6 Electronic Circuits 11

## Chapter 1 Electricity 12

- 1-1 Negative and Positive Polarities 14
- 1-2 Electrons and Protons in the Atom 14
- 1-3 Structure of the Atom 17
- 1-4 The Coulomb Unit of Charge 19
- 1-5 The Volt Unit of Potential Difference 21
- 1-6 Charge in Motion Is Current 22
- 1-7 Resistance Is Opposition to Current 26
- 1-8 The Closed Circuit 27
- 1-9 Direct Current (DC) and Alternating Current (AC) 30
- 1-10 Sources of Electricity 31
- Summary 32

## Chapter 2 Ohm's Law 36

- 2-1 The Current  $I = V/R$  38
- 2-2 The Voltage  $V = IR$  39
- 2-3 The Resistance  $R = V/I$  40
- 2-4 Practical Units 40
- 2-5 Multiple and Submultiple Units 41
- 2-6 The Linear Proportion between  $V$  and  $I$  42
- 2-7 Electric Power 43
- 2-8 Power Dissipation in Resistance 45
- 2-9 Power Formulas 46
- 2-10 Electric Shock 47
- Summary 48

## Chapter 3 Series Circuits 52

- 3-1 Why  $I$  Is the Same in All Parts of a Series Circuit 54
- 3-2 Total  $R$  Equals the Sum of All Series Resistances 55
- 3-3 Series  $IR$  Voltage Drops 57
- 3-4 The Sum of Series  $IR$  Drops Equals the Applied  $V_T$  57

- 3-5 Polarity of  $IR$  Voltage Drops 58
- 3-6 Polarities to Chassis Ground 60
- 3-7 Total Power in a Series Circuit 60
- 3-8 Series-Aiding and Series-Opposing Voltages 61
- 3-9 Analyzing Series Circuits 62
- 3-10 Effect of an Open Circuit in a Series Path 63
- Summary 65

## Chapter 4 Parallel Circuits 70

- 4-1 The Applied Voltage  $V_A$  Is the Same Across Parallel Branches 72
- 4-2 Each Branch  $I$  Equals  $V_A/R$  72
- 4-3 The Main-Line  $I_T$  Equals the Sum of the Branch Currents 73
- 4-4 Resistances in Parallel 75
- 4-5 Conductances in Parallel 79
- 4-6 Total Power in Parallel Circuits 79
- 4-7 Analyzing Parallel Circuits 80
- 4-8 Effect of an Open Branch in Parallel Circuits 80
- 4-9 Effect of a Short Circuit Across Parallel Branches 81
- Summary 82

## Chapter 5 Series-Parallel Circuits 86

- 5-1 Finding  $R_T$  for Series-Parallel Resistances 88
- 5-2 Resistance Strings in Parallel 89
- 5-3 Resistance Banks in Series 90
- 5-4 Resistance Banks and Strings in Series-Parallel 91
- 5-5 Analyzing Series-Parallel Circuits 92
- 5-6 Wheatstone Bridge 95
- 5-7 Chassis-Ground Connections 96
- 5-8 Voltages Measured to Chassis Ground 96
- 5-9 Opens and Shorts in Series-Parallel Circuits 98
- Summary 100

## Chapter 6 Resistors 106

- 6-1 Types of Resistors 108
- 6-2 Resistor Color Coding 110
- 6-3 Variable Resistors 111
- 6-4 Rheostats and Potentiometers 113
- 6-5 Power Rating of Resistors 115
- 6-6 Choosing the Resistor for a Circuit 116
- 6-7 Series and Parallel Combinations of Resistors 117
- 6-8 Resistor Troubles 117
- Summary 118

## **Review: Chapters 1 to 6 123**

### **Chapter 7 Voltage Dividers and Current Dividers 126**

- 7-1 Series Voltage Dividers 128
- 7-2 Current Divider with Two Parallel Resistances 129
- 7-3 Current Division by Parallel Conductances 131
- 7-4 Series Voltage Divider with Parallel Load Current 132
- 7-5 Design of a Loaded Voltage Divider 133
- Summary 134

### **Chapter 8 Direct-Current Meters 138**

- 8-1 Moving-Coil Meter 140
- 8-2 Measurement of Current 141
- 8-3 Meter Shunts 143
- 8-4 The Ayrton or Universal Shunt 145
- 8-5 Voltmeters 147
- 8-6 Loading Effect of a Voltmeter 151
- 8-7 Ohmmeters 152
- 8-8 Multimeters 156
- 8-9 Digital Multimeter (DMM) 158
- 8-10 Meter Applications 159
- 8-11 Checking Continuity with the Ohmmeter 161
- Summary 162

## **Review: Chapters 7 and 8 166**

### **Chapter 9 Kirchhoff's Laws 168**

- 9-1 Kirchhoff's Current Law 170
- 9-2 Kirchhoff's Voltage Law 170
- 9-3 Method of Branch Currents 172
- 9-4 Node-Voltage Analysis 175
- 9-5 Method of Mesh Currents 177
- Summary 179

### **Chapter 10 Network Theorems 182**

- 10-1 Superposition 184
- 10-2 Thevenin's Theorem 185
- 10-3 Thevenizing a Circuit with Two Voltage Sources 188
- 10-4 Thevenizing a Bridge Circuit 189
- 10-5 Norton's Theorem 191
- 10-6 Thevenin-Norton Conversions 194
- 10-7 Conversion of Voltage and Current Sources 195
- 10-8 Millman's Theorem 196
- 10-9 T and  $\pi$  Networks 198
- Summary 202

## **Review: Chapters 9 and 10 206**

### **Chapter 11 Conductors and Insulators 208**

- 11-1 Function of the Conductor 210
- 11-2 Standard Wire Gage Sizes 210
- 11-3 Types of Wire Conductors 212
- 11-4 Printed Wiring 213
- 11-5 Switches 214
- 11-6 Fuses 216
- 11-7 Wire Resistance 217
- 11-8 Temperature Coefficient of Resistance 220
- 11-9 Ion Current in Liquids and Gases 221
- 11-10 Electrons and Hole Charges in Semiconductors 223
- 11-11 Insulators 224
- 11-12 Troubleshooting Hints 225
- Summary 226

### **Chapter 12 Batteries 230**

- 12-1 General Features of Batteries 232
- 12-2 The Voltaic Cell 233
- 12-3 Carbon-Zinc Dry Cell 235
- 12-4 Alkaline Cell 236
- 12-5 Additional Types of Primary Cells 236
- 12-6 Lithium Cell 237
- 12-7 Lead-Acid Wet Cell 238
- 12-8 Additional Types of Secondary Cells 242
- 12-9 Series and Parallel Cells 243
- 12-10 Current Drain Depends on Load Resistance 245
- 12-11 Internal Resistance of a Generator 245
- 12-12 Why the Terminal Voltage Drops with More Load Current 246
- 12-13 Constant-Voltage and Constant-Current Sources 248
- 12-14 Matching a Load Resistance to the Generator 249
- Summary 251

## **Review: Chapters 11 and 12 254**

### **Chapter 13 Magnetism 256**

- 13-1 The Magnetic Field 258
- 13-2 Magnetic Flux  $\phi$  259
- 13-3 Flux Density  $B$  260
- 13-4 Induction by the Magnetic Field 261
- 13-5 Air Gap of a Magnet 262
- 13-6 Types of Magnets 264
- 13-7 Ferrites 265
- 13-8 Magnetic Shielding 266
- 13-9 The Hall Effect 266
- Summary 267

### **Chapter 14 Magnetic Units 270**

- 14-1 Ampere-Turns ( $NI$ ) 272
- 14-2 Field Intensity ( $H$ ) 273

- 14-3 Permeability ( $\mu$ ) 274
- 14-4  $B$ - $H$  Magnetization Curve 275
- 14-5 Magnetic Hysteresis 276
- 14-6 Ohm's Law for Magnetic Circuits 277
- 14-7 Relations between Magnetic Units 278
- 14-8 Comparison of Magnetic and Electric Fields 279
- Summary 281

## Chapter 15 Electromagnetic Induction 284

- 15-1 Magnetic Field Around an Electric Current 286
- 15-2 Magnetic Polarity of a Coil 287
- 15-3 Motor Action between Two Magnetic Fields 288
- 15-4 Induced Current 290
- 15-5 Lenz' Law 291
- 15-6 Generating an Induced Voltage 292
- 15-7 Faraday's Law of Induced Voltage 293
- Summary 295

## Chapter 16 Alternating Voltage and Current 298

- 16-1 AC Applications 300
- 16-2 Alternating-Voltage Generator 300
- 16-3 The Sine Wave 303
- 16-4 Alternating Current 304
- 16-5 Voltage and Current Values for a Sine Wave 305
- 16-6 Frequency 307
- 16-7 Period 309
- 16-8 Wavelength 309
- 16-9 Phase Angle 311
- 16-10 The Time Factor in Frequency and Phase 314
- 16-11 AC Circuits with Resistance 315
- 16-12 Nonsinusoidal AC Waveforms 317
- 16-13 Harmonic Frequencies 318
- 16-14 The 60-Hz AC Power Line 319
- 16-15 Motors and Generators 321
- Summary 322

## Review: Chapters 13 to 16 327

## Chapter 17 Inductance 330

- 17-1 Inductance by Alternating Current 332
- 17-2 Self-Inductance  $L$  333
- 17-3 Self-Induced Voltage  $v_L$  335
- 17-4 How  $v_L$  Opposes a Change in Current 335
- 17-5 Mutual Inductance  $L_M$  337
- 17-6 Transformers 339
- 17-7 Core Losses 343
- 17-8 Types of Cores 344
- 17-9 Variable Inductance 345
- 17-10 Inductances in Series or Parallel 346

- 17-11 Stray Inductance 348
- 17-12 Energy in Magnetic Field of Inductance 348
- 17-13 Troubles in Coils 349
- Summary 350

## Chapter 18 Inductive Reactance 354

- 18-1 How  $X_L$  Reduces the Amount of  $I$  356
- 18-2  $X_L = 2\pi fL$  357
- 18-3 Series or Parallel Inductive Reactances 359
- 18-4 Ohm's Law Applied to  $X_L$  360
- 18-5 Applications of  $X_L$  for Different Frequencies 360
- 18-6 Waveshape of  $v_L$  Induced by Sine-Wave Current 362
- Summary 365

## Chapter 19 Inductive Circuits 368

- 19-1 Sine-Wave  $i_L$  Lags  $v_L$  by  $90^\circ$  370
- 19-2  $X_L$  and  $R$  in Series 371
- 19-3 Impedance  $Z$  372
- 19-4  $X_L$  and  $R$  in Parallel 374
- 19-5  $Q$  of a Coil 377
- 19-6 AF and RF Chokes 379
- 19-7 The General Case of Inductive Voltage 381
- 19-8 Calculating the  $L/R$  Time Constant 382
- Summary 383

## Review: Chapters 17 to 19 388

## Chapter 20 Capacitance 390

- 20-1 How Charge Is Stored in the Dielectric 392
- 20-2 Charging and Discharging a Capacitor 393
- 20-3 The Farad Unit of Capacitance 394
- 20-4 Typical Capacitors 397
- 20-5 Electrolytic Capacitors 400
- 20-6 Capacitor Color Coding 401
- 20-7 Parallel Capacitances 402
- 20-8 Series Capacitances 402
- 20-9 Stray Capacitive and Inductive Effects 403
- 20-10 Energy in Electrostatic Field of Capacitance 405
- 20-11 Troubles in Capacitors 406
- Summary 407

## Chapter 21 Capacitive Reactance 412

- 21-1 Alternating Current in a Capacitive Circuit 414
- 21-2  $X_C = 1/(2\pi fC)$  415
- 21-3 Series or Parallel Capacitive Reactances 417
- 21-4 Ohm's Law Applied to  $X_C$  418
- 21-5 Applications of Capacitive Reactance 419
- 21-6 Sine-Wave Charge and Discharge Current 419
- Summary 423

**Chapter 22 Capacitive Circuits 426**

- 22-1 Sine-Wave  $v_C$  Lags  $i_C$  by  $90^\circ$  428
- 22-2  $X_C$  and  $R$  in Series 429
- 22-3 RC Phase-Shifter Circuit 431
- 22-4  $X_C$  and  $R$  in Parallel 431
- 22-5 RF and AF Coupling Capacitors 433
- 22-6 Capacitive Voltage Dividers 434
- 22-7 The General Case of Capacitive Current  $i_C$  436
- 22-8 Calculating the RC Time Constant 436
- Summary 437

**Chapter 23 RC and L/R Time Constants 442**

- 23-1 Response of Resistance Alone 444
- 23-2 L/R Time Constant 444
- 23-3 High Voltage Produced by Opening RL Circuit 445
- 23-4 RC Time Constant 447
- 23-5 RC Charge and Discharge Curves 449
- 23-6 High Current Produced by Short-Circuiting RC Circuit 450
- 23-7 RC Waveshapes 451
- 23-8 Long and Short Time Constants 452
- 23-9 Charge and Discharge with Short RC Time Constant 453
- 23-10 Long Time Constant for RC Coupling Circuit 454
- 23-11 Universal Time Constant Graph 455
- 23-12 Comparison of Reactance and Time Constant 457
- Summary 458

**Review: Chapters 20 to 23 462****Chapter 24 Alternating-Current Circuits 466**

- 24-1 AC Circuits with Resistance but No Reactance 468
- 24-2 Circuits with  $X_L$  Alone 468
- 24-3 Circuits with  $X_C$  Alone 470
- 24-4 Opposite Reactances Cancel 470
- 24-5 Series Reactance and Resistance 472
- 24-6 Parallel Reactance and Resistance 473
- 24-7 Series-Parallel Reactance and Resistance 475
- 24-8 Real Power 476
- 24-9 AC Meters 477
- 24-10 Wattmeters 478
- 24-11 Summary of Types of Ohms in AC Circuits 479
- 24-12 Summary of Types of Phasors in AC Circuits 479
- Summary 481

**Chapter 25 Complex Numbers for AC Circuits 484**

- 25-1 Positive and Negative Numbers 486
- 25-2 The  $j$  Operator 486

- 25-3 Definition of a Complex Number 487
- 25-4 How Complex Numbers Are Applied to AC Circuits 488
- 25-5 Impedance in Complex Form 488
- 25-6 Operations with Complex Numbers 490
- 25-7 Magnitude and Angle of a Complex Number 491
- 25-8 Polar Form of Complex Numbers 492
- 25-9 Converting Polar to Rectangular Form 494
- 25-10 Complex Numbers in Series AC Circuits 495
- 25-11 Complex Numbers in Parallel AC Circuits 497
- 25-12 Combining Two Complex Branch Impedances 498
- 25-13 Combining Complex Branch Currents 499
- 25-14 Parallel Circuit with Three Complex Branches 499
- Summary 501

**Chapter 26 Network Analysis for AC Circuits 504**

- 26-1 Double-Subscript Notation 506
- 26-2 Kirchhoff's Voltage Law 506
- 26-3 Kirchhoff's Current Law 509
- 26-4 Thevenin's Theorem 512
- 26-5 Norton's Theorem 514
- 26-6 Superposition Theorem 515
- Summary 517

**Review: Chapters 24 to 26 522****Chapter 27 Resonance 524**

- 27-1 The Resonance Effect 526
- 27-2 Series Resonance 526
- 27-3 Parallel Resonance 529
- 27-4 The Resonant Frequency  $f_r = 1/(2\pi\sqrt{LC})$  532
- 27-5 Q Magnification Factor of Resonant Circuit 535
- 27-6 Bandwidth of Resonant Circuit 538
- 27-7 Tuning 540
- 27-8 Mistuning 542
- 27-9 Analysis of Parallel Resonant Circuits 542
- 27-10 Damping of Parallel Resonant Circuits 544
- 27-11 Choosing  $L$  and  $C$  for a Resonant Circuit 545
- Summary 546

**Chapter 28 Filters 550**

- 28-1 Examples of Filtering 552
- 28-2 Direct Current Combined with Alternating Current 552
- 28-3 Transformer Coupling 554
- 28-4 Capacitive Coupling 555
- 28-5 Bypass Capacitors 557
- 28-6 Filter Circuits 559
- 28-7 Low-Pass Filters 560
- 28-8 High-Pass Filters 561

28-9	Resonant Filters	563
28-10	Interference Filters	565
	Summary	566

## **Review: Chapters 27 and 28 570**

## **Chapter 29 Electronic Devices 572**

29-1	Rectifiers, Amplifiers, and Oscillators	574
29-2	Semiconductors	575
29-3	The PN Junction	578
29-4	Semiconductor Diodes	581
29-5	The Bipolar Transistor	583
29-6	Field-Effect Transistor (FET)	585
29-7	Thyristors	588
29-8	Special-Purpose Diodes	590
29-9	Simple Visual Displays	591
29-10	The Cathode-Ray Tube (CRT)	594
29-11	Vacuum Tubes	596
	Summary	601

## **Chapter 30 Transistor Amplifiers 606**

30-1	The Transistor as a Switch	608
30-2	The Transistor as an Amplifier	609
30-3	Transistor Amplifier Circuits	610
30-4	Analysis of the Common-Emitter (CE) Amplifier	613
30-5	Transistor Specifications	615
30-6	Practical Testing and Troubleshooting	618
30-7	Troubleshooting Examples	622
	Summary	623

## **Chapter 31 Digital Electronics 626**

31-1	Binary Numbers	628
31-2	Binary Arithmetic	630
31-3	Basic Logic Gates	631
31-4	Other Logic Gates	633
31-5	Combining Logic Gates	636
31-6	Practical Logic Gates	639
31-7	Practical TTL Gating Circuit	640
31-8	Practical CMOS Gating Circuit	642

31-9	Flip-Flops	644
31-10	Using Flip-Flops	646
31-11	Other Digital Devices	649
31-12	Troubleshooting Digital Circuits	651
	Summary	653

## **Chapter 32 Integrated Circuits 658**

32-1	Types of Integrated Circuits	660
32-2	Production of Integrated Circuits	661
32-3	Integrated Components	662
32-4	Linear IC Applications	665
32-5	Operational Amplifier Circuits	668
32-6	Multivibrators	670
	Summary	671

## **Review: Chapters 29 to 32 674**

## **Appendixes 678**

### **Appendix A Electronic Frequency Spectrum 680**

### **Appendix B FCC Frequency Allocations from 30 kHz to 300,000 MHz 681**

### **Appendix C Alphabetical Listing of the Chemical Elements 682**

### **Appendix D Physics Units 684**

### **Appendix E Trigonometric Functions 688**

### **Appendix F Electrical Symbols and Abbreviations 691**

### **Appendix G Color Codes 693**

### **Appendix H Soldering and Tools 697**

### **Appendix I Schematic Symbols 699**

### **Glossary 706**

### **Bibliography 714**

### **Answers to Self-Examinations 717**

### **Answers to Odd-Numbered Problems 724**

### **Index 731**