

CONTENTS

PREFACE	xxiii
1 INTRODUCTION	1
<i>1-1 Overview of AM, FM, and FM Stereo Receivers</i> 1	
<i>Superheterodyne receivers</i>	<i>1</i>
<i>Amplitude modulation</i>	<i>2</i>
<i>Frequency modulation</i>	<i>4</i>
<i>AM-FM receivers</i>	<i>6</i>
<i>FM stereo</i>	<i>6</i>
<i>Organization of This Text</i> 8	
<i>Looking Ahead</i> 10	
2 POWER SUPPLIES	13
<i>Objectives</i> 13	
<i>2-1 Transformer Fundamentals</i> 13	
<i>Secondary voltage and current</i>	<i>13</i>
<i>Multiple secondaries</i>	<i>14</i>
<i>Power relationships</i>	<i>14</i>
<i>Isolation properties of a transformer</i>	<i>15</i>
<i>2-2 Filament Power Supplies</i> 16	

2-3	Half-Wave Rectifiers	17
	<i>Basic circuit</i>	17
	<i>Filter capacitors</i>	17
	<i>Half-wave rectifier with filter capacitors</i>	19
	<i>Surge current</i>	20
	<i>Vacuum-tube half-wave rectifier</i>	20
	<i>Filament string</i>	21
	<i>Plate circuit</i>	21
	<i>Filter circuit</i>	21
	<i>Effect of ripple</i>	22
2-4	Full-Wave Rectifier Using Center-Tapped Transformer	22
	<i>Vacuum-Tube Full-Wave Rectifier Variation</i>	24
	<i>Use of an inductor as a filter element</i>	25
2-6	Bridge Rectifier	25
2-7	Regulated Power Supplies	26
	<i>Zener regulators</i>	27
	<i>Variation in load current</i>	28
	<i>Pass transistor regulator</i>	29
	<i>Voltage Doublers</i>	30
	<i>Summary</i>	33
	<i>Problems</i>	33
	<i>References</i>	35
3	VACUUM-TUBE AND SOLID-STATE BIASING ARRANGEMENTS	36
	<i>Objectives</i>	36
3-1	Cathode Biasing (Self-Biased) Triode Amplifier	37
	<i>Biasing requirements of vacuum tubes</i>	37
	<i>Plate characteristics of a triode</i>	37
	<i>RC-coupled triode amplifier</i>	38
	<i>Q-point</i>	40
	<i>AC operation</i>	40
	<i>AC load line</i>	41
	<i>Dynamic transfer curve</i>	41
	<i>Degeneration by cathode resistor</i>	42
	<i>Cathode bypass capacitor</i>	43
	<i>Advantages of negative feedback</i>	43

3-2 Contact (Grid Leak)-Biased Triode Amplifier	43
3-3 Biasing Requirements of Bipolar Junction Transistors (BJTs)	44
<i>Biasing the base-emitter junction</i>	45
3-4 Base Bias	46
<i>Signal amplification</i>	47
<i>AC junction resistance</i>	47
<i>Demonstration circuit</i>	49
<i>Input resistance to base</i>	49
<i>Input impedance Z_{in} for base bias</i>	50
<i>Gain formula for base bias</i>	51
<i>Disadvantages of the base-bias circuit</i>	51
3-5 Base Bias with Emitter Feedback (BBEF)	52
<i>Collector-current stability</i>	52
<i>AC characteristics</i>	53
3-6 Base Bias with Collector Feedback (BBCF)	53
<i>Input impedance, Z_{in}</i>	54
<i>Collector-current stability</i>	54
<i>Gain dependence upon AC junction resistance</i>	55
3-7 Base Bias with Collector and Emitter Feedback (BBCEF)	55
3-8 Base Bias with Separate Supply (BBSS)	56
<i>Universal Bias</i>	57
<i>Input impedance</i>	58
<i>Stability of the universal-bias arrangement</i>	59
<i>Modified universal bias</i>	59
<i>Universal Bias with Collector Feedback (UBCF)</i>	60
<i>Emitter Bias with Two Supplies (EBTS)</i>	62
Miscellaneous Topics	63
<i>Biasing PNP transistors</i>	63
<i>Relocation of ground</i>	63
<i>Emitter bypass capacitor</i>	65
<i>Emitter bypass capacitance versus input impedance</i>	67
Junction Field-Effect Transistors (JFETs)	67
<i>Junction FET (JFET)</i>	68
<i>Drain characteristics</i>	71
<i>Channel material</i>	72

<i>DC voltage polarities</i>	73
<i>FET versus BJT biasing</i>	73
JFET Biasing Arrangements	74
<i>Self-bias</i>	74
<i>DC load line for self-biased JFET RC-coupled amplifier</i>	75
<i>Source biasing</i>	75
<i>Voltage-divider bias</i>	76
<i>Modification</i>	77
Insulated Gate FETs—MOSFETs	77
<i>Depletion and enhancement modes</i>	78
<i>Substrate</i>	78
<i>Dual-gate MOSFETs</i>	80
<i>Handling MOSFETs</i>	80
3-16 Biasing Arrangements for MOSFETs	81
<i>Biasing dual-gate MOSFETs</i>	82
<i>Summary</i>	83
<i>Problems</i>	85
<i>References</i>	88
4 AUDIO AND POWER AUDIO AMPLIFIERS	89
<i>Objectives</i>	89
4-1 Cascaded Stages	90
4-2 Direct-Coupled Amplifiers	91
<i>Complementary amplifier</i>	92
<i>DC-stabilized direct-coupled amplifier</i>	93
<i>Darlington pair</i>	94
4-3 Amplifier Configurations	95
<i>Common-base configuration</i>	95
<i>Cathode follower</i>	96
<i>Emitter follower (common collector)</i>	97
4-4 Tube-Type Single-Ended Power Audio Amplifiers	98
<i>Output transformer</i>	98
<i>Plate-to-speaker impedance matching</i>	99
<i>Output circuit operation</i>	100
4-5 BJT Single-Ended Power Audio Amplifiers	100
4-6 Vacuum-Tube Push-Pull Audio Amplifiers	101

<i>Phase inversion by interstage transformer</i>	101
<i>Output transformer core saturation</i>	
<i>Hum rejection</i>	103
4-7 Harmonic Distortion	104
4-8 Phase Inverter	105
4-9 Phase Splitter	106
4-10 Solid State Transformer-Coupled Push-Pull Amplifier	108
<i>Basic circuit</i>	108
<i>Crossover distortion</i>	109
<i>Practical circuit</i>	110
<i>Thermistor</i>	111
<i>Complete audio section</i>	113
4-11 Output Transformer-Less (OTL) Audio Output Stage	113
4-12 Complementary-Symmetry Amplifier	114
<i>Practical circuit</i>	115
4-13 Quasi-Complementary Amplifier	
4-14 Commercial Amplifiers	118
<i>Second commercial amplifier</i>	119
<i>Third commercial amplifier</i>	120
<i>Summary</i>	122
<i>Problems</i>	124
<i>References</i>	125
5 RADIO-FREQUENCY AMPLIFIERS	126
<i>Objectives</i>	126
5-1 Introduction	126
5-2 Resonant Circuits	127
<i>Frequency response</i>	128
<i>Shunt resistance</i>	129
<i>Tuned transformers</i>	131
5-3 Triodes as RF Amplifiers	131
<i>Miller effect</i>	133
<i>Grounded grid RF amplifier</i>	134
5-4 Pentode RF Amplifiers	134
5-5 Gain of Triode and Pentode RF Amplifiers	

5-6	<i>Transistor (BJT) RF Amplifiers</i>	137
	<i>Cutoff frequencies</i>	137
	<i>Typical circuit</i>	137
	<i>Common-base RF amplifier</i>	138
5-7	<i>Automatic Volume Control (AVC)</i>	140
	<i>Bipolar transistor AVC</i>	141
5-8	<i>JFET RF Amplifiers</i>	142
	<i>JFET RF amplifier</i>	142
5-9	<i>MOSFET RF Amplifiers</i>	143
5-10	<i>Dual-Gate MOSFET Amplifiers</i>	144
	<i>AVC for MOSFET amplifiers</i>	144
	<i>MOSFETs versus JFETs and bipolar</i>	145
5-11	<i>Noise</i>	145
	<i>Thermal noise</i>	146
	<i>Shot noise</i>	146
	<i>Partition noise</i>	146
	<i>Flicker noise</i>	147
	<i>Semiconductor resistance noise</i>	147
	<i>Noise spectrum of a transistor</i>	147
	<i>Noise dependence upon bandwidth</i>	148
	<i>Signal/noise ratio</i>	148
	<i>Noise factor</i>	148
	<i>Noise factor of cascaded stages</i>	149
	<i>Effects of noise</i>	149
	<i>Zener regulator noise</i>	151
	<i>Summary</i>	151
	<i>Problems</i>	152
	<i>References</i>	154

6 FREQUENCY CHANGERS

	<i>Objectives</i>	156
6-1	<i>Introduction</i>	156
6-2	<i>Principle of Frequency Changers—Heterodyning</i>	157
6-3	<i>Basic Oscillator Circuits</i>	158
	<i>Resonant circuits as signal sources</i>	158

<i>Simple oscillator</i>	159
<i>Series-fed Hartley oscillator</i>	160
<i>Shunt-fed Colpitts oscillator</i>	161
<i>Transistor versions</i>	162
6-4 Separate Mixer-Oscillator Frequency Changer	163
6-5 Pentagrid Converters	164
<i>Practical circuit</i>	166
<i>Capacitive winding</i>	167
<i>Series-fed Hartley</i>	168
<i>RF amplifier—converter</i>	168
6-6 Bipolar Transistor Converters	168
6-7 Frequency-Changer Considerations	170
<i>Oscillator drift</i>	171
<i>Oscillator pulling</i>	172
<i>Conversion transconductance</i>	172
6-8 Frequency Changers for FM	172
6-9 Automatic Frequency Control (AFC)	173
<i>Reactance Tube</i>	174
<i>FM Frequency Changer with AFC</i>	176
6-11 Voltage-Variable Capacitors (VVC)	178
6-12 FM Converter with VVC Type AFC	179
<i>Summary</i>	180
<i>Problems</i>	182
<i>References</i>	183
PRINCIPLES OF AMPLITUDE MODULATION	184
<i>Objectives</i>	184
7-1 Aspects of Radio Waves	184
<i>Frequency and wavelength</i>	187
<i>Reception of radio waves</i>	187
<i>Field strength</i>	188
<i>Ionospheric effects</i>	188
<i>Atmospheric effects—lightning</i>	189
<i>Antennas for AM receivers</i>	189
7-2 Simple Transmission System	190

7-3	Voice Transmission System	192
7-4	Practical AM Transmitter	194
	<i>Characteristics of an AM signal</i>	196
	<i>AM sidebands</i>	196
	<i>AM power distribution</i>	199
7-5	Tuned Radio-Frequency (TRF) Receivers	199
	Superheterodyne Receivers	200
	<i>Local oscillator radiation</i>	200
	<i>Antenna-local oscillator tracking</i>	201
	<i>Images and spurious responses</i>	201
	<i>IF amplifier</i>	202
	<i>Intermediate frequency selection</i>	202
	Summary	203
	Problems	204
	References	205
8	VACUUM-TUBE RECEIVER ANALYSIS	207
	Objectives	207
8-1	Power Supply	207
	<i>Input circuit</i>	209
	<i>Rectifier and filter</i>	
	<i>Hum-bucking winding</i>	211
8-2	Converter	211
	<i>Oscillator</i>	211
	<i>Output circuit</i>	212
	<i>Converter adjustments</i>	212
8-3	IF Amplifier	213
8-4	Detector	214
	<i>AVC source</i>	215
8-5	First Audio Amplifier	215
8-6	Power Audio Amplifier	
8-7	Current Analysis	216
8-8	Resistance Analysis	217

<i>Receiver with RF Amplifier</i>	218
<i>Power supply</i>	218
<i>RF Amplifier</i>	221
<i>Converter and IF Amplifier</i>	221
<i>Detector—AVC</i>	221
<i>AVC circuit</i>	223
<i>Tone Compensation at the Volume Control</i>	223
8-14 Audio Section	225
<i>Output stage</i>	227
8-15 Decoupling	227
<i>Summary</i>	228
<i>Problems</i>	229
<i>References</i>	231
 9 SOLID-STATE AM RECEIVER ANALYSIS	 232
<i>Objectives</i>	232
9-1 Power Supply	232
<i>B+ circuitry</i>	234
9-2 Direct-coupled, single-ended audio amplifier	235
<i>First AF amplifier</i>	235
<i>Tone compensation</i>	235
<i>Tone control</i>	235
<i>Direct-coupled power amplifier</i>	237
<i>AF signal feedback</i>	237
<i>Output circuit</i>	237
9-3 IF Amplifier, Detector, AVC	239
<i>Detector and AVC</i>	239
<i>First IF amplifier</i>	240
<i>Second IF amplifier</i>	240
9-4 Converter Stage	241
<i>Output circuit</i>	241
9-5 Variation: Bridge Rectifier; Push-Pull Audio	242

<i>Power supply</i>	242
<i>First audio amplifier—driver</i>	
<i>Tone control</i>	244
<i>Audio output stage</i>	244
9-6 Variation: Transformer Power Supply; OTL Push-Pull Audio Amplifier	
<i>Power supply</i>	245
<i>Detector</i>	247
<i>Audio Section</i>	248
9-7 Variation: Complex Power Supply	250
<i>Power supply</i>	252
<i>Converter, IF amplifier, and AF amplifier</i>	253
<i>AF amplifier</i>	255
9-8 Variation: Quasi-Complementary AF AMP with Darlington Pairs	256
<i>Power supply</i>	256
<i>Audio amplifier</i>	256
<i>DC feedback loop</i>	259
<i>AC feedback loop</i>	260
<i>Converter, IF, Detector, AGC</i>	261
<i>Summary</i>	261
<i>Problems</i>	262
10 INTRODUCTION TO TROUBLESHOOTING	265
<i>Objectives</i>	265
10-1 Tools for Electronic Servicing	265
<i>Service data</i>	266
<i>Receiver disassembly</i>	266
<i>Removing and replacing components</i>	267
<i>Soldering and desoldering devices</i>	268
<i>Light sources</i>	268
<i>Alignment tools</i>	269
<i>Chemicals</i>	269
<i>Miscellaneous items</i>	269
<i>Safety</i>	270
10-2 Equipment Considerations	271
<i>VTVM-VOM</i>	271
<i>RF Probe for VTVM</i>	274

<i>Signal generators</i>	274
<i>Component checkers</i>	277
<i>Use of VTVM as a component checker</i>	
<i>Oscilloscope</i>	277
<i>Signal tracer</i>	278
10-3 Failure Mechanisms In Tubes	278
<i>Microphonics</i>	279
<i>Tube sockets</i>	279
10-4 Failure Mechanisms in transistors	280
10-5 Ohmmeter Identification and Testing of BJTs	
<i>Procedure</i>	281
<i>Trick</i>	282
10-6 Choosing Replacements for Defective Parts	
<i>Resistors</i>	283
<i>Control potentiometers</i>	284
<i>Capacitors</i>	285
<i>Temperature coefficient</i>	285
<i>Transformers</i>	285
<i>Solid-state devices</i>	286
10-7 Tips on Replacing Defective Parts	286
<i>Volume controls</i>	286
<i>Top-side exchange</i>	287
<i>Heat sinks</i>	287
<i>Forming leads</i>	288
<i>Broken PC boards</i>	289
<i>Summary</i>	289
<i>Problems</i>	290
<i>Reference</i>	292
11 BASIC TROUBLESHOOTING PROCEDURE	294
<i>Objectives</i>	293
11-1 Basic Troubleshooting Procedure (BTP)	294
<i>Questioning the owner</i>	294
<i>Verify the complaint</i>	294
<i>Sensual examination</i>	295
<i>Isolation procedures</i>	295
<i>Replacement or repair of defective part</i>	

<i>Air check</i>	295
<i>Cleanup</i>	296
Signal Injection	296
<i>Audio section</i>	297
<i>IF amplifier</i>	298
<i>Front end</i>	298
Signal Tracing	301
Voltage-Resistance Analysis	303
<i>Basic circuits</i>	303
<i>V-R analysis of a simple power supply</i>	304
<i>Resistance analysis of leakage on B+ line</i>	305
Voltage-Resistance Analysis of Tube Amplifiers	306
<i>Pentode amplifier</i>	309
Voltage-Resistance Analysis of Transistor Circuits	310
<i>Universal bias with collector feedback</i>	311
<i>Universal bias</i>	313
<i>Base bias with emitter feedback</i>	314
11-7 Generator Coupling to Receiver Test Points	315
<i>Summary</i>	316
<i>Problems</i>	318
12 TROUBLESHOOTING TUBE-TYPE AM RECEIVERS	321
<i>Objectives</i>	321
12-1 Symptom-Function Diagnosis	321
12-2 Filaments Do Not Light	322
12-3 Filaments Light; No Sound From Speaker	324
<i>Low resistance from B+ to ground</i>	326
<i>Audio output troubles</i>	326
12-4 Low-Level 60-Hz Hum from Speaker; No Static with Volume Control at Full Volume	326
<i>IF amplifier problem</i>	329
12-5 Low-Level Hum; Static Present at Full Volume Setting	330
<i>Circuit disturbance</i>	330

12-6	<i>Loud Ripple Hum</i>	332
	<i>Distorted Audio</i>	333
	<i>Micromorphic tubes</i>	337
	<i>Loss of Sensitivity</i>	337
	<i>Standard output</i>	338
	<i>Modulation</i>	338
	<i>Procedure</i>	338
	<i>Unknown generator</i>	342
	<i>No generator</i>	343
12-9	<i>Insufficient Volume with Normal Sensitivity</i>	343
12-10	<i>Receiver Oscillations: Motorboating, Squeals, Howls</i>	345
	<i>Procedure</i>	346
	<i>Microphonic oscillations</i>	346
12-11	<i>Noisy Reception</i>	347
12-12	<i>Intermittent Problems</i>	348
	<i>Mechanical defects</i>	349
	<i>Thermal problems</i>	349
	<i>Special problems</i>	350
12-13	<i>AM Receiver Alignment</i>	350
	<i>General accuracy</i>	352
	<i>Alignment instructions</i>	352
	<i>Typical procedure</i>	352
	<i>Precautions</i>	354
	<i>Summary</i>	354
	<i>Problems</i>	356
13	TROUBLESHOOTING SOLID-STATE AM RECEIVERS	359
	<i>Objectives</i>	359
13-1	<i>Introduction</i>	359
13-2	<i>Dead Receivers</i>	360
13-3	<i>Turn-on Plop Is Present; Little Static</i>	364
13-4	<i>Turn-On Plop with Lots of Static</i>	365
13-5	<i>Loud 60-Hz Hum with Volume Control CCW</i>	367
13-6	<i>Distorted Audio</i>	368

13-7	<i>Loss of Sensitivity</i>	371
13-8	<i>Insufficient Volume, Sensitivity Normal</i>	374
	<i>Oscillations</i>	375
	<i>Noisy Reception</i>	375
	<i>Intermittents</i>	376
13-12	<i>Solid-State AM Receiver Alignment</i>	377
	<i>Summary</i>	378
	<i>Problems</i>	379
14	<i>PRINCIPLES OF FM RECEIVERS</i>	382
	<i>Objectives</i>	382
	<i>Introduction to FM</i>	382
	<i>Noise reduction by amplitude limiting</i>	384
	<i>FM propagation</i>	385
	<i>Antennas for FM</i>	385
	<i>Audio fidelity of FM transmissions</i>	385
	<i>Modulation index</i>	386
	<i>FM Sidebands</i>	386
	<i>Sideband frequencies</i>	387
	<i>Sideband amplitudes</i>	387
	<i>Superheterodyne Receivers for FM</i>	388
14-4	<i>Limiters</i>	391
	<i>Sharp-cutoff pentode limiter</i>	391
	<i>Solid-state limiters</i>	391
14-5	<i>Phasors—Vector Representation of Sine Waves</i>	393
	<i>Phasor addition of sine waves</i>	394
14-6	<i>Foster-Seely Discriminator</i>	396
	<i>Phase relationship of primary and secondary voltages</i>	397
	<i>Phasor addition of primary and secondary voltages, $f_{in} = f_c$</i>	399
	$f_{in} > f_c$	400
	$f_{in} < f_c$	400
	<i>Discriminator operation</i>	400
	<i>Discriminator sensitivity to AM</i>	401

<i>Variation</i>	402
<i>Ratio Detector</i>	402
<i>Ratio-detector response</i>	404
<i>Limiting action of ratio detector</i>	405
<i>Variation</i>	407
<i>Quadrature Detectors</i>	407
<i>Solid-state quadrature detectors</i>	407
<i>Phase-Locked-Loop (PLL) FM Detector</i>	407
14-10 Preemphasis and Deemphasis	410
<i>Summary</i>	411
<i>Problems</i>	413
<i>References</i>	415
15 VACUUM-TUBE AM-FM RECEIVERS	416
<i>Objectives</i>	416
<i>Introduction</i>	416
<i>FM Front End</i>	417
<i>FM RF amplifier</i>	418
<i>FM converter</i>	419
<i>AM Front End and AM-FM IF Sections</i>	421
<i>FM IF and FM detector</i>	421
<i>Ratio detector</i>	421
<i>Function switch</i>	422
<i>AM-FM Front End; Common AM Converter—First FM IF</i>	422
<i>FM RF amplifier</i>	422
<i>FM oscillator and AFC</i>	422
<i>FM mixer</i>	425
<i>AM converter; first FM IF amplifier</i>	425
<i>AM converter</i>	426
<i>AM detector; FM limiter; F-S discriminator</i>	427
<i>AM detector</i>	427
<i>FM limiter</i>	428
<i>Discriminator</i>	428
15-5 Separate Front-End and IF Sections	428
<i>FM RF amplifier and mixer</i>	428

<i>FM oscillator</i>	429
<i>FM IF amplifiers</i>	429
<i>Ratio detector and tuning indicator</i>	431
15-6 Complex IF Coupling	433
<i>AM signal path</i>	433
<i>FM signal path</i>	433
15-7 Stereo Audio Amplifier	435
<i>Volume-balance control</i>	435
<i>Common cathode connection at output stages</i>	436
<i>Function switch</i>	436
15-8 Switch B+ Power Supply	437
<i>Summary</i>	437
<i>Problems</i>	438
<i>References</i>	440
16 SOLID-STATE AM-FM RECEIVERS	441
<i>Objectives</i>	441
16-1 Typical AM-FM Front End	441
<i>FM RF amplifier</i>	443
<i>Complex coupling</i>	444
<i>FM converter</i>	444
16-2 Typical AM-FM IF Section	445
<i>First AM-FM IF amplifier</i>	445
<i>Second IF amplifier</i>	445
<i>AM detector</i>	447
<i>Third FM IF amplifier and ratio detector</i>	447
16-3 Common AM Converter—FM First IF Amplifier	449
<i>FM front end</i>	449
<i>First FM IF amplifier</i>	450
16-4 Complex Coupling in IF Sections	450
<i>Ceramic and crystal filters</i>	452
16-5 Tuning Meter	452
16-6 Switched B+ Power Supply	456
<i>Simple switched power supply</i>	456

<i>An unswitched power supply</i>	456
<i>Full-wave supply with center-tapped transformer</i>	457
Summary	
Problems	
17 TROUBLESHOOTING AM-FM RECEIVERS	462
<i>Objectives</i>	462
17-1 Introduction	462
17-2 AM Normal; No FM	464
17-3 AM or FM; Turn-On Plop (or Hum) Present	470
17-4 AM Normal; Insufficient FM Sensitivity	471
17-5 Oscillations on FM; AM Normal	473
17-6 Distorted Audio on FM; AM Normal	474
17-7 Insufficient AM and FM Sensitivity	474
17-8 Noisy FM; AM Normal	475
17-9 FM Alignment—An Introduction	475
17-10 FM IF Alignment; AM-VTVM Method	476
<i>Discriminator</i>	476
<i>Ratio detector</i>	477
17-11 Sweep/Marker Generator Operation	478
<i>Marker generators</i>	479
17-12 Sweep/Marker FM IF Alignment	481
<i>Discriminator</i>	481
<i>Ratio detector</i>	482
17-13 FM Front-End Alignment	484
Summary	486
Problems	488
18 PRINCIPLES OF FM STEREO	490
<i>Objectives</i>	490
18-1 Compatibility Requirements	490

<i>Subcarrier transmissions</i>	491
<i>SCA</i>	492
<i>Direct approach to FM stereo</i>	492
18-2 <i>(L + R), (L - R) Scheme of Multiplexing</i>	492
<i>Special property of (L + R) and (L - R)</i>	495
18-3 <i>FM-Stereo System</i>	495
<i>Modulation percentages</i>	496
18-4 <i>Simple Balance Modulator</i>	497
<i>AM waveform restoration</i>	499
18-5 <i>Frequency Doublers</i>	499
18-6 <i>Composite FM-Stereo Signal</i>	501
<i>Second example</i>	502
<i>Transmitter block diagram</i>	502
18-7 <i>Matrix Decoder Principles</i>	505
<i>Separation control</i>	507
18-8 <i>Time-Division (TD) Decoding</i>	507
<i>Diode voltages</i>	508
<i>Illustration</i>	509
18-9 <i>Qualitative Description of TD Decoding</i>	513
<i>Credibility</i>	513
<i>Graphical construction of the composite waveform</i>	516
<i>Block Diagram of a Typical FM-Stereo Receiver</i>	516
<i>Summary</i>	516
<i>Problems</i>	518
19 <i>FM-STEREO DECODER CIRCUIT ANALYSIS</i>	521
<i>Objectives</i>	521
19-1 <i>Typical Matrix Decoder</i>	521
<i>Input amplifier and cathode follower</i>	523
<i>19-KHz oscillator-doubler</i>	523
<i>Two-phase detector and matrix</i>	524
<i>FM/FM stereo switching</i>	524
19-2 <i>Matrix-Decoder Variation</i>	524

<i>Signal separation</i>	524
<i>19-KHz oscillator-doubler</i>	526
<i>Single-phase detector</i>	526
<i>Standard Time-Division Multiplex Decoder</i>	526
<i>MPX input amplifier and signal separation</i>	526
<i>19-KHz amplifier and doubler</i>	528
<i>Decoder circuit</i>	528
<i>Stereo indicator</i>	528
<i>Mono-stereo switch</i>	529
<i>Bridge-Type Time-Division Decoder</i>	529
<i>Composite amplifier</i>	529
<i>Doubler, 38-KHz AMP, and indicator control</i>	531
<i>Bridge MPX detector</i>	531
<i>Correction</i>	533
<i>FM/FM stereo function switch</i>	533
19-5 <i>Bipolar Detector</i>	534
<i>FM monaural signal path</i>	536
<i>Typical circuit</i>	536
19-6 <i>Integrated-Circuit Time-Division Decoder</i>	537
19-7 <i>Phase-Locked-Loop Decoder Principles</i>	539
<i>PLL decoder</i>	540
19-8 <i>AM, FM, FM-Stereo Receiver</i>	541
<i>FM limiter/decoder, mute source</i>	543
<i>Mute amplifier</i>	543
<i>Mute buffer</i>	543
<i>PLL stereo decoder</i>	543
<i>AM section</i>	544
<i>Summary</i>	544
<i>Problems</i>	545
20 <i>TROUBLESHOOTING FM-STEREO RECEIVERS</i>	548
<i>Objectives</i>	548
<i>Introduction</i>	548
<i>One Channel Inoperative on All Functions</i>	549
<i>Troubleshooting IC stages</i>	549

<i>AM Normal; FM and FM Stereo Inoperative</i>	550
<i>Precaution</i>	553
20-4 One Channel Inoperative in FM-Stereo Code	554
20-5 Monaural FM Stereo	554
20-6 Nonfunctioning Stereo Indicator	558
20-7 Stereo-Decoder Alignment—An Introduction	558
<i>Matrix-Decoder Alignment</i>	559
<i>Matrix-decoder alignment without stereo generator</i>	560
<i>Time-Division-Decoder Alignment</i>	562
<i>Time-division-decoder alignment without a stereo generator</i>	563
<i>PLL-Decoder Alignment</i>	563
<i>Summary</i>	565
<i>Problems</i>	566
INDEX	577