

CONTENTS

	Page
1. Introduction	1
2. Static Fields	4
2.1 The electric field	4
2.2 The magnetic field	5
2.3 The D and H vectors	7
2.4 Flux and flux density	8
2.5 Voltage	8
2.6 Gauss's law	10
2.7 Ampere's law	11
2.8 Differential forms	12
2.9 Ohm's law	13
2.10 Poisson's and Laplace's equations	13
2.11 Magnetic vector potential	15
2.12 Forces	16
2.13 Summary	18
Examples	18
3. Changing Fields	27
3.1 Faraday's law and e.m.f.	27
3.2 Continuity and displacement current	30
3.3 Maxwell's equations	32
3.4 Capacitance	32
3.5 Inductance	33
3.6 The calculation of capacitance and inductance	37
3.7 Duality of field patterns	39
3.8 Discontinuities	40
3.9 Energy	44
Examples	46
4. Circuit Properties	55
4.1 Circuit parameters	55
4.2 Kirchhoff's laws	57
4.3 Sinusoidal waveforms	59
4.4 The Argand diagram	62
4.5 Impedance and admittance	63
4.6 Generalized impedance and admittance	68
4.7 Current and voltage generators	70
4.8 Non-sinusoidal waveforms	72
4.9 Energy flow	77
4.10 Three-phase circuits	84
Examples	90
5. Circuit Analysis	97
5.1 Network equations	97
5.2 Thevenin's and Norton's theorems	103
5.3 Reciprocity and superposition	104
5.4 Connexion transformations	105
5.5 Networks with mutual inductance	106
5.6 Coupled circuits	109
5.7 The transformer	111
5.8 Frequency response	117

5.9	Transient solutions	128
5.10	Poles and zeros	135
	Examples	139
6.	Materials	148
6.1	The solid state	148
6.2	Electrical conductors	152
6.3	Semiconductors	154
6.4	The p-n junction	155
6.5	The emission of electrons from a surface	156
6.6	Dielectrics	158
6.7	Magnetic materials	162
6.8	The Hall effect	166
6.9	Gaseous conduction	168
	Examples	169
7.	Magnetic Circuits	172
7.1	Reluctance and permeance	172
7.2	Circuits with gaps	176
7.3	Permanent magnets	176
7.4	Rotating machine circuits	177
7.5	Magnetic gap force	178
7.6	Eddy currents	179
	Examples	181
8.	Electromechanics	186
8.1	Force and torque	186
8.2	Electrical machines	189
8.3	Field patterns	190
8.4	The reluctance machine	195
8.5	The generation of e.m.f.	197
8.6	Commutation	201
8.7	Direct-current machines	203
8.8	The polyphase synchronous machine	210
8.9	The polyphase induction machine	218
8.10	Other machines	225
	Examples	226
9.	Electronic Amplification	234
9.1	General	234
9.2	The thermionic triode valve	234
9.3	The equivalent circuit for small signals	237
9.4	The basic triode amplifier	239
9.5	Tetrodes and pentodes	242
9.6	The transistor	243
9.7	The common-base transistor amplifier	246
9.8	The common-emitter transistor amplifier	250
9.9	Hybrid parameters	252
9.10	The common-collector and cathode-follower circuits	253
9.11	Bias	255
9.12	Coupling	259
9.13	Frequency response	261
9.14	Gain and bandwidth	265
9.15	Power in amplifiers	267
9.16	Amplifier types and classification	269
	Examples	272
10.	Circuits with Feedback	283
10.1	General	283
10.2	Negative feedback	284

10.3	Operational amplifiers	287
10.4	The general case of feedback	289
10.5	The Nyquist criterion	291
10.6	The root locus	294
10.7	Oscillators	295
10.8	Pulse circuits	300
	Examples	302
11.	Transmission and Propagation	310
11.1	Distributed circuits	310
11.2	Travelling waves	312
11.3	Reflection	315
11.4	Line impedance	318
11.5	The propagation constant	320
11.6	Standing waves	321
11.7	The transmission line as a two-port; network chains	324
11.8	Propagation	327
11.9	Skin depth	327
11.10	The Poynting vector	329
11.11	Radiation	330
	Examples	331
Index		363