

## CONTENTS

	Page
<b>1. INTRODUCTION</b>	<b>1</b>
1. On Studying Electric Circuits	1
2. Energy	2
3. The Nature of Electricity	2
4. The Free Electron	5
5. The mks System of Units	8
6. Conversion of Units	11
<b>2. CURRENT AND VOLTAGE</b>	<b>14</b>
1. Hydraulic Analogy	14
2. Conductors and Insulators	14
3. Quantity of the Electric Medium	16
4. Flow of the Electric Medium	17
5. Electron Velocity	18
6. Electric Pressure	20
7. Batteries	21
8. The Volt	27
9. Electromotive Force and Voltage Drop	28
10. Conventional Current Direction	30
<b>3. RESISTANCE</b>	<b>35</b>
1. Ohm's Law of Constant Proportionality	35
2. The Nature of Resistance	36
3. Factors Governing the Resistance of Metallic Conductors	38
4. Specific Resistance or Resistivity	39
5. Wire Tables	42
6. Effect of Temperature on Resistance	45
7. Temperature Coefficient of Resistance	47
8. Nonlinear Resistors	49
9. Some Other Consequences of Ohm's Law	52
<b>4. WORK AND POWER</b>	<b>55</b>
1. Energy and Work	55
2. The Joule	56
3. Efficiency	57
4. Power	58
5. The Horsepower	60
6. The Kilowatt-hour	61
7. Interrelationship of Basic Electrical Units	62
<b>5. SERIES AND PARALLEL RESISTANCES</b>	<b>68</b>
1. Resistances in Series	68
2. Kirchhoff's Voltage Law	70
3. Characteristics of Series Circuits	70
4. Internal Resistance	72
5. Maximum Power Transfer	73
6. Resistances in Parallel-Kirchhoff's Current Law	75
7. Conductance	76
8. Conductivity	78
9. Characteristics of Parallel Circuits	78
10. Series-Parallel Circuits	79

11. Voltage Dividers	83
<b>6. RESISTANCE NETWORKS</b>	<b>92</b>
1. Networks With More Than One Source of emf	92
2. The Superposition Theorem	94
3. Thevenin's Theorem	96
4. Norton's Theorem	100
5. Delta-Wye Transformation	101
6. The Wheatstone Bridge	102
<b>7. MAGNETIC CIRCUITS</b>	<b>109</b>
1. Magnetism and Electricity	109
2. The Nature of a Magnetic Field	109
3. The Characteristics of Magnetic Lines of Force	111
4. Magnetic Field Around a Current-Carrying Conductor	113
5. Magnetic Flux	116
6. Magnetomotive Force	117
7. Reluctance	117
8. Permeability	118
9. Flux Density and Magnetizing Force	119
10. Diamagnetic and Paramagnetic Materials	120
11. Ferromagnetic Materials	121
12. Magnetization Curves	122
13. Permeability from the BH Curve	125
14. Hysteresis	128
15. Eddy Current	130
16. Magnetic Shielding	131
17. Practical Magnetic Circuits	132
18. Long Air-Core Coils	133
19. Simple Magnetic Circuit	134
20. Leakage Flux	137
21. Series Magnetic Circuits	138
22. Air Gaps	140
23. Parallel Magnetic Circuits	142
24. Tractive Force of an Electromagnet	143
<b>8. ELECTRICAL MEASUREMENT</b>	<b>150</b>
1. Mechanical Torque from Electric Current	150
2. The Ammeter	154
3. The Voltmeter	158
4. Resistance measurements	160
5. The Moving Iron Movement	164
6. The Electro-Dynamometer Movement	166
<b>9. INDUCTANCE</b>	<b>173</b>
1. Electromagnetic Induction	173
2. Faraday's Law	175
3. Lenz's Law	175
4. Self-Induction	177
5. Self-Inductance	177
6. Factors Governing Inductance	178
7. Rise of Current in a Pure Inductance	181
8. Rise of Current a Practical Inductance	184
9. Time Constant	187
10. Graphical Solution for Instantaneous Current	189
11. Algebraic Solution for Instantaneous Current	192
12. Energy stored by an Inductance	194
13. Fall of Current in an Inductive Circuit	197
14. Characteristics of Inductive d-c Circuits	201

<b>10. CAPACITANCE</b>	<b>206</b>
1. Static Electricity	206
2. The Nature of an Electric Field	208
3. Electrostatic Induction	212
4. Dielectrics	212
5. Capacitance	214
6. Factors Governing Capacitance	217
7. Charging a Capacitor	223
8. Time Constant	225
9. Graphical Solution for Instantaneous Potential Difference	227
10. Discharging a Capacitor	229
11. Algebraic solution of Instantaneous Potential Differences	232
12. Energy Stored by a Capacitor	234
13. Characteristics of Capacitance in d-c Circuits	236
<b>11. ALTERNATING CURRENT</b>	<b>243</b>
1. A Simple Rotating Generator	243
2. The Nature of the Induced emf	244
3. The Sine Wave	246
4. The Peak Value of a Sine Wave	250
5. The Instantaneous Value of a Sine Wave	250
6. The Radian	254
7. Instantaneous Current in a Resistance	255
8. Instantaneous Power in a Resistance	257
9. The Effective Value of a Sine Wave	258
10. Average Voltage and Current	261
<b>12. REACTANCE</b>	<b>264</b>
1. Nature of the Instantaneous Current in an Inductance	265
2. Inductive Reactance	267
3. Factors Governing Inductive Reactance	268
4. Nature of the Instantaneous Current in a Capacitance	269
5. Capacitive Reactance	271
6. Factors Governing Capacitive Reactance	272
7. Resistance, Inductive Reactance, and Capacitive Reactance	273
<b>13. VECTOR ALGEBRA</b>	<b>276</b>
1. Addition of sine Waves	276
2. Addition of Instantaneous Values on a Linear Graph	277
3. Representing a Sine Wave by a Vector	280
4. Vector Addition by Geometrical Construction	281
5. Addition of Vectors Which Are at Right Angles	282
6. Expressing a Vector Quantity in Rectangular Coordinates	284
7. Vector Addition by Rectangular Coordinates	288
8. Subtraction of Vector Quantities	289
9. Multiplication and Division of Vector Quantities	290
<b>14. IMPEDANCE</b>	<b>294</b>
1. Resistance and Inductance in Series	294
2. Impedance	296
3. Practical Inductors	298
4. Resistance and Capacitance in Series	301
5. Resistance, Inductance, and Capacitance in Series	302
6. Resistance, Inductance, and Capacitance in Parallel	304
7. Conductance, Susceptance, and Admittance	306
<b>15. POWER IN ALTERNATING CURRENT CIRCUITS</b>	<b>312</b>
1. Power in a Pure Resistance	312
2. Power in a Pure Inductance	313
3. Power in a Pure Capacitance	315

4.	Power in a circuit Containing Resistance and Reactance	316
5.	The Power Triangle	318
6.	Power Factor	321
7.	Power Factor Correction	324
8.	Measuring Power in an a-c Circuit	329
9.	Effective Resistance	330
<b>16.</b>	<b>IMPEDANCE NETWORKS</b>	<b>335</b>
1.	Impedances in Series	335
2.	Impedances in Parallel	336
3.	Equivalent Circuits	338
4.	Kirchhoff's Laws	341
5.	The Superposition Theorem	343
6.	Thevenin's Theorem	345
7.	Delta-Wye Transformation	346
8.	Alternating Current Bridges	348
9.	Circle Diagrams	351
<b>17.</b>	<b>RESONANCE</b>	<b>359</b>
1.	Effect of Varying Frequency in a Series RLC Circuit	359
2.	Series Resonance	361
3.	Q of Resonant Circuits	363
4.	Resonant Rise of Voltage	365
5.	Selectivity	367
6.	The Theoretical Parallel Resonant Circuit	368
7.	Practical Parallel Resonant Circuits	370
8.	Filter Networks	374
<b>18.</b>	<b>TRANSFORMER ACTION AND MUTUAL INDUCTANCE</b>	<b>379</b>
1.	Mutual Induction	379
2.	Transformer Action	379
3.	Transformation Ratio	381
4.	Leakage Reactance	383
5.	The Open-Circuit and Short - Circuit Tests	385
6.	Effect of Loading a Transformer	386
7.	Audio Transformers	388
8.	Coefficient of Coupling	389
9.	Mutual Inductance	390
10.	Coupled Impedance	392
11.	Tuned Transformers	394
<b>19.</b>	<b>THREE-PHASE SYSTEMS</b>	<b>401</b>
1.	Advantages of Polyphase System	401
2.	Generation of a Three-Phase emf	405
3.	Double Subscript Notation	407
4.	The Four-Wire Wye Connected System	408
5.	The Delta Connected System	412
6.	The Wye-Delta System	417
7.	Power in a Balanced Three-Phase System	420
8.	Measuring Power in a Three-Phase System	421
9.	Two-Wattmeter Measurement of Three-Phase Power	423
10.	Phase Sequence	427
11.	Unbalanced Three-Wire Wye Loads	430
<b>20.</b>	<b>HARMONICS</b>	<b>439</b>
1.	Nonsinusoidal Waves	439
2.	Addition of Harmonically Related sine Waves	440
3.	Generation of Harmonics	444
4.	Generation of Harmonics in a Vacuum Tube Amplifier	445
5.	Generation of Harmonics in an Iron-Core Transformer	447

6. Effective Value of a Nonsinusoidal Wave	449
7. Square Waves and Sawtooth Waves	451
8. Nonsinusoidal Waves in Linear Impedance Networks	452

<b>INDEX</b>	<b>469</b>
--------------	------------