

## CONTENTS

	Page
<b>1. INTRODUCTORY CONCEPTS</b>	<b>2</b>
1-1 SI Units	2
1-2 Scientific Notation	6
1-3 Prefixes	8
1-4 Resolution and Rounding	10
1-5 The structure of Matter	13
1-6 The Nature of Electricity	16
Summary	23
 <b>2. ELECTRIC CIRCUITS AND QUANTITIES</b>	 <b>28</b>
2-1 Circuits and Diagrams	28
2-2 Electric Current Flow	32
2-3 Measuring Current	36
2-4 Electric Potential	40
2-5 Resistance and Ohm's Law	43
2-6 Measuring Voltage and Resistance	45
Summary	49
 <b>3. POWER AND ENERGY</b>	 <b>54</b>
3-1 Power	54
3-2 Energy	58
3-3 Efficiency	60
3-4 Energy Sources	61
3-5 Protective Devices	63
Summary	67
 <b>4. ELECTRICAL MATERIALS</b>	 <b>70</b>
4-1 Characteristics	70
4-2 Resistivity	74
4-3 Temperature Coefficient	79
4-4 Wire and Cable	81
4-5 Connections and Connectors	85
Summary	88
 <b>5. RESISTIVE COMPONENTS</b>	 <b>92</b>
5-1 Fixed Resistors	92
5-2 Resistor Color Code	97
5-3 Variable Resistors	99
5-4 Other Resistive Devices	102
Summary	106
 <b>6. SERIES CIRCUITS</b>	 <b>110</b>
6-1 Current in a Series Circuit	110
6-2 Kirchhoff's Voltage Law	113
6-3 Voltage Dividers	117
6-4 Applications of Series Circuit Concepts	121
6-5 Fault Analysis in Series Circuits	125
Summary	129
 <b>7. PARALLEL CIRCUITS</b>	 <b>134</b>
7-1 Voltage and Current in Parallel Circuits	134

7-2	Conductance	139
7-3	The Current Divider Rule	143
7-4	Applications of Parallel Circuit Concepts	145
7-5	Fault Analysis in Parallel Circuits	148
	Summary	151
<b>8.</b>	<b> SERIES-PARALLEL CIRCUITS</b>	<b>156</b>
8-1	Applying Laws to Series-Parallel Circuits	156
8-2	Analysis of Series-Parallel Circuits by Reduction	160
8-3	Applications of Series-Parallel Circuits	165
8-4	Fault Analysis in Series-Parallel Circuits	170
	Summary	173
<b>9.</b>	<b> NETWORK ANALYSIS</b>	<b>178</b>
9-1	Current Sources	178
9-2	Determinants	182
9-3	Branch Analysis	185
9-4	Mesh analysis	188
9-5	Nodal Analysis	190
9-6	Superposition	193
9-7	Thevenin's Theorem	196
9-8	Norton's Theorem	200
9-9	Millman's theorem	203
9-10	Power Transfer and Network Transforms	206
	Summary	212
<b>10.</b>	<b> MAGNETISM</b>	<b>218</b>
10-1	Magnetic Fields	218
10-2	Electromagnetism	222
10-3	Magnetic Units	224
10-4	Magnetization Curves	228
10-5	Magnetic Circuits	232
10-6	Applications	238
	Summary	242
<b>11.</b>	<b> ELECTRIC ENERGY SOURCES</b>	<b>248</b>
11-1	Electromagnetic Induction and Generators	248
11-2	Primary Cells and Batteries	254
11-3	Secondary Cells and Batteries	259
11-4	Other Electric Sources	264
	Summary	268
<b>12.</b>	<b> ALTERNATING CURRENT</b>	<b>274</b>
12-1	The Sine Wave	274
12-2	Frequency and Phase	278
12-3	Phasors	281
12-4	Resistive Circuits	284
12-5	Electronic Function Generators	287
	Summary	289
<b>13.</b>	<b> INDUCTANCE</b>	<b>294</b>
13-1	Induction	294
13-2	Self-Induction	297
13-3	Types of Inductors	300
13-4	Series Inductors and Parallel Inductors	304
	Summary	306
<b>14.</b>	<b> INDUCTORS IN DC AND AC CIRCUITS</b>	<b>310</b>
14-1	Energy Stored in an Inductor	310
14-2	Current Rise in Inductive Circuits	313

14-3	Time Constants for Rising Currents	314
14-4	Current Fall in Inductive Circuits	317
14-5	Inductor Action in an AC circuit	320
14-6	Inductive Reactance	322
14-7	Inductive Reactance in Series and Parallel	324
14-8	Quality Factor	325
14-9	Measuring Inductance	328
	Summary	330
<b>15.</b>	<b>CAPACITANCE</b>	<b>336</b>
15-1	Electric Fields	336
15-2	Dielectrics	339
15-3	Capacitance and Capacitors	341
15-4	Factors Affecting Capacitance	343
15-5	Energy Storage	345
15-6	Characteristics of Capacitors	346
15-7	Types of Capacitors	347
15-8	Stray Capacitance	352
15-9	Indicating Capacitance	352
15-10	Series, Parallel, and Series-Parallel Capacitors	353
	Summary	356
<b>16.</b>	<b>CAPACITORS IN AND AC CIRCUITS</b>	<b>362</b>
16-1	Controlled Charging and Discharging	362
16-2	Time Constant	365
16-3	Capacitor Action in an AC Circuit	369
16-4	Phase Angle and Power	370
16-5	Capacitive Reactance	371
16-6	Capacitive Reactances in Series and Parallel	373
16-7	Capacitor Dissipation Factor	374
16-8	Measuring Capacitance	376
	Summary	377
<b>17.</b>	<b>RCL CIRCUITS</b>	<b>382</b>
17-1	Series RC Circuits	382
17-2	Series RL Circuits	388
17-3	Series RCL Circuits	389
17-4	Parallel RC Circuits	390
17-5	Parallel RL Circuits	393
17-6	Parallel RCL Circuits	394
17-7	Response to Pulses	395
	Summary	401
<b>18.</b>	<b>RESONANCE AND FILTERS</b>	<b>406</b>
18-1	Series-Resonant Circuits	406
18-2	Ideal Parallel-Resonant Circuits	415
18-3	Practical Parallel LC Circuits	418
18-4	Gain, Attenuation, and the Decibel	420
18-5	Filters	422
	Summary	430
<b>19.</b>	<b>AC NETWORK ANALYSIS</b>	<b>436</b>
19-1	The $j$ Operator	436
19-2	Rectangular and Polar Notation	438
19-3	Rectangular-to-Polar Conversion	440
19-4	Polar-to-Rectangular Conversion	440
19-5	Phasor Algebra	441
19-6	Conductance, Susceptance, and Admittance	443
19-7	Series and parallel Impedances	445
19-8	Equivalent Series and Parallel Impedances	448

19-9 Thevenin's and Norton's Theorems	449
Summary	452
<b>20. TRANSFORMERS</b>	<b>456</b>
20-1 Mutual Inductance and Coupling	456
20-2 Basic Transformer Action	459
20-3 Ideal Iron-Core Transformer	460
20-4 Real Iron-Core Transformers	466
20-5 Measuring Core and Copper Losses	469
20-6 Equivalent Circuits	470
20-7 Multiple and Tapped Windings	473
20-8 Types of Transformers	476
Summary	478
<b>21. MEASUREING INSTRUMENTS</b>	<b>484</b>
21-1 Meter Specifications	484
21-2 Meter Loading	487
21-3 Digital Meter	491
21-4 Analog Meter	493
21-5 Cathode - Ray Oscilloscopes	498
21-6 Oscilloscope Measurements	506
21-7 Oscilloscope Probes and Circuit Loading	511
Summary	513
<b>22. THREE-PHASE CIRCUITS</b>	<b>520</b>
22-1 Reference Point and Subscripts	520
22-2 Three-Phase Generation	522
22-3 The Wye Connection	524
22-4 The Delta Connection	526
22-5 Wye-Delta and Delta-Wye Systems	528
22-6 Three-Phase transformer Connections	529
22-7 Calculating Power in Three-Phase Systems	530
22-8 Types of Power and Power Factor	532
22-9 Measuring AC Power	535
22-10 Advantages of Three-Phase Systems	538
Summary	540
<b>23. INTRODUCTION TO DISCRETE ELECTRONICS</b>	<b>544</b>
23-1 Semiconductor Materials	544
23-2 PN Junction	549
23-3 Diodes	552
23-4 Rectification	558
23-5 Filters	563
23-6 Zener Regulator	571
Summary	573
<b>24. ELECTRONIC AMPLIFICATION</b>	<b>580</b>
24-1 Bipolar Transistor	580
24-2 Transistor Amplifiers	588
24-3 Common-Emitter Amplifier No.1	590
24-4 Common-Emitter Amplifier No.2	659
24-5 Negative Feedback	600
24-6 Voltage Amplifiers	601
24-7 Dual-Supply Amplifier Circuits	602
24-8 Other Circuit Configurations	603
24-9 Field-Effect Transistors	605
Summary	611
<b>25. INTEGRATED CIRCUITS AND OPERATIONAL AMPLIFIERS</b>	<b>618</b>
25-1 Integrated Circuits	618

25-2 Fabricating Monolithic ICs	620
25-3 Fabricating Hybrid ICs	625
25-4 Integrated Component Characteristics	626
25-5 The Differential Amplifier	627
25-6 The Operational Amplifier	637
25-7 Operational Amplifier Circuits	641
Summary	647
<b>26. INTRODUCTION TO DIGITAL CIRCUITS</b>	<b>654</b>
26-1 A Little Terminology	655
26-2 Binary Numbers	656
26-3 Decision-Making Gates	659
26-4 Combinational Logic	668
26-5 Sequential Logic	676
26-6 Arithmetic Circuits	687
26-7 Memory Circuits	688
26-8 Microcomputer Systems	691
Summary	692
<b>INDEX</b>	<b>717</b>