

681.2 BRO

CONTENTS

1. Shackless continuity tester	9
2. A tester's sinewave generator	10
3. Household handy wattmeter	12
4. Novel VOM range expandel	13
5. Dry cell rejuvenator	14
6. Transistor variable power supply	16
7. Homemade RF probe	18
8. Inexpensive impedance checker	20
9. Experimenter 's power supply	22
10. Ham's RF meter	24
11. Line – voltage booster	26
12. Transistorized moisturemeter	28
13. Neon lamp tone generator	30
14. Dynamic mike for testing	32
15. Transistor experimenter's power supply	34
16. One – tube frequency standard	36
17. Crystal microphone substitute	38
18. Electronic timer	40
19. Intermediate frequency checker	42
20. Simple astable multivibrator	44
21. Ham 's audio oscillator	46
22. VOM RF indicator	48
23. High – voltage silicon rectifier checker	50
24. Diode RF probe	52
25. One – transistor CB field strength meter	54
26. Dial – a – volt miniature power supply	56
27. Two – transistor sine – wave generator	58
28. Sound level meter	60
29. The \$1.50 signal generator	62
30. Audio frequency meter	64
31. Frequency meter / monitor	66
32. Inexpensive meter sensitizer	68
33. Deluxe transistor signal tracer	70
34. Tubeless, transistoriess light meter	72
35. Simple short detector	74
36. Transistor frequency standard	76

37. Neon – lamp signal tracer	78
38. Miniature voltmeter	80
39. AC – DC voltmeter	82
40. A small multimeter	84
41. Radio frequency calibrator	86
42. All – around multimeter	88
43. Junk – box capacitor tester	90
44. Flashlight battery rejuvenator	92
45. Multipurpose comparator	94
46. Transistor checker	96
47. Add a signal – strength meter	98
48. Radio – TV tube rejuvenator	100
49. One – transistor signal tracer	102
50. Handy fuse saver	104
51. Professional dual – meter transistor checker	106
52. Low – voltage silicon rectifier tester	108
53. Transistor metronome	110
54. Flashlight cell tester / charger	112
55. Filament – type tube tester	114
56. Diode frequency meter	116
57. Miniature VOM	118
58. Capacitor leakage checker	120
59. World’s simplest SCR checker	122
60. VOM Used to indicate RF	124
61. Inexpensive 40 – 13,000 audio oscillator	126
62. Shop interference filter	128
63. Variable output transistorized power supply	130
64. Inexpensive photo relay	132
65. Footswitch unit controller	134
66. 100 KHZ receiver calibrator	136
67. High – frequency oscillator	138
68. Automatic tool magnetizer	140
69. Handy vibrator rejuvenator	142
70. Diode – type CB field strength meter	144
71. Simple audio tracer	146
72. Transistorized square – wave generator	148
73. Transistor signal – injector probe	150
74. DC motor supply unit	152
75. Neon – lamp polarity tester	154
76. 108 MHz receiver calibrator	156

77. Filament transformer power supply	158
78. Blown – fuse indicator	160
79. TV picture tube rejuvenator	162
80. Versatile crystal oscillator	164
81. Two – transistor signal generator	166
82. One – transistor dip meter	168
83. RF meter	170
84. One – tube CB Q – multiplier	172
85. In – circuit transistor tester	174
86. Radiation finder	176
87. Universal two – way radio tester	178
88. Tubeless variable frequency oscillator	180
89. Simple signal tracer	182
90. Variable bench – voltage supply	184
91. Transistorized injector probe	186
92. Grid dipper modulator	188
93. Simple phase – shift oscillator	190
94. One – tube signal injector	192
95. Direct current controller	193
96. Versatile \$1.99 tester	194
97. Metal locator	196
98. Capacitor tester for VOM ‘s	198
99. High – voltage converter for your battery	200
100. Antenna current indicator	202
101. Universal test speaker	204
Appendix A Substitution guide	206
Appendix B Resistor color codes	207
Appendix C Capacitor color codes	208
Index	210