

INDEX

- A**bsorption wave meter, 623
 Air coaxial line, 483
 Altitude determination, 667
 Amplifier circuits, electron tube, 207-254
 Amplifiers
 audio power, 256-291
 buffer, 405
 circuits, electron tube, 207-254
 class-A triode, 257-274
 classification of, 161-174
 classified according to
 circuit configuration, 171
 condition of operation (bias), 165
 frequency, 170
 resonant quality of load, 174
 d-c, 207-211
 distortion in, 174-180
 electron-tube; introduction to, 161-205
 feedback, 211-219
 intermediate-frequency, 564, 572, 591
 paraphrase, 251-254
 power, 163, 164, 281, 408-413, 454
 push-pull power, 274-284
 r-f, 564
 transformer-coupled push-pull, 275-277
 tuned, 174, 219-235
 video, 235-241
 Amplitude modulation, 398, 550
 Antennas, 509-534
 and propagation, 509-547
 basic principles, 517-525
 coupling, 533
 half-wave; radiation pattern for, 530
- Antennas—Continued
 Hertz, 525
 Marconi, 528
 system, radar, 673
 transmitting and receiving, 682
 tuning, 529
 types, basic, 525-529
 Audio power amplifiers. *See above*
- B**andwidth requirements, 340
Basic Electronics (this book), 1-3
 introduction, 1-3
 Bias methods in receivers, 413-416
 B-voltage supplies, 97-142
- C**apacitance, interelectrode, 69
 Capacitance-inductance-resistance bridges, 637-639
 Capacitors, neutralizing, 70
- C**athode
 followers, 241-248, 689
 heating power, 95-97
 Cathode-ray oscilloscope, 603-618
 Cathode-ray tubes, 89-91
- C**ircuits
 clamping, 688
 electron-tube amplifier, 207-254
 filter, 116-126
 for tube tests, 639
 of a-m radiotelephone transmitter, 445
 of c-w transmitter, 430
 of f-m
 radiotelephone transmitter, 450
 tuner, 598
 of superheterodyne receiver, 584
 of t-r-f receiver, 560
 oscilloscope, 610-615

- Circuits—Continued
 parallel-resonant, 25
 reshaping, 688
 resistance-capacitance coupled, 236
 series resonant, 13
 tuned, 1-46
 voltage divider, 138
 voltage-multiplying, 142-146
- Closed-end transmission line, 470, 475
- Color coding and symbols, electronic, 713
- Communications
 receivers, elementary, 550-601
 introduction, 550
 U-H-F, 544
 V-H-F, 544
- Compensation
 high-frequency, 237
 low-frequency, 239
- Complex numbers, 10
- Continuous-wave method, radar, 657
- Control
 automatic gain, 577, 579
 brightness, 605
- Coupling
 direct, 203
 double-tuned transformer; analysis, 224-234
 impedance, 195
 methods, 181-205
 resistance-capacitance, 184-195
 single-tuned
 r-c; analysis, 220
 transformer; analysis, 223
 transformer-coupled stage of amplification, 196
- Current and voltage ratios, 285
- Decibel, 284-291
- Demodulation, 337, 368-394
 of amplitude-modulated waves, 368-387
 of frequency-modulated waves, 387-394
- Detection. *See* Demodulation.
- Detectors
 a-m, 372-387
 diode, 373
 discriminator, 388, 597
 first, 569
 f-m, 387-394
 for t-r-f receiver, 555
 grid-leak, 377
 heterodyne, 385
 plate, 381
 ratio, 389
 regenerative, 383
 second, 575
 slope, 387
- Diodes, 55-60
 gas, 86
- Direct coupling, 203
- Direct current amplifiers, 207-211
- Discriminator, 388, 597
- Distortion
 caused by limiting, 246
 frequency, 175
 in amplifiers, 174-180
 of amplitude, 67, 177
 miscellaneous, 179
 phase, 175
 second-harmonic, 266-269
- Double-tuned transformer coupling, 224-234
- Dynamotors, 151
- Earphones, 558
- Edison effect, 56, 57
- Electromechanical systems, 151-158
- Electronic
 color coding and symbols, 713
 switching, 619-622, 689
 test equipment, 603-650
- Electron-tube
 amplifier circuits, 207-254

- Electron-tube—Continued
 - materials; physical characteristics of, 53-55
 - operating principles of, 48-91
- Emission
 - photoelectric, 49
 - secondary, 50, 72
 - thermionic, 49
 - types of, 48-50
- Emitters
 - heating, 52
 - oxide-coated, 52
 - thoriated-tungsten, 50
 - tungsten, 50
 - types of, 50-52
- Fading, 543
- Feedback amplifiers, 211-219
- Filter circuits, 116-126
- Filters
 - band-elimination, 36-38
 - band-pass, 32-36
 - capacitance, 118
 - crystal, 574
 - inductance, 120
 - L-section, 123
 - pi-section, 121
 - power supply, 116
 - tuned circuits as, 32-39
- Fixed bias voltage supply, 149
- Frequencies, general use of, 546
- Frequency
 - blackouts, 543
 - carrier, 674
 - converter, 590
 - intermediate, 386
 - modulation, 398
 - multipliers, 454
 - pulse-repetition, 675
 - signal, 371
 - standards, 625
 - primary, 625
 - secondary, 626-628
- Frequency-modulation method, radar, 658
- Full-wave doubler, 144
- Functional components, 672
- Gas diodes, 86
- Gas-filled tubes, 82-89
 - electrical conduction in, 84
 - limitations in use of, 85
- Generators
 - a-f signal, 630
 - r-f signal, 628
 - saw-tooth, 318-324, 688
- Grid-bias voltages, 146-150
- Half-wave
 - dipole, 174
 - doubler, 142
- Hertz antennas, 525
- High-frequency
 - compensation, 237
 - long-range communications, 541
- Imaginary numbers, 6
- Impedance
 - antenna input, 520
 - characteristic, of transmission line, 458-463, 465
 - coupled, 226
 - input, 245, 646
 - microphones, 436, 437
 - output, 245
 - parallel, near resonance, 28
- Induction field, 513
- Insulators, metallic, 498
- Interference, measurement and location of, 634
- Inverters, 157
- Ionosphere, 536
 - effect of, on sky wave, 539
- Keying systems, 425-430
- Line reflections, 465-471
- Lines
 - lecher, 495
 - nonresonant, 471
 - quarter-wave, as filters, 504
 - resonant, 472, 497
 - r-f; measurements on, 490-497
 - transmission, 457-506

- Load line, 258-262
- Long-range communications, high-frequency, 541
- Loudspeakers, 558
- Low-frequency compensation, 239
- Marconi antenna**, 528
- Meters**
 - grid-dip, 624
 - radio-interference field-intensity, 631-635
- Microphones, 436-445
- Modulation, 337
 - amplitude, 338-354, 371-387
 - degree of, 358
 - frequency, 354-368, 387
 - grid, 352
 - intensity, 661
 - phase, 364-368
 - plate, 345
- Motor, shunt-wound, 153
- Multielement tubes, 71-80
- Multiple refraction, 542
- Multivibrators, 324-335, 620, 688
- Neutralization**, 418-423
- Nonregistered Publications Memoranda* (NRPM's), 547
- Numbers**
 - complex, 10
 - imaginary, 6
- Open-end transmission line**, 466, 472
- Oscillations, parasitic, 423
- Oscillators**, 294-335
 - beat-frequency, 386, 582
 - Colpitts, 301
 - crystal-controlled, 311-317
 - electron-coupled, 305
 - Hartley, 297-301
 - in transmitter, 402
 - inductance-capacitance, 294-317
 - local; radar, 688
 - negative-resistance, 306
 - push-pull, 304
- Oscillators—Continued
 - repetition-rate, 687
 - resistance-capacitance, 317-335
 - tickler-feedback, 296
 - transitron, 307
 - tuned-plate tuned-grid, 302
 - ultraudion, 301
 - Wein-bridge, 678
- Oscilloscope**
 - cathode-ray; applications of, 603-618
 - circuit, 610-615
- Parallel resonance**, 25-32
 - conditions required for, 26
- Parallel-resonant circuits**, 25
 - applications of, 31
 - loading, 29-31
- Pentodes**, 74
- Phase inverters**, 248-254, 689
 - electron-tube, 251
 - transformer, 249
- Polar**
 - coordinates, 11
 - diagrams, 525
- Power**
 - amplifiers, 163, 164, 281, 408-413, 454, 274-284
 - gain or loss, unit of, 284
 - output, 262-265, 277-284
 - supplies
 - for electronic equipments, 94-158
 - radar, 673, 687
- Propagation**, 509
 - of radio waves, 534-547
 - wave; effect of daylight on, 541
- Pulse-modulation method**, radar, 658
- Push-pull oscillator**, 304
- Quality**, or **Q**, of inductor, 17-24
- Quarter-wave lines**, as filters, 504
- Radar**
 - aircraft, 671

- Radar—Continued
 - circuits, special, 687
 - connecting, 689
 - generating, 687
 - reshaping, 688
 - continuous-wave method, 657
 - development, historical, 659
 - elementary transmitter and receiver, 678-687
 - fighter-director, 671
 - fire control, 671
 - introduction to, 653-689
 - oscillator, local, 688
 - search, 671
 - system constants, 673-678
 - transmitters, 397
 - uses, 659
- Radiation, 509-517
 - field, 515
 - resistance, 523
- Radio waves
 - propagation of, 534-547
 - reflection, 656
- Ratios, current and voltage, 285
- Receivers
 - bias methods in, 413-416
 - communications, elementary, 550-601
 - f-m, 551, 587-601
 - radar, 673, 685
 - superheterodyne, 551, 563-587
 - t-r-f, 551-563
- Rectifiers
 - bridge, 113
 - circuits, 107-116
 - diode as, 60
 - for power supplies, 98-107
 - full-wave, 99, 110
 - half-wave, 107
 - high-vacuum, 99
 - mercury-vapor, 100
 - metallic, 104-107
- Reference levels, zero-power, 286-289
- Repetition-rate oscillator, 687
- Resistance-capacitance
 - coupled circuit, 236
 - coupling, 184-195
 - oscillator, 317-335
- R-f amplifier, 564
- Saturation
 - amplitude, 305
 - current, 58
 - temperature, 59
 - voltage, 58
- Series resonance, 13-24
 - conditions required, 14-17
- Series-resonant circuits, 13
 - applications of, 24
- Shielded pair, wires, 482
- Side bands, f-m, 354
- Slope detector, 387
- Sound-wave reflection, 653
- Spectrum analyzer, 635
- Standing-wave ratio, transmission line, 478
- Supplies, B-voltage, 97-142
- Synchroscope, 618
- Test equipment, electronic, 603
 - 650
- Tester, tubes, 639-644
- Test-tool set, 648-650
- Tetrodes, 71-74
- Thyratrons, 87
- Tickler-feedback oscillator, 296
- Tone control, 558
- Transformers
 - coupling, 196, 223-234
 - output, 269-274
- Transitron oscillator, 307
- Transmission
 - high-frequency; effect of atmosphere on, 545
 - lines, 457-506
 - types, 480
 - tone, 353
 - u-h-f, 544
 - v-h-f, 544

Transmitters, 397-454
 amplitude-modulated radiotele-
 phone, 435-449
 continuous-wave, 401-435
 frequency-modulated radiotele-
 phone, 449-454
 radar, 397, 673, 680
Transmitting and receiving an-
 tenna, 682
Triode amplifiers, Class-A, 257-
 274
Triodes, 60-70
Tubes
 beam-power, 76
 cathode-ray, 89-91, 603-610
 characteristics, 63-67
 electron-ray, 89
 multielement, 71-80
 multigrad, 79
 multiunit, 80
 operating at ultrahigh frequen-
 cies, 80-82
 ordinary, 82
 testers, 639-644
 transmitter electron, 416
 variable-mu, 77
Tuned circuits, 1-46
 as filters, 32-39
 inductively coupled, 39-46
 introduction, 3-5
Tuned-primary tuned-secondary
 circuit, 42
Twisted pair, 482

U-h-f communication, 544
Ultraudion oscillator, 301
Untuned-primary tuned-second-
 ary circuit, 41

Vectors
 expressed algebraically, 6-13
 polar, 13

V-h-f communication, 544
Vibrators, 154
Video amplifiers, 235-241
Voltage
 amplifiers, 163, 256
 dividers and bleeders, 135-142
 gain, 242, 287
 or loss, 287
 multipliers, 145
 peak inverse, 115
 ratio, 285
 regulators, 126-135
 saturation, 58
 supply, fixed bias, 149
Voltage-multiplying circuits,
 142-146
Voltmeter
 electron-tube, 645
 errors, 644
Volt-ohm-ammeter, electronic,
 644-647

Wave
 continuous (c-w), 398
 frequency modulation (fm), 398
 ground, 535
 modulated, 398
 modulated-continuous, 398
 motion on infinite line, 463-465
 polarization, 524
 propagation; effect of daylight
 on, 541
 radio
 propagation of, 509, 534-547
 reflection, 656
 sound; reflection, 653
 sky, 536, 539
 traps, 38
 unmodulated, 398
Waveforms, observation of, 615
Waveguides, 484-490
Wavelength measurements, 494
Wein-bridge oscillator, 678