

**A**

AC circuit, LLFT networks  
 average power, 24-63–24-73  
 input impedance, 24-64  
 load impedance, 24-71  
 maximum average power,  
 24-72–24-73  
 power factor (PF), 24-63  
 power triangle, 24-67  
 RMS values, 24-66  
 sinusoidal sources, 24-62–24-63

Active filter synthesis, SFG  
 filter transfer function  
 all-pole transfer function,  
 21-20  
 differential-input op-amp  
 circuit, 21-17  
 dummy branch insertion,  
 21-13  
 four op-amp circuit,  
 21-18–21-19  
 gain function, 21-12–21-13  
 lowpass filter specifications,  
 21-19  
 Mason's gain formula, 21-12  
 RC-op-amp circuits,  
 21-14–21-15  
 state variable biquad,  
 21-19–21-20  
 transfer voltage ratio, 21-11  
 two op-amp circuit  
 realizations, 21-15–21-16

passive filter circuit  
 bandpass passive filter,  
 21-9  
 Butterworth low-pass filter,  
 21-7–21-9

Chebyshev low-pass  
 response, 21-10  
 component op-amp circuits,  
 21-5–21-7  
 doubly terminated passive  
 filter, 21-4  
 general ladder network,  
 21-4–21-5  
 leapfrog realization,  
 21-5–21-9  
 normalization,  
 21-10–21-11

Adaptive fault tolerance (AFT),  
 4-27–4-28

Adjustable capacitor,  
 11-27–11-28

Air inductor  
 advantages, 11-48  
 coil dimensions, 11-45–11-47  
 design guidance, 11-47  
 disadvantages, 11-49  
 frequency ranges, 11-48  
 quality factor, 11-47–11-48

Algebra  
 ring concept, 2-2  
 vector multiplication, 2-2–2-3

Analog 2-D filter  
 quadrantal and octagonal  
 symmetry,  
 10-28–10-29  
 rotational and diagonal  
 symmetry, 10-29  
 transfer function, 10-27

Arc coloring theorem  
 graph painting, 7-25–7-26  
 induction hypothesis, 7-26  
 resistances and voltages, 7-27

**B**

Bandpass filter (BPF)  
 MATLAB optimization, 10-32  
 specifications, 10-31–10-32

Bandpass sampling theorem,  
 6-5–6-6

Bandstop filter (BSF)  
 coefficients and specification,  
 10-35  
 contour and 3-D magnitude  
 plots, 10-36

Bijjective function, 1-4

Bilinear operators  
 basis tensors  
 finite-dimensional vector  
 spaces, 2-5–2-8  
 Kronecker product, 2-8  
 determinants, 2-9–2-11  
 matrix inversion, 2-14–2-16  
 multiple products, 2-8–2-9  
 property interchange, 2-16–2-18  
 skew symmetric products  
 $k$  interchanges, 2-11  
 $p$ -linear operator, 2-12–2-14  
 tensor product  
 arbitrary bilinear operator,  
 2-4  
 isomorphism, 2-5

Binet–Cauchy theorem, 7-15–7-16

Bipolar junction transistor (BJT)  
 amplifier  
 amplification, 15-1–15-2  
 circuit schematic symbol,  
 18-1, 18-2  
 discrete vs. IC amplifier  
 component differences,  
 15-6–15-7

- parasitic differences, 15-7-15-8
  - history, 15-2
  - IC amplifiers
    - active loads, 15-10-15-11
    - BJT differential pair, 15-20-15-21
    - cascode amplifier stage, 15-15-15-17
    - common-base stage, 15-13-15-14
    - common emitter stage, 15-11-15-13
    - differential stage, 15-18-15-20
    - emitter follower, 15-14-15-15
    - small-signal models, 15-8-15-10
  - IC power output stages
    - circuit efficiency, 15-31-15-32
    - class-B output stage, 15-32-15-33
    - class-D output stage, 15-33-15-36
    - limitations, 15-29-15-30
    - thermal resistance, 15-30-15-31
  - operational amplifiers
    - analog computer, 15-21-15-22
    - classical architecture, 15-22-15-23
    - features, 15-22
    - high-gain differential stage, 15-23-15-24
    - second amplifier stage, 15-24-15-26
    - specifications, 15-26-15-27
  - types and applications
    - distortion-free and nonlinear distortion, 15-4
    - frequency range and output power, 15-3
    - input and output variables, 15-2-15-3
    - intercept points, 15-5
    - operational amplifiers (op-amp), 15-5-15-6
    - total harmonic distortion (THD), 15-4
  - wideband amplifiers
    - composite stages, 15-27-15-28
    - feedback cascades, 15-28-15-29
  - BJT amplifier, *see* Bipolar junction transistor amplifier
  - Broad-sense Hurwitz polynomial (BHP), 9-5
  - Butterworth low-pass filter
    - fourth-order, 21-7
    - third-order, 21-8-21-9
- C**
- Capacitive tree-branch voltages, 27-7, 27-8
  - Capacitor
    - dielectric constant, 11-24
    - geometry
      - air variable capacitor, 11-36
      - chip capacitor, 11-37
      - ESI and ESR, 11-34, 11-36
      - high-voltage capacitor, 11-29, 11-37
    - linear capacitor
      - adjustable capacitor, 11-27-11-28
      - energetic power capacitor, 11-28, 11-29
      - fixed capacitor-class 1, 11-26-11-27
      - high-voltage capacitor, 11-28-11-29
      - interference suppression capacitor, 11-30
      - leakage current and ionization threshold, 11-39
      - power factor and capacitance dependence, 11-37-11-38
    - nonlinear capacitor
      - ferroelectric capacitor, 11-31-11-32
      - polar polymer dielectric capacitor, 11-32-11-33
    - power and quality factor, 11-25
    - properties
      - nonorganic capacitor, 11-33-11-34
      - organic capacitor, 11-34, 11-35
      - super capacitor, 11-34
    - $\nu'$  index, 11-25-11-26
  - Cauchy's residue theorem, 5-7
  - Chirp z-transform algorithm, 5-17
  - Circuit elements
    - characterization
      - dynamic model, 13-9-13-10
      - formal methods, 13-3-13-4
      - memristive element, 13-8
      - reactive element, 13-7-13-8
      - resistive element, 13-4-13-7
    - connecting multiport (CMP)
      - linear circuit, KCL and KVL, 13-10-13-11
      - nonlinear circuit and partition, 13-1-13-2
    - lumped circuit approximation, 13-1
    - tableau formulation, 13-11
  - CMOS, *see* Complementary metal oxide semiconductor
  - Coates' gain formula
    - coefficient matrix, 8-7-8-8
    - $n \times n$  matrix, 8-6-8-7
    - nonsingular matrix, 8-5
    - topological formula, 8-4
  - Common-mode rejection ratio (CMRR), 15-27
    - common-mode gain, 16-16-16-17
    - differential and noninverting configuration, 16-17
    - total output voltage, 16-17-16-18
  - Continuous-time Fourier transform
    - convergence, 4-10-4-11
    - CT and the DT sampled model, 4-5-4-6
    - exponential Fourier series, 4-7-4-8
    - Fourier spectrum, 4-6
    - periodic continuous-time signals, 4-11
    - properties, 4-2-4-5
    - trigonometric expansion, 4-8-4-10
  - Continuous-time signals
    - convergence, 4-10-4-11
    - CT and the DT sampled model, 4-5-4-6
    - exponential Fourier series, 4-7-4-8
    - Fourier spectrum, 4-6
    - periodic continuous-time signals, 4-11
    - properties, 4-2-4-5

- trigonometric expansion, 4-8-4-10
  - Continuous wavelet transform (CWT), 6-15
  - Controlled circuit elements
    - controlled sources
      - CCCS and CCVS, 14-4-14-7
    - circuit representation, 14-1, 14-2
    - VCCS and VCVS, 14-1-14-4
    - signal converters
      - circulator, 14-12-14-15
      - current negative impedance converter, 14-11-14-12
      - definition, 14-15
      - gyrator, 14-8-14-10
      - network ports, 14-7-14-8
      - voltage negative impedance converter, 14-11
  - Cooley-Tukey FFT, 10-11
  - Cored inductor
    - advanced inductor, 11-56
    - closed magnetic circuit
      - air gap, 11-51-11-53
      - apparent permeability, 11-54
      - equivalent dimensions and parameters, 11-50-11-51
      - incomplete coupling, 11-53
      - joint effect, 11-54-11-55
      - leakage coefficient, 11-54
    - open magnetic circuit, 11-55-11-56
    - parameters, 11-49-11-50
    - power loss
      - definition, 11-56-11-57
      - dielectric loss, 11-59-11-60
      - magnetic loss, 11-57-11-59
      - resistive loss, 11-57
      - sinusoidally excited inductor, 11-60
  - Cramer's rule, 1-19
  - Critical temperature resistors (CTR), 11-10
  - Current-controlled current source (CCCS)
    - circuit implementation, 14-7
    - circuit schematic symbol, 18-3, 18-4
    - equivalent circuit, 14-6
    - SPICE format, 14-6
  - Current-controlled voltage source (CCVS), 14-4
    - circuit implementation, 14-5-14-6
    - circuit schematic symbol, 18-3
    - SPICE format, 14-5
  - Current feedback op-amp (CFOA)
    - bipolar realization, 17-5
    - buffer and CFOA
      - implementation
        - frequency response, 17-7, 17-9
      - open-loop transimpedance, 17-7, 17-9
      - output impedance
        - characteristics, 17-7-17-8
      - schematics and layout plot, 17-6-17-7
      - step response and harmonic distortion, 17-11
      - voltage buffer performance, 17-7
    - closed-loop gain, 17-3-17-4
    - CMOS compound device, 17-5
    - macromodel, 17-2-17-3
    - total impedance, 17-3
  - Current-mode op-amp
    - closed-loop characteristics, 16-35-16-36
    - dynamics, 16-37-16-38
    - higher-order effects, 16-38-16-40
  - Cutset-loop circuit analysis
    - analogous problem, mesh analysis, 19-31
    - circuit representation, 19-39-19-41
    - failure, nodal analysis, 19-30-19-31
    - fundamental cutset and loop, 19-32
    - graphical representation, 19-31-19-32
    - KCL equation, 19-32-19-34
    - KVL equation, 19-34
    - norator, 19-35-19-36
    - nullator and equivalent subcircuit, 19-37
    - passive element and equivalent circuits, 19-36-19-37
    - three-terminal/two-port element, 19-37-19-39
    - two-terminal element, 19-35-19-40
- ## D
- Determinant decision diagrams (DDD)
    - matrix determinant and representation, 25-24-25-25
    - nodal analysis, 25-23-25-24
    - vertex and vertex ordering, 25-24
  - Differential-input op-amp circuit, 21-7
  - Digital filter banks
    - basis function, 6-29-6-30
    - half-band filter, 6-27
    - paraunitary filter bank
      - parametrization, 6-27
      - reconstruction system, 6-25-6-27
    - polyphase representation, 6-24-6-25
    - subband reconstruction
      - conjugate quadrature filter, 6-23-6-24
      - PR property, 6-23
    - tree-structured system, 6-28-6-29
    - two-channel filter bank, 6-22
  - Digital filters
    - continuous-time frequency response, 10-15
    - discrete-time frequency response, 10-15-10-16
    - magnitude response, 10-16
    - quadrantal and octagonal symmetry, 10-29-10-30
    - rotational and diagonal symmetry, 10-30
  - Dirac delta function
    - definition, 3-42-3-43
    - doublet signal, 3-44
    - impulse function, 3-43
  - Discrete Fourier transform (DFT), 25-16
    - FFT algorithm
      - applications, 4-19
      - ordered inputs and bit-reversed outputs, 4-18-4-19
      - types and development, 4-17
    - properties, 4-15-4-17

Discrete-time Fourier transform (DTFT)  
 vs. CT spectra, 4-14-4-15  
 DTFT pairs  
 definition and bilateral z-transform, 4-12  
 types, 4-13  
 properties, 4-13-4-14  
 Doubly terminated passive filter, 21-4

## E

Eigenvalues  
 inverse matrix, 1-18  
 singular-value decomposition (SVD), 1-17  
 Electrical circuit  
 classifications  
 active vs. passive, 18-12  
 linear vs. nonlinear, 18-11-18-12  
 lumped vs. distributed, 18-13-18-15  
 time-varying vs. time-invariant, 18-12-18-13  
 current polarity  
 charge transport, 18-5-18-6  
 current flow, 18-4-18-5  
 energy and voltage, 18-7-18-8  
 power  
 calculations, 18-8-18-9  
 conversation, 18-8-18-9  
 schematic symbols  
 controlled sources, 18-2-18-4  
 multiterminal elements, 18-1-18-2  
 two-terminal elements, 18-1, 18-2  
 voltage-mode operational amplifier, 18-4, 18-5  
 Electromagnetic interference (EMI), 11-49  
 Energetic power capacitor, 11-28, 11-29  
 Equivalence transformation, 1-14-1-15  
 Equivalent series inductance (ESI), 11-34  
 Equivalent series resistance (ESR), 11-25  
 Eternal signals, 26-3-26-4

## F

Fast Fourier transform (FFT), 25-17  
 algorithms  
 applications, 4-19  
 ordered inputs and bit-reversed outputs, 4-18-4-19  
 types and development, 4-17  
 centrosymmetry, 10-13  
 quadrantal symmetry, 10-14  
 symmetry-based 1-D FFT, 10-11-10-12  
 Ferrodielectric capacitor, 11-31-11-32  
 Filter banks  
 digital filter banks  
 basis function, 6-29-6-30  
 half-band filter, 6-27  
 paraunitary properties, 6-25-6-27  
 polyphase representation, 6-24-6-25  
 subband construction, 6-22-6-24  
 tree-structured system, 6-28-6-29  
 two-channel filter bank, 6-22  
 paraunitary filter banks  
 dilation equation application, 6-63-6-64  
 infinite product convergence, 6-64-6-65  
 orthonormal wavelet basis, 6-65-6-70  
 parametrization, 6-27  
 wavelet tight frames, 6-70-6-71  
 synthesis and reconstruction, 6-13-6-14  
 time-frequency representation, 6-13  
 wavelet function design, 6-14-6-15  
 Filter transfer function  
 all-pole transfer function, 21-20  
 differential-input op-amp circuit, 21-17  
 dummy branch insertion, 21-13  
 four op-amp circuit, 21-18-21-19  
 gain function, 21-12-21-13  
 lowpass filter specifications, 21-19  
 Mason's gain formula, 21-12

RC-op-amp circuits, 21-14-21-15  
 state variable biquad, 21-19-21-20  
 transfer voltage ratio, 21-11  
 two op-amp circuit realizations, 21-15-21-16  
 First-order circuits, time domain analysis  
 network time constant, 26-10  
 transfer functions, 26-6-26-7  
 transient and steady-state responses, 26-9-26-10  
 zero-input response, 26-7-26-8  
 zero-state response, 26-8-26-9  
 Fixed capacitor, 11-26-11-27  
 Fixed resistor  
 chip resistor, 11-6, 11-7  
 dynamic tolerance  $\Delta$  and resistor class, 11-2-11-3, 11-4  
 high-ohmic, high-voltage resistor, 11-6  
 high-power resistor, 11-6-11-7  
 resistive network, 11-5-11-6  
 temperature coefficient of resistance (TCR), 11-3, 11-5  
 Fourier transform  
 adaptive fault tolerance (AFT), 4-27-4-28  
 complex Fourier transform, 4-6-4-7  
 continuous-time signals  
 convergence, 4-10-4-11  
 CT and the DT sampled model, 4-5-4-6  
 exponential Fourier series, 4-7-4-8  
 Fourier spectrum, 4-6  
 periodic continuous-time signals, 4-11  
 properties, 4-2-4-5  
 trigonometric expansion, 4-8-4-10  
 discrete Fourier transform (DFT)  
 FFT algorithm, 4-17-4-19  
 properties, 4-15-4-17  
 discrete-time Fourier transform (DTFT)  
 vs. CT spectra, 4-14-4-15  
 DTFT pairs, 4-12-4-13  
 properties, 4-13-4-14

- FFT spectral analysis
    - leakage and the picket-fence effect, 4-21-4-22
    - windowing and zero-padding, 4-21
  - FIR digital filter design
    - bandpass FIR filter, 4-22-4-23
    - frequency response, 4-22
  - functional relationships, 4-19-4-20
  - real-time filtering, Fourier block processing
    - block algorithms, 4-24
    - overlap-add processing, 4-23-4-24
    - overlap-save processing, 4-23
  - transform domain adaptive filter (TDAF)
    - adaptive tap vector, 4-25
    - autocorrelation matrix, 4-24-4-25
    - characteristics, 4-26-4-27
    - filter output and LMS adaptive algorithm, 4-24
    - Karhunen-Loe'v transform (KLT), 4-26
    - power, 4-25-4-26
    - transformed outputs, 4-25
  - Fractal capacitors
    - boost factor vs. horizontal spacing, 12-7
    - bottom-plate parasitic capacitance, 12-5-12-6
    - fractal dimension, 12-4-12-6
    - high-density capacitor, 12-2
    - interdigitated capacitor, 12-7-12-8
    - lateral flux capacitors, 12-2-12-3
    - parallel-plate and MOS, 12-1-12-2
    - quality factor and lateral spacing, 12-7
    - three-dimensional representation, 12-5, 12-6
    - woven structure, 12-8
  - Frequency-dependent negative resistance (FDNR), 14-10
  - Frequency-domain analysis
    - advanced network analysis
      - CCCS and VCVS gain, 22-34-22-35
      - circuit branch admittance, 22-27-22-30
      - circuit branch impedance, 22-30
      - circuit transadmittance, 22-31-22-33
      - circuit transimpedance, 22-31
      - driving point impedances, 22-35-22-39
      - engineering utility, 22-18-22-25
      - fundamental concepts, 22-11-12-15
      - Kron-Bode formula, 22-25-22-27
      - Kron's formula, 22-15-22-18
      - sensitivity analysis, 22-39
      - transposed connection vector, 22-14
    - LLFT network
      - capacitor voltage and current, 24-2
      - dividers, 24-15-24-18
      - inductor voltage and current, 24-3
      - Middlebrook's extra element theorem, 24-38-24-42
      - Norton's theorem, 24-31-24-32
      - Ohm's law, 24-1-24-2
      - one-port LLFT network, 24-5
      - properties, 24-10-24-12
      - $\pi$ -T conversion, 24-34-24-35
      - reciprocity, 24-35-24-37
    - network functions
      - Cramer's rule, 22-3
      - definition, 22-1
      - inductor current, 22-5-22-6
      - Laplace transform, 22-9-22-10
      - modified nodal, 22-4
      - network stability, 22-8-22-9
      - output and input impedance, 22-2
      - output voltage and input voltage, 22-1
      - ratio of two polynomials, 22-6
      - roots of the numerator and denominator, 22-7
      - stability, 22-8-22-9
      - time-domain response, 22-10
      - transfer function, 22-3
    - sinusoidal steady state analysis
      - AC circuit power, 24-62-24-73
      - network transfer function, 24-46-24-47
      - output voltage, 24-48
      - phase lead and lag, 24-55-24-57
      - phasor and network, 24-53-24-55
      - RC and RL network, 24-57-24-59
      - resonance, 24-60-24-62
      - steady-state output voltage, 24-49
      - transient and steady-state response, 24-45
    - source transformations, 24-12-24-15
    - substitution theorem, 24-43-24-44
    - superposition theorem
      - dependent and independent source, 24-19-24-20
      - loop impedance matrix, 24-18
    - Thévenin's theorem
      - application, 24-28-24-29
      - dependent sources, 24-24-24-25
      - impedance, 24-26
      - source transformation, 24-29-24-30
      - subnetworks, 24-24
      - two-port networks, 24-5-24-6
- Front-end amplifier, *see* RF low-noise amplifiers
- ## G
- Gate-drain capacitance ( $C_{gd}$ ) effect, 17-14-17-15
  - Generalized impedance convertor (GIC), 14-10
  - Geometric mean distance (GMD), 12-13
  - Graph theory
    - arc coloring theorem
      - graph painting, 7-25-7-26
    - induction hypothesis, 7-26
    - resistances and voltages, 7-27
    - circuit and cutset
      - circuit matrix, 7-12
      - cut matrix, 7-10-7-11

- electrical networks
    - KCL and the KVL, 7-19
    - loop and cutset methods, 7-20–7-21
    - network elements and directed graph, 7-18
  - incidence matrix
    - determinant, 7-10
    - directed graph, 7-9
    - incidence vector, 7-9–7-10
  - orthogonality relation, 7-12–7-14
  - relative orientations, 7-12
  - Tellegen theorem
    - 2-port network, 7-21–7-22
    - adjoint elements, 7-23–7-24
    - open-circuit voltage ratio, 7-24
    - voltage and current change, 7-22
  - tree enumeration spanning
    - Binet–Cauchy theorem, 7-15–7-16
    - directed graph, 7-17
    - undirected graph, 7-16–7-17
- H**
- Haar wavelet basis, 6-11–6-12
  - Hierarchical methods
    - advantage, 25-17, 25-18
    - bipolar cascode stage, 25-19–25-20
    - modified nodal analysis and NAM, 25-19
    - resistance ladder network, 25-17–25-18
    - topological analysis, 25-18
  - Higher-order log-domain filters, 17-45
  - High-frequency (HF) amplifiers
    - current feedback op-amp (CFOA)
      - bipolar realization, 17-5
      - buffer and CFOA implementation, 17-7–17-11
      - closed-loop gain, 17-3–17-4
      - CMOS compound device, 17-5
      - macromodel, 17-2–17-3
      - total impedance, 17-3
    - high-Q resonators
      - gm-C bandpass biquad, 17-32–17-34
      - IF-sampling, 17-29–17-30
      - triode region transistor, 17-31
      - unity-gain frequency, 17-32
    - log-domain process
      - basic log-domain integrator, 17-41–17-44
      - filter synthesis, 17-36–17-37
      - higher-order log-domain filters, 17-45
      - instantaneous companding, 17-34–17-36
      - performance aspects, 17-37–17-40
    - operation layout
      - feedback reduction, 17-23
      - flip-chip connection, 17-24
      - high-frequency (HF) ground, 17-23
      - input/output isolation, 17-23
      - I/O pads, 17-23
    - optical low-noise preamplifiers
      - front-end noise sources, 17-17–17-18
      - receiver performance criteria, 17-19–17-21
      - transimpedance (TZ) amplifiers, 17-21–17-22
    - RF low-noise amplifiers
      - cascode common source LNA, 17-15–17-16
      - CMOS common-source LNA, 17-12–17-15
      - gain, 17-10–17-12
      - input impedance matching and linearity, 17-12
      - noise, 17-8
    - RF power amplifier
      - classification, 17-24–17-25
      - PA requirements, 17-24
      - practical considerations, 17-27
      - wireless transceiver, 17-2
    - High-pass filter (HPF)
      - coefficients and specification, 10-34
      - contour and 3-D magnitude plots, 10-35
  - High-Q resonators
    - gm-C bandpass biquad
      - biquad bandpass and SFDR, 17-33
      - Q passive on-chip inductors, 17-32
      - simulated bandpass frequency response, 17-34
    - IF-sampling
      - ADC and sampling receiver, 17-29
      - continuous-time Sigma-Delta modulator, 17-30
    - linear region transistor implementation
      - triode region transistor, 17-31
      - unity-gain frequency, 17-32
  - High-voltage capacitor, 11-28–11-29
  - Hilbert space frame
    - arbitrary vector representation, 6-44
    - definition, 6-44
    - dual frame and sequence, 6-47
    - frame operator, 6-46
    - Riesz basis, 6-44–6-45
    - tight frame, 6-46
  - Hölder regularity index, 6-74
  - Hurwitz polynomials
    - analog
      - 2-V polynomials, zeroes continuity property, 9-7–9-10
    - broad-sense Hurwitz polynomial (BHP), 9-5
    - Hurwitz polynomial in the strict sense (HPSS), 9-6
    - immittance Hurwitz polynomial (IHP), 9-7
    - narrow-sense Hurwitz polynomial (NHP), 9-5
    - reactance Hurwitz polynomial (RHP), 9-7
    - scattering Hurwitz polynomial (SHP), 9-5–9-6
    - self-paraconjugate polynomial and SPHP, 9-5
    - very strict Hurwitz polynomial (VSHP), 9-6

- preliminaries and notations
    - analog biplane, 9-2-9-3
    - infinite distant points, 9-2
    - isolated and continuum of zeroes, 9-3
  - two-dimensional Hurwitz polynomials, 9-11-9-12
  - two-variable polynomial, infinity
    - 1-D complex plane, 9-3
    - 2-D biplane, 9-4
  - nonessential singularities
    - second kind (NSSK), 9-4
  - 2-V very strict Hurwitz polynomial (VSHP), 9-10-9-11
  - Hybrid parameters
    - bipolar transistors, 20-11-20-12
    - circuit model, 20-10-20-11
    - common emitter configuration, 20-11
- ## I
- 
- Ideal bandpass wavelet
    - Fourier transform, 6-5-6-6
    - frequency axis splitting, 6-6-6-7
    - impulse response, 6-8
    - vs. low-pass, 6-5-6-6
  - Ideal operational amplifier
    - circuit applications
      - frequency dependence, 16-5-16-6
    - instrumentation amplifiers, 16-8
    - inverting configuration, 16-5
    - multiple input circuits, 16-7-16-8
    - noninverting configuration, 16-4-16-5
    - nonlinear transfer functions, 16-6
    - simple attenuator, 16-4
    - unity gain buffer, 16-3
    - comparators, 16-9-16-10
    - inverting amplifier
      - configuration, 16-10-16-11
    - open-loop equivalent circuit
      - characterization, 16-1
      - types and configurations, 16-2-16-3
    - voltage op-amps, 16-3
  - Impedance Hurwitz polynomial (IHP), 9-7
  - Impact avalanche transit time (IMPATT) diode, 11-73
  - Indefinite admittance matrix (IAM) approach
    - basics, 25-10-25-11
    - resistive circuit, 25-11-25-12
  - Inductive link current
    - capacitive tree-branch voltages, 27-7-27-8
    - state equations, 27-5-27-6
  - Inductor
    - air inductor
      - advantages, 11-48
      - coil dimensions, 11-45-11-47
      - design guidance, 11-47
      - disadvantages, 11-49
      - frequency ranges, 11-48
      - quality factor, 11-47-11-48
    - circuit representation, 11-45
    - cored inductor
      - advanced inductor, 11-56
      - closed magnetic circuit, 11-50-11-55
      - open magnetic circuit, 11-55-11-56
      - parameters, 11-49-11-50
      - power loss, 11-56-11-60
    - definition, 11-63-11-64
    - functions and parameters, 11-44
    - fundamental observations, 11-42, 11-43
    - graphical symbols, 11-40
    - inductance, 11-40-11-42
    - magnetic core materials, 11-61-11-63
    - nonlinearity, 11-60-11-61
    - physical irregularities, 11-63
    - qualifiers and attributes, 11-42-11-43
  - Integrated circuit (IC) amplifiers, 15-3
    - active loads, 15-10-15-11
    - BJT differential pair, 15-20-15-21
    - cascode stage
      - advantages, 15-15-15-16
      - high-frequency equivalent circuit, 15-16-15-17
    - circuit efficiency, 15-31-15-32
    - class-B output stage
      - bias circuit, 15-33
      - Darlington output stages, 15-33
      - short-circuit proof, 15-32
    - class-D output stage,
      - PWM amplifier
        - advantage and disadvantage, 15-35
        - architecture, 15-33, 15-34
        - configurations, 15-35-15-36
        - duty cycle, 15-33-15-34
    - common-base stage, 15-13-15-14
    - common emitter stage
      - configuration, 15-11
      - equivalent circuit, 15-11-15-12
      - upper corner frequency, 15-12-15-13
    - differential stage
      - advantages and configuration, 15-18
      - mode of operation, 15-19-15-20
    - emitter follower, 15-14-15-15
    - limitations, power output, 15-29-15-30
    - small-signal models
      - hybrid- $\pi$  model, 15-8-15-9
      - unilateral equivalent circuit, 15-9-15-10
    - thermal resistance, 15-30-15-31
  - Interference suppression capacitor, 11-30
  - Inverse Laplace transform
    - partial fraction expansion (PFE)
      - repeated linear factors, 3-31
      - repeated quadratic factors, 3-31-3-32
      - simple linear factors, 3-27-3-29
      - simple quadratic factors, 3-29-3-30
    - residue theory
      - differentiated time function, 3-24
      - LT occurrence, 3-25
      - Taylor series expansion, 3-23
    - time function, 3-22
  - Inverse z-transform
    - contour integration
      - Cauchy's residue theorem, 5-7
    - order interchanging, 5-6-5-7
    - residues, 5-6-5-7

inspection method and power series expansion, 5-8  
 partial fraction expansion, 5-7-5-8  
 Inversion negative impedance converter (INIC), 14-11

## K

Kirchhoff's current law (KCL), 13-10-13-11  
 circuit paths, 19-6-19-7  
 cutset-loop circuit analysis, 19-32-19-34  
 Gaussian surface, 19-5-19-6  
 illustration, 19-4-19-5  
 mesh analysis, 19-24, 19-25  
 voltage rise and drop, 19-7  
 Kirchhoff's voltage law (KVL)  
 circuit analysis, 19-8-19-9  
 circuit paths, 19-8  
 cutset-loop circuit analysis, 19-34  
 illustration, 19-7-19-8  
 mesh analysis, 19-24-19-26  
 Kron's formula  
 engineering utility  
 bipolar junction transistor amplifier, 22-23  
 Bode's theory, 22-21  
 common emitter amplifier, 22-21-22-22  
 perturbed voltage gain, 22-18-22-19  
 transfer function sensitivity, 22-20-22-21  
 generalization  
 I-O transfer characteristic node, 22-25  
 return ratio, 22-26-22-27  
 transfer function and return ratio, 22-26  
 impedance inclusion, 22-15-22-16  
 output voltage, 22-17-22-18  
 Thévenin voltage and impedance, 22-16-22-17

## L

Laplace transformation  
 bilateral Laplace transform (BLT), 3-8-3-9  
 Dirac delta function  
 definition, 3-42-3-43

doublet signal, 3-44  
 impulse function, 3-43  
 discrete-time Laplace transform (DTLT), 3-45  
 forced response, 3-4  
 homogeneous solution and natural response, 3-2-3-3  
 inverse Laplace transform  
 partial fraction expansion (PFE), 3-27-3-32  
 residue theory, 3-23-3-27  
 time function, 3-22  
 Laplace-domain phasor circuits, 3-41-3-42  
 linear system  
 differential equation, 3-32-3-34  
 generalized phasor, 3-34-3-35  
 magnitude and phase response, 3-35-3-37  
 nonhomogeneous solution and forced response, 3-4-3-5  
 phasor concept generalization  
 complex number, 3-7  
 generalized phasor, 3-7-3-8  
 pole-zero analysis  
 BIBO stability, 3-38-3-39  
 general function,  $F(s)$ , 3-15  
 natural modes, 3-37-3-38  
 polynomial factorization, 3-16  
 ROC, 3-16-3-18  
 stability and natural modes, 3-39-3-41  
 properties  
 convolution property, 3-20-3-21  
 modulation property, 3-19  
 square wave, 3-19  
 time-differentiation property, 3-20  
 ULT, 3-18  
 series RLC circuit, 3-2  
 solution scrutinization, 3-6-3-7  
 total solution, 3-5-3-6  
 unilateral Laplace transforms  
 direct computation, 3-11-3-15  
 operational properties, 3-18-3-22  
 Linear capacitor  
 adjustable capacitor, 11-27-11-28

energetic power capacitor, 11-28, 11-29  
 fixed capacitor-class  
 1, 11-26-11-27  
 high-voltage capacitor, 11-28-11-29  
 interference suppression capacitor, 11-30  
 Linear operators and matrices  
 bijective function, 1-4  
 characteristics  
 eigenvalues, 1-15-1-17  
 eigenvectors, 1-16  
 singular values, 1-17-1-18  
 determinants  
 definition, 1-8  
 first-and second order matrix, 1-10  
 Laplace's expansion, 1-9  
 linear systems  
 Cramer's rule, 1-19  
 input and output system, 1-18  
 poles and zeros, 1-18-1-19  
 matrix operations  
 matrix addition, 1-7  
 matrix multiplication, 1-7-1-8  
 matrix transposition, 1-8  
 vector addition, 1-6  
 matrix representations, 1-6  
 transformations  
 equivalence transformation, 1-14-1-15  
 similarity transformation, 1-12-1-14  
 vector spaces over fields  
 field  $F$ , properties, 1-2  
 $F$ -vector space, 1-2-1-3  
 $n$ -dimensional vector space, 1-3-1-4  
 Linear resistor, 11-1-11-2  
 fixed resistor  
 chip resistor, 11-6, 11-7  
 dynamic tolerance  $\Delta$  and resistor class, 11-2-11-3, 11-4  
 high-ohmic, high-voltage resistor, 11-6  
 high-power resistor, 11-6-11-7  
 resistive network, 11-5-11-6  
 temperature coefficient of resistance (TCR), 11-3, 11-5



- variable resistor, potentiometers
    - electric circuit, 11-7, 11-8
    - tapers, 11-9
    - types, 11-7–11-9
  - Linear time-invariant systems,
    - $z$ -Transform
    - one-sided  $z$ -transform, 5-14
    - system transfer function, 5-13–5-14
  - Log-domain process
    - basic log-domain integrator
      - component mismatch, 17-41
      - frequency limitations, 17-43–17-44
      - noise, 17-44
      - Ohmic resistance, 17-42–17-43
    - filter synthesis, 17-36–17-37
    - higher-order log-domain filters, 17-45
    - instantaneous companding, 17-34–17-36
    - performance aspects
      - finite current gain, 17-38–17-39
      - frequency performance, 17-39–17-40
      - tuning range, 17-37–17-38
  - Low-pass filter (LPF)
    - coefficients and specification, 10-33
    - contour and 3-D magnitude plots, 10-34
  - Lumped, linear, finite, time-invariant (LLFT) networks
    - capacitor voltage and current, 24-2
    - impedance concept
      - one-port network, 24-3–24-5
      - two-port networks, 24-5–24-6
    - independent nodes, 24-6–24-7
    - inductor voltage and current, 24-3
    - inverse transform phasors, 24-52–24-53
    - LLFT networks, 24-3–24-4
    - loop impedance matrix, 24-9–24-10
    - Middlebrook's extra element theorem
      - parallel version, 24-38–24-40
      - series version, 24-40–24-43
    - nodal admittance matrix, 24-6–24-7
    - Ohm's law, 24-1–24-2
    - one-port LLFT network, 24-5
    - phasor transforms
      - Euler's identity, 24-49
      - integration constant, 24-52
      - sine and cosine function, 24-50
    - properties
      - driving-point network
        - function polynomial, 24-11–24-12
        - poles and zeroes, 24-10
        - transfer function, 24-12
    - $\pi$ -T conversion
      - loop equation, 24-35
      - networks, 24-34–24-35
      - T replacement, 24-35
    - reciprocity
      - circuit modification, 24-36–24-37
      - excitation and response, 24-37
      - reciprocal network, 24-35–24-36
    - sinusoidal steady state analysis
      - AC circuit power, 24-62–24-73
      - network transfer function, 24-46–24-47
      - output voltage, 24-48
      - phase lead and lag, 24-55–24-57
      - phasor and network, 24-53–24-55
      - RC and RL network, 24-57–24-59
      - resonance, 24-60–24-62
      - steady-state output voltage, 24-49
      - transient and steady-state response, 24-45
    - source transformations, 24-12–24-15
    - substitution theorem, 24-43–24-44
    - superposition
      - dependent and independent source, 24-19–24-20
      - loop impedance matrix, 24-18
    - Thévenin's theorem
      - application, 24-28–24-29
      - dependent sources, 24-24–24-25
      - impedance, 24-26
      - source transformation, 24-29–24-30
      - subnetworks, 24-24
      - two-port networks, 24-5–24-6
      - voltage excitation, 24-8–24-9
- M**


---

  - Magnitude response symmetry
    - 2-D polynomials determination
      - diagonal symmetry, 10-25–10-26
      - fourfold rotational symmetry, 10-26
      - octagonal symmetry, 10-27
      - quadrantal symmetry, 10-21–10-25
    - analog 2-D filter
      - quadrantal and octagonal symmetry, 10-28–10-29
      - rotational and diagonal symmetry, 10-29
      - transfer function, 10-27
    - applications
      - continuous-time frequency response, 10-15
      - discrete-time frequency response, 10-15–10-16
      - magnitude-squared functions, 10-16
    - bandpass filter
      - MATLAB optimization, 10-32
      - specifications, 10-31–10-32
    - bandstop filter
      - coefficients and specification, 10-35
      - contour and 3-D magnitude plots, 10-36
    - digital filters
      - continuous-time frequency response, 10-15
      - discrete-time frequency response, 10-15–10-16
      - magnitude response, 10-16
      - quadrantal and octagonal symmetry, 10-29–10-30
      - rotational and diagonal symmetry, 10-30

- high-pass filter
    - coefficients and specification, 10-34
    - contour and 3-D magnitude plots, 10-35
  - low-pass filter
    - coefficients and specification, 10-33
    - contour and 3-D magnitude plots, 10-34
    - magnitude-squared functions, 10-16
  - Mason's gain formula
    - feedback loops, 8-10
    - $j$  self-loops, 8-9
    - Mason graph, 8-8-8-9
  - Matrix operations
    - addition, 1-7
    - multiplication, 1-7-1-8
    - transposition, 1-8
    - vector addition, 1-6
  - Maximum power transfer theorem
    - load resistance, 19-55-19-58
    - power vs. resistance, 19-55, 19-56
  - Mesh analysis
    - circuit graph, 19-22-19-23
    - current sources, 19-26
    - deactivated current, 19-27
    - dependent source, 19-28-19-30
    - features and constraints, 19-27-19-28
    - independent source, 19-30
    - KCL, 19-24, 19-25
    - KVL, 19-24-19-26
    - mesh current, 19-24, 19-25
    - one-mesh circuit, 19-23
    - two-mesh circuit, 19-23-19-24
  - Metal-insulator-metal (MIM), 11-14
  - Metal-oxide-semiconductor field-effect transistor (MOSFET), 18-1, 18-2
  - Middlebrook's extra element theorem
    - parallel version, 24-38-24-40
    - series version, 24-40-24-43
  - Miller effect capacitance, 15-9-15-10
  - Modified nodal analysis (MNA), 25-19
  - Modified  $z$ -transform, 5-16
  - Multidimensional  $z$ -transforms, 5-15
- N**
- Narrow-sense Hurwitz polynomial (NHP), 9-5
  - Negative impedance converter (NIC), 14-8
  - Negative temperature coefficient (NTC) thermistor, 11-10
  - Network analysis
    - CCCS and VCVS gain, 22-34-22-35
    - circuit branch admittance, 22-27-22-30
    - circuit branch impedance, 22-30
    - circuit transadmittance
      - linear circuit, 22-31-22-32
      - voltage feedback amplifier, 22-33
    - circuit transimpedance, 22-31
    - driving point impedances
      - Blackman's formula, 22-37
      - critical circuit parameters, 22-35
      - transimpedance, 22-36
      - zero parameter, 22-36-22-37
  - functions
    - Cramer's rule, 22-3
    - definition, 22-1
    - inductor current, 22-5-22-6
    - Laplace transform, 22-9-22-10
    - modified nodal, 22-4
    - network stability, 22-8-22-9
    - output and input impedance, 22-2
    - output voltage and input voltage, 22-1
    - ratio of two polynomials, 22-6
    - roots of the numerator and denominator, 22-7
    - stability, 22-8-22-9
    - time-domain response, 22-10
    - transfer function, 22-3
  - fundamental concepts
    - branch linear network, 22-11-22-12
    - impedance and transimpedance, 22-14-12-15
    - nodal admittance matrix, 22-12-22-13
    - Norton equivalent circuit, 22-11-22-12
    - vector concept, 22-13
    - voltage gain, 12-15
  - Kron-Bode formula, 22-25-22-27
  - Kron's formula
    - bipolar junction transistor amplifier, 22-23
    - Bode's theory, 22-21
    - common emitter amplifier, 22-21-22-22
    - impedance inclusion, 22-15-22-16
    - I-O transfer characteristic node, 22-25
    - output voltage, 22-17-22-18
    - perturbed voltage gain, 22-18-22-19
    - return ratio, 22-26-22-27
    - Thévenin voltage and impedance, 22-16-22-17
    - transfer function and return ratio, 22-26
    - transfer function sensitivity, 22-20-22-21
    - sensitivity analysis, 22-39
    - transposed connection vector, 22-14
  - Network laws and theorems
    - basic circuit theory, 19-3
    - circuit analysis, 19-3-19-4
    - conductors and elements, 19-1, 19-2
    - current measurement, 19-2-19-3
    - cutset-loop circuit analysis
      - analogous problem, mesh analysis, 19-31
      - circuit graph, 19-31-19-32
      - example circuit, 19-39-19-41
      - failure, nodal analysis, 19-30-19-31
      - fundamental cutset and loop, 19-32
      - KCL equation, 19-32-19-34
      - KVL equation, 19-34
      - norator, 19-35-19-36
      - nullator and equivalent subcircuit, 19-37
      - passive element and equivalent circuits, 19-36-19-37
      - three-terminal/two-port element, 19-37-19-39
      - two-terminal element, 19-35-19-40

- Kirchhoff's current law (KCL)
    - circuit paths, 19-6-19-7
    - Gaussian surface, 19-5-19-6
    - illustration, 19-4-19-5
    - voltage changes, 19-7
  - Kirchhoff's voltage law (KVL)
    - circuit analysis, 19-8-19-9
    - circuit paths, 19-8
    - illustration, 19-7-19-8
  - linear circuit
    - KCL, 19-42-19-43
    - superposition and homogeneity condition, 19-43-19-44
  - maximum power transfer theorem
    - load resistance, 19-55-19-58
    - power vs. resistance, 19-55, 19-56
  - mesh analysis
    - circuit graph, 19-22-19-23
    - current sources, 19-26
    - deactivated current, 19-27
    - dependent source, 19-28-19-30
    - features and constraints, 19-27-19-28
    - independent source, 19-30
    - KCL, 19-24, 19-25
    - KVL, 19-24-19-26
    - mesh current, 19-24, 19-25
    - one-mesh circuit, 19-23
    - two-mesh circuit, 19-23-19-24
  - nodal analysis
    - deactivated circuit configuration, 19-14-19-15
    - dependent source, 19-16-19-17
    - differentiation and integration operators, 19-19-19-20
    - dynamic circuit analysis, 19-20-19-22
    - dynamic element relationships, 19-18-19-19
    - floating element, 19-10-19-12
    - independent voltage source, 19-13-19-14
    - node voltage concept, 19-9-19-10
    - nonessential node, 19-17-19-18
    - reference node, 19-10, 19-11
    - resistive circuit, 19-12-19-13
    - supernode and essential node, 19-15, 19-18
  - nonessential node, 19-17-19-18
  - reference node, 19-10, 19-11
  - resistive circuit, 19-12-19-13
  - supernode and essential node, 19-15, 19-18
  - Norton theorem
    - current calculation and power dissipation, 19-54-19-55
    - equivalent circuit, 19-51-19-52
    - mesh equation method, 19-52-19-53
    - reciprocity theorem statement, 19-58
    - verification, 19-58-19-59
    - superposition theorem current calculation, 19-46-19-47
    - deactivated sources, 19-44-19-46
  - Thévenin theorem
    - current calculation, 19-48-19-50
    - voltage determination, 19-50-19-51
    - voltage divider circuit, 19-47-19-48
  - voltage rise and drop, 19-7
  - voltmeter, 19-1-19-2
  - Nodal analysis
    - deactivated circuit configuration, 19-14-19-15
    - dependent source, 19-16-19-17
    - differentiation and integration operators, 19-19-19-20
    - dynamic circuit analysis, 19-20-19-22
    - dynamic element relationships, 19-18-19-19
    - floating element, 19-10-19-12
    - independent voltage source, 19-13-19-14
    - node voltage concept, 19-9-19-10
    - nonessential node, 19-17-19-18
    - reference node, 19-10, 19-11
    - resistive circuit, 19-12-19-13
    - supernode and essential node, 19-15, 19-18
  - Node admittance matrix (NAM) determinant, 25-5
  - Non ideal op-amp
    - common-mode rejection ratio (CMRR)
      - common-mode gain, 16-16-16-17
      - differential and noninverting configuration, 16-17
      - total output voltage, 16-17-16-18
    - electrical noise
      - amplifier noise, 16-21-16-22
      - circuit's noise performance, 16-23
      - white-noise voltage and density, 16-23-16-24
    - finite differential gain
      - frequency dependent gain, 16-11-16-12
      - noninverting configuration, 16-13
      - output saturation, 16-13-16-14
    - finite input impedance, 16-18-16-19
    - input bias currents
      - input offset current, 16-20
      - nonzero offset current, 16-20-16-21
      - nonzero output impedance, 16-19-16-20
    - offset voltage
      - output offset voltage, 16-15-16-16
      - transfer function, 16-14-16-15
      - power-supply rejection ratio, 16-18
  - Norton theorem, 24-31-24-32
    - current calculation and power dissipation, 19-54-19-55
    - equivalent circuit, 19-51-19-52
    - mesh equation method, 19-52-19-53
- ## O
- Ohm's law, 24-1-24-2
  - On-chip transformers
    - analytical transformer models capacitances, 12-18
    - stacked transformer, 12-17
    - tapped transformer, 12-16

- monolithic transformer
    - realizations
    - models and coupling
      - expression, 12-15-12-16
      - port applications, 12-16-12-7
  - Operational amplifier (op-amp)
    - BJT
      - analog computer, 15-21-15-22
      - classical architecture,
        - 15-22-15-23
      - features, 15-22
      - high-gain differential stage,
        - 15-23-15-24
      - second amplifier stage,
        - 15-24-15-26
      - specifications, 15-26-15-27
    - circuit schematic symbol,
      - 18-4, 18-5
    - current feedback op-amp (CFOA)
      - bipolar realization, 17-5
      - closed-loop gain, 17-3-17-4
    - CMOS compound device,
      - 17-5
    - frequency response,
      - 17-7, 17-9
    - macromodel, 17-2-17-3
    - open and close-loop
      - transimpedance,
        - 17-7, 17-9
    - output impedance
      - characteristics,
        - 17-7-17-8
    - schematics and layout plot,
      - 17-6-17-7
    - step response and harmonic
      - distortion, 17-11
    - total impedance, 17-3
    - voltage buffer performance,
      - 17-7
  - current-mode op-amp
    - closed-loop characteristics,
      - 16-35-16-36
    - current-mode op-amp
      - dynamics, 16-37-16-38
    - higher-order effects,
      - 16-38-16-40
  - ideal op-amp
    - circuit applications,
      - 16-3-16-8
    - comparators, 16-9-16-10
    - inverting amplifier
      - configuration,
        - 16-10-16-11
  - open-loop equivalent circuit,
    - 16-1-16-3
  - voltage op-amps, 16-3-16-11
  - nonideal op-amp
    - common-mode rejection
      - ratio (CMRR),
        - 16-16-16-18
    - electrical noise, 16-21-16-24
    - finite differential gain,
      - 16-11-16-14
    - finite input impedance,
      - 16-18-16-19
    - input bias currents,
      - 16-20-16-21
    - nonzero output impedance,
      - 16-19-16-20
    - offset voltage, 16-14-16-16
    - power-supply rejection ratio,
      - 16-18
  - voltage-mode op-amps
    - closed-loop frequency
      - response, 16-26-16-30
    - closed-loop transient
      - response, 16-30-16-32
    - current-mode op amps,
      - 16-32-16-34
    - open-loop voltage gain, 16-26
    - SPICE stimulation, 16-32
- Optical low-noise preamplifiers
- front-end noise sources
    - amplifier and resistor noise,
      - 17-18
    - PIN photodiode noise,
      - 17-17-17-18
  - receiver performance criteria
    - dynamic range, 17-21
  - equivalent input noise
    - current, 17-18-17-19
  - intersymbol interference,
    - 17-20-17-21
  - optical sensitivity,
    - 17-19-17-20
  - photodiode terminal, SNR,
    - 17-20
  - transimpedance (TZ) amplifiers,
    - 17-21-17-22
- P**
- 
- Parameter extraction method
- indefinite admittance matrix (IAM) approach
    - basics, 25-10-25-11
    - resistive circuit, 25-11-25-12
- interpolation method,
  - 25-16-25-17
- techniques and limitations,
  - 25-10
- two graph-based tableau
  - approach
    - determinants and cotree,
      - 25-13-25-14
    - element stamps, 25-12
    - matrices, 25-13, 25-15
    - tableau equation, 25-13
    - voltage and current graph,
      - 25-12, 25-14-25-15
- Paraunitary filter banks
- dilation equation application,
    - 6-63-6-64
  - infinite product convergence,
    - 6-64-6-65
  - multiresolution analysis
    - fast wavelet transform, 6-58
    - orthonormal multiresolution,
      - 6-57
    - power symmetric filter, 6-56
    - wavelet generation,
      - 6-57-6-58
  - orthonormal wavelet basis
    - Haar basis, 6-69
    - $L^2$  and pointwise
      - convergence, 6-67-6-68
    - Lawton's eigenfunction
      - condition, 6-68
    - nonorthonormal, 6-69-6-70
    - scaling and wavelet
      - functions, 6-68
  - parameterization, 6-27
  - wavelet tight frames, 6-70-6-71
- Partial fraction expansion (PFE)
- repeated linear factors, 3-31
  - repeated quadratic factors,
    - 3-31-3-32
  - simple linear factors, 3-27-3-30
  - simple quadratic factors,
    - 3-29-3-30
- Passive circuit elements
- active filter synthesis, SFG
    - bandpass passive filter, 21-9
    - Butterworth low-pass filter,
      - 21-7-21-9
    - Chebyshev low-pass
      - response, 21-10
    - component op-amp circuits,
      - 21-5-21-7
    - doubly terminated passive
      - filter, 21-4

- general ladder network, 21-4–21-5
  - leapfrog realization, 21-4–21-5
  - normalization, 21-10–21-11
  - capacitor
    - dielectric constant, 11-24
    - geometry, 11-34, 11-36–11-37
    - linear capacitor, 11-26–11-30
    - nonideal linear capacitor, 11-37–11-39
    - nonlinear capacitor, 11-31–11-33
    - power and quality factor, 11-25
    - properties, 11-33–11-35
    - $v'$  index, 11-25–11-26
  - inductor
    - air inductor, 11-45–11-49
    - circuit representation, 11-45
    - cored inductor, 11-49–11-60
    - definition, 11-63–11-64
    - functions and parameters, 11-44
    - fundamental observations, 11-42, 11-43
    - graphical symbols, 11-40
    - inductance, 11-40–11-42
    - International Standards, 11-63
    - magnetic core materials, 11-61, 11-62
    - magnetic material
      - measurements, 11-61, 11-63
    - nonlinearity, 11-60–11-61
    - physical irregularities, 11-63
    - qualifiers and attributes, 11-42–11-43
  - resistor
    - fixed resistor, 11-2–11-7
    - magnetic geometry, 11-17–11-20
    - magnetic properties, 11-11–11-17
    - nonideal linear resistor, 11-20–11-23
    - photoresistor and magnetoresistor, 11-11
    - thermistor, 11-10–11-11
    - variable resistor, 11-7–11-9
    - varistor, 11-9–11-10
  - semiconductor diode
    - depletion capacitances, 11-79–11-80
    - diode capacitances, 11-78–11-79
    - impurity profiles, 11-73, 11-74
    - nonlinear static I-V characteristics, 11-73–11-78
    - piecewise linear model, 11-83–11-84
    - as switch, 11-80–11-82
    - symbols, 11-84
    - temperature properties, 11-82–11-83
  - transformer
    - characteristics, 11-66–11-67
    - circuit model, 11-70–11-72
    - definition, 11-66, 11-72
    - ideal transformer model, 11-67–11-68
    - leakage and magnetizing inductances, 11-69–11-70
    - linear transformer model, 11-68–11-69
  - Phasor transforms
    - Euler's identity, 24-49
    - integration constant, 24-52
    - sine and cosine function, 24-50
  - Polar polymer dielectric capacitor, 11-32–11-33
  - Pole-zero analysis
    - linear system, LT
      - BIBO stability, 3-38–3-39
      - natural modes, 3-37–3-38
      - stability and natural modes, 3-39–3-41
    - ULT and BLT
      - general function,  $F(s)$ , 3-15
      - polynomial factorization, 3-16
      - ROC, 3-16–3-18
  - Port representations
    - feedback systems
      - Beta Network, 20-16–20-17
      - phase and gain margins, 20-15
      - Tow-Thomas biquad, 20-18–20-19
      - transfer function, 20-15
      - voltage-controlled voltage source (VCVS), 20-16
  - two-port network
    - bipolar transistor, 20-11–20-12
    - calculation, 20-7
    - Cramer's rule and circuit models, 20-10–20-11
    - hybrid parameters, 20-8–20-9
    - interconnections, 20-13–20-14
    - port voltages and current, 20-5
    - transmission parameters, 20-6, 20-14–20-15
    - $y$  parameters, 20-6–20-8
    - $z$  parameters, 20-6
  - Positive real function (PRF), 9-3
  - Positive temperature coefficient (PTC), 11-10
  - Power supply rejection ratio (PSRR), 15-27
  - Pulse-width modulation (PWM) amplifier
    - advantage and disadvantage, 15-35
    - architecture, 15-33, 15-34
    - configurations, 15-35–15-36
    - duty cycle, 15-33–15-34
    - IC amplifier, 15-3
  - Pulse-width modulation (PWM) IC amplifier, 15-3
- ## R
- Reactance function (RF), 9-3
  - Reactance Hurwitz polynomial (RHP), 9-7
  - Real-time filtering, Fourier block
    - block algorithms, 4-24
    - overlap-add processing, 4-23–4-24
    - overlap-save processing, 4-23
  - Reciprocity theorem
    - statement, 19-58
    - verification, 19-58–19-59
  - Resistive circuit element
    - bipolar NPN transistor, 13-5–13-6
    - op-amp, 13-6–13-7
    - photodiode, 13-4–13-5
    - tunnel diode, 13-5

- Resistor
- geometry
    - fail-safe resistor, 11-19-11-20
    - potentiometer, shape complication, 11-19
    - resistive element shape, 11-17-11-19
  - linear resistor
    - fixed resistor, 11-2-11-7
    - Ohm's law and types, 11-1-11-2
    - variable resistor, 11-7-11-9
  - nonideal linear resistor
    - noise, 11-20, 11-21
    - potentiometer, regulation curve, 11-21-11-23
    - rotational noise and CRV, 11-21
    - voltage coefficient of resistance (VCR), 11-20-11-22
  - nonlinear resistor
    - photoresistor and magnetoresistor, 11-11
    - thermistor, 11-10-11-11
    - varistor, 11-9-11-10
  - properties
    - ceramic substrate influence, 11-16-11-17
    - parameter comparison, 11-15-11-16
    - polymer resistor, 11-15
    - pyrolytic carbon resistor, 11-14
    - TCR, 11-11-11-17
    - thick film resistor, 11-14-11-15
    - thin film resistor, 11-13-11-14
  - RF low-noise amplifiers
    - cascode common source LNA
      - input matching, 17-15
      - noise figure, 17-16
      - voltage gain, 17-15-17-16
    - CMOS common-source LNA
      - CS input stage, noise, 17-13
      - gate-drain capacitance ( $C_{gd}$ ) effect, 17-14-17-15
      - input impedance matching, 17-12-17-13
      - simplified analysis, 17-12
      - voltage amplifier, inductive load, 17-14
    - gain, 17-10-17-12
    - input impedance matching and linearity, 17-12
    - noise, 17-8
  - RF passive IC components
    - fractal capacitors
      - boost factor vs. horizontal spacing, 12-7
      - bottom-plate parasitic capacitance, 12-5-12-6
      - fractal dimension, 12-4-12-5, 12-6
      - high-density capacitor, 12-2 interdigitated capacitor, 12-7-12-8
      - lateral flux capacitors, 12-2-12-3
      - parallel-plate and MOS, 12-1-12-2
      - quality factor and lateral spacing, 12-7
      - three-dimensional representation, 12-5, 12-6
      - woven structure, 12-8
    - on-chip transformers, 12-4
      - analytical transformer models, 12-16-12-19
      - monolithic transformer realizations, 12-15-12-17
    - spiral inductors
      - noise coupling, 12-8-12-9
      - planar spiral inductors, 12-11-12-14
      - substrate effects, 12-9-12-11
  - RF power amplifier
    - classification, 17-24-17-25
    - PA requirements, 17-24
    - practical considerations, 17-27
- S**
- Scattering Hurwitz polynomial (SHP), 9-5-9-6
  - Scattering matrix, circulator, 14-12-14-14
  - Second-order circuits, time domain analysis
    - network characterization, 26-17
    - transfer function, 26-11-26-12
    - transient and steady-state responses, 26-15-26-17
    - zero-input response, 26-13-26-14
    - zero-state response, 26-14-26-15
  - Semiconductor diode
    - depletion capacitances, 11-79-11-80
    - diode capacitances, 11-78-11-79
    - impurity profiles, 11-73, 11-74
    - nonlinear static I-V characteristics, 11-73
      - forward I-V diode characteristics, 11-75, 11-77-11-78
      - p-n junction equation, 11-74-11-76
      - reverse I-V characteristics, 11-75, 11-78
    - piecewise linear model, 11-83-11-84
      - as switch, 11-80-11-82
    - symbols, 11-84
    - temperature properties, 11-82-11-83
  - Sequence of expressions (SoE), *see* Hierarchical methods
  - SFG, *see* Signal flow graph
  - Short-time Fourier transform (STFT)
    - definition, 6-16-6-17
    - filter impulse response, 6-17
    - Gabor window, time-frequency resolution, 6-18-6-19
    - invertibility, 6-47-6-48
    - limitations, 6-30
    - orthonormality, 6-48-6-49
    - shifted filters, analysis bank, 6-18
    - time-frequency localization, 6-49-6-50
    - vs. wavelet transform
      - mathematical issues, 6-22
      - Morlet wavelet, 6-21-6-22
      - signal analysis, 6-20
      - time-frequency tiling scheme, 6-19-6-20
  - Signal converters
    - circulator, 14-12-14-15
      - 2-port circulator, 14-13
      - 3-port circulator, 14-13-14-14
      - nullator and norator, 14-14, 14-15
      - nullor, 14-14-14-15
      - terminated 2-port network, 14-12-14-13
    - current negative impedance converter, 14-11-14-12

- definition, 14-15
- gyrator, 14-8–14-10
  - Antoniou's circuit, 14-9–14-10
  - ideal 2-port gyrator, 14-8–14-9
- network ports, 14-7–14-8
- voltage negative impedance converter, 14-11
- Signal flow graphs
  - active filter, filter transfer function
    - differential-Input op-amp circuit, 21-17
  - dummy branche insertion, 21-13
  - four op-amp circuit, 21-18–21-19
  - gain function, 21-12–21-13
  - lowpass filter specifications, 21-19
  - Mason's gain formula, 21-12
  - RC-op-amp circuits, 21-14–21-15
  - state variable biquad, 21-19–21-20
  - transfer voltage ratio, 21-11
  - two op-amp circuit
    - realizations, 21-15–21-16
- active filter synthesis, passive filter circuit
  - bandpass passive filter, 21-9
  - Butterworth low-pass filter, 21-7–21-9
  - Chebyshev low-pass
    - response, 21-10
  - component op-amp circuits, 21-5–21-7
  - doubly terminated passive filter, 21-4
  - general ladder network, 21-4–21-5
  - leapfrog realization, 21-4–21-5
  - normalization, 21-10–21-11
- adjacency matrix, directed graph
  - definition, 8-1
  - edge weight, 8-4
  - permutation, 8-2–8-3
- Coates' gain formula
  - coefficient matrix, 8-7–8-8
  - $n \times n$  matrix, 8-6–8-7
  - nonsingular matrix, 8-5
  - topological formula, 8-4
- definition, 25-8
- formulation, 25-9, 25-10
- Harary theorem, 8-3–8-4
- linear network
  - construction, 21-1–21-2
  - network branches, 21-1
- Mason's gain formula
  - feedback loops, 8-10
  - $j$  self-loops, 8-9
  - Mason graph, 8-8–8-9
  - Mason's SFG, 25-7–25-8
- Similarity transformation, 1-12–1-14
- Singular-value decomposition (SVD), 1-17
- Sinusoidal steady state analysis
  - AC circuit power
    - average power and RMS values, 24-65–24-66
    - average power delivered, 24-71
    - input impedance, 24-64
    - load impedance, 24-70–24-71
    - maximum average power, 24-72–24-73
    - power factor (PF), 24-63
    - power triangle, 24-67
    - sinusoidal sources, 24-62–24-63
  - network transfer function, 24-46–24-47
  - output voltage, 24-48
  - phase lead and lag, 24-55–24-57
  - phasor and network, 24-53–24-55
  - RC and RL network, 24-57–24-59
  - resonance
    - parallel resonant circuit, 24-60–24-61
    - series resonant circuit, 24-61–24-62
  - steady-state output voltage, 24-49
  - transient and steady-state response, 24-45
- Sinusoids, 26-3
- Spiral inductors
  - noise coupling, 12-8–12-9
  - planar spiral inductors
    - current sheet approximation, 12-3–12-14
- data-fitted monomial
  - expression, 12-14, 12-15
- layouts, 12-11–12-12, 12-13
- modified Wheeler formula, 12-12–12-3
- substrate effects
  - patterned ground shield (PGS), 12-10–12-11
  - physical model, 12-9–12-10
- State transition matrix
  - complete response, 27-20–27-21
  - Jordan canonical form, 27-16
  - Laplace transform technique, 27-17
  - normal mode approach, 27-18
  - parallel RLC circuit, 27-17
  - similarity transformation
    - method, 27-19
  - zero-input response, 27-21
- State-variable techniques
  - complete response, 27-20–27-21
  - concept of states
    - capacitive loop, 27-2–27-3
    - definition, 27-1
    - simple RC circuit, 27-2
  - network topology
    - capacitive tree-branch voltages, 27-8
    - first-order differential equation, 27-3
    - inductive link current, 27-8
    - KCL and KVL, 27-4
    - order of complexity, 27-1–27-2
    - resistive link currents, 27-7
    - state equations, 27-5–27-6
  - state transition matrix
    - Jordan canonical form, 27-16
    - Laplace transform technique, 27-17
    - normal mode approach, 27-18
    - parallel RLC circuit, 27-17
    - similarity transformation
      - method, 27-19
    - zero-input response, 27-21
- Superposition theorem
  - current calculation, 19-46–19-47
  - deactivated sources, 19-44–19-46

- Symbolic analysis
- approximate symbolic analysis
  - bipolar cascode stage, 25-21–25-23
  - classification, 25-20–25-21
  - error criteria, 25-21
  - determinant decision diagrams (DDD)
    - matrix determinant and representation, 25-24–25-25
    - nodal analysis, 25-23–25-24
    - vertex and vertex ordering, 25-24
  - frequency domain analysis, 25-3
  - hierarchical methods
    - advantage, 25-17, 25-18
    - bipolar cascode stage, 25-19–25-20
    - modified nodal analysis and NAM, 25-19
    - resistance ladder network, 25-17–25-18
    - topological analysis, 25-18
  - illustration, 25-1–25-2
  - time domain analysis
    - fully symbolic, 25-25
    - problems and limitation, 25-25
    - semisymbolic, 25-26
  - traditional methods
    - cancellation-free equation, 25-4–25-5
    - interpolation method, 25-16–25-17
    - parameter extraction method, 25-10–25-16
    - RLC<sub>m</sub> circuit and term cancellations, 25-4
    - signal flowgraph method (SFG), 25-7–25-9, 25-10
    - tree enumeration methods, 25-5–25-7
- Symmetric magnitude response
- analog 2-D filter
    - quadrantal and octagonal symmetry, 10-28–10-29
    - rotational and diagonal symmetry, 10-29
    - transfer function, 10-27
  - bandpass filter
    - MATLAB optimization, 10-32
    - specifications, 10-31–10-32
  - bandstop filter
    - coefficients and specification, 10-35
    - contour and 3-D magnitude plots, 10-36
  - digital filters
    - quadrantal and octagonal symmetry, 10-29–10-30
    - rotational and diagonal symmetry, 10-30
  - high-pass filter
    - coefficients and specification, 10-34
    - contour and 3-D magnitude plots, 10-35
  - low-pass filter
    - coefficients and specification, 10-33
    - contour and 3-D magnitude plots, 10-34
  - magnitude-squared functions, 10-16
- Symmetry applications
- 2-D Fourier transform
    - continuous-time continuous-frequency case, 10-7–10-8
    - continuous-time discrete-frequency case, 10-8
    - discrete-time continuous-frequency case, 10-9
    - discrete-time discrete-frequency case, 10-9–10-10
  - 2-D magnitude response
    - continuous-time frequency response, 10-15
    - discrete-time frequency response, 10-15–10-16
    - magnitude-squared functions, 10-16
  - 2-D polynomials determination
    - diagonal symmetry, 10-25–10-26
    - fourfold rotational symmetry, 10-26
    - octagonal symmetry, 10-27
    - quadrantal symmetry, 10-21–10-25
  - analog 2-D filter stability, magnitude response
    - quadrantal and octagonal symmetry, 10-28–10-29
    - rotational and diagonal symmetry, 10-29
    - transfer function, 10-27
  - digital filter stability, magnitude response
    - quadrantal and octagonal symmetry, 10-29–10-30
    - rotational and diagonal symmetry, 10-30
- FFT
- one dimensional, 10-11–10-12
  - symmetrical decomposition, 10-14
  - two dimensional, 10-12–10-14
- filter design, magnitude response
- bandpass filter, 10-31–10-33
  - bandstop filter, 10-35–10-36
  - high-pass filter, 10-34–10-35
  - low-pass filter, 10-33–10-34
  - objective function, 10-29–10-30
  - transfer function, 10-29
- magnitude-squared function
- polynomial P, 10-19–10-20
  - quadrantal symmetry, 10-20
  - spectral forms, 10-20–10-21
- polynomial operations
- anti-self-paraconjugate polynomial, 10-18–10-19
  - paraconjugate operation, 10-17
  - self-paraconjugate polynomial, 10-17–10-18
- T-ψ symmetries
- basic symmetries, 10-4–10-5
  - quadrantal and diagonal symmetry, 10-5–10-6
  - rotational and octagonal symmetry, 10-6–10-7
- T**
- Taylor series, 3-23
- Tellegen theorem
- 2-port network, 7-21–7-22
  - adjoint elements, 7-23–7-24
  - open-circuit voltage ratio, 7-24
  - voltage and current change, 7-22
- Temperature coefficient of capacitance (TCC), 11-24



- Tensor
  - basis tensors
    - finite-dimensional vector spaces, 2-5-2-8
  - Kronecker product, 2-8
  - tensor product
    - arbitrary bilinear operator, 2-4
    - isomorphism, 2-5
- Terminal representation
  - four-terminal network
    - first application, 20-3
    - passive circuit, 20-1-20-2
    - second application, 20-4
  - indefinite admittance matrix, 20-3
  - network analysis, 20-5
  - nodal admittance matrix, 20-2-20-3
- Thévenin theorem
  - application, 24-28-24-29
  - current calculation, 19-48-19-50
  - dependent sources, 24-24-24-25
  - impedance, 24-26
  - source transformation, 24-29-24-30
  - subnetworks, 24-24
  - voltage determination, 19-50-19-51
  - voltage divider circuit, 19-47-19-48
- Third-order intercept point (TOI), 15-5
- Time domain analysis
  - first-order circuits
    - network time constant, 26-10
    - transfer functions, 26-6-26-7
    - transient and steady-state responses, 26-9-26-10
    - zero-input response, 26-7-26-8
    - zero-state response, 26-8-26-9
  - second-order circuits
    - network characterization, 26-17
    - transfer function, 26-11-26-12
    - transient and steady-state responses, 26-15-26-17
    - zero-input response, 26-13-26-14
    - zero-state response, 26-14-26-15
- signal types
  - causal circuit, 26-4
  - eternal signals, 26-3-26-4
  - impulse, 26-2-26-3
  - periodic and aperiodic waveforms, 26-4-26-6
  - ramp function, 26-2
  - sinusoids, 26-3
  - unit step function, 26-1-26-2
- z-Transform
  - discrete-time FT, 5-3-5-4
  - generating function, 5-2
  - inverse z-transform
    - contour integration, 5-5-5-7
    - inspection method and power series expansion, 5-8
    - partial fraction expansion, 5-7-5-8
  - linear time-invariant systems
    - one-sided z-transform, 5-14
    - system transfer function, 5-13-5-14
  - properties
    - ROC, 5-8-5-9
    - transform, 5-9-5-10
    - z-domain convolution, 5-10-5-12
  - ROC, unit circle, 5-3
  - two-sided z-transform, 5-2
  - variations
    - chirp z-transform algorithm, 5-17
    - modified z-transform, 5-16
    - multidimensional z-transforms, 5-15
- Transform domain adaptive filter (TDAF)
  - adaptive tap vector, 4-25
  - autocorrelation matrix, 4-24-4-25
  - characteristics, 4-26-4-27
  - filter output and LMS adaptive algorithm, 4-24
  - Karhunen-Loe've transform (KLT), 4-26
  - power, 4-25-4-26
  - transformed outputs, 4-25
- Transformer
  - characteristics, 11-66-11-67
  - definition, 11-66, 11-72
  - ideal transformer model, 11-67-11-68
- nonideal transformer
  - circuit model, 11-70-11-72
  - leakage and magnetizing inductances, 11-69-11-70
  - linear transformer model, 11-68-11-69
- Transimpedance (TZ) amplifiers, 17-21-17-22
- Tree enumeration methods
  - augmented circuit, 25-6-25-7
  - circuit construction, 25-5-25-6
  - NAM determinant and cofactors, 25-5
- Tree-structured filter banks
  - analysis and synthesis bank, 6-28
  - analysis filter response, 6-28-6-29
- Two-dimensional (2-D) digital filters
  - 2-D symmetries
    - centrosymmetry, 10-13
    - quadrantal symmetry, 10-14
  - magnitude response symmetry
    - continuous-time frequency response, 10-15
    - discrete-time frequency response, 10-15-10-16
    - magnitude response, 10-16
  - symmetry
    - anti-self-paraconjugate polynomial, 10-18-10-19
    - magnitude-squared function, 10-19-10-21
    - octagonal, 10-6-10-7
    - paraconjugate operation, 10-17
    - quadrantal and diagonal, 10-5-10-6
    - reflection and rotational, 10-4-10-5
    - self-paraconjugate polynomial, 10-17-10-18
    - symmetry-based 1-D FFT, 10-11-10-12
- T operations, 10-3
- T- $\psi$  operations, 10-2-10-3
- $\psi$ -operation, 10-4
- two-dimensional (2-D) Fourier transform
  - continuous-time continuous-frequency, 10-7-10-8

- discrete-time continuous-frequency, 10-9
  - discrete-time discrete-frequency, 10-9-10-10
  - Two graph-based tableau approach
    - determinants and cotree, 25-13-25-14
    - element stamps, 25-12
    - matrices, 25-13, 25-15
    - tableau equation, 25-13
    - voltage and current graph, 25-12, 25-14-25-15
  - Two-port network
    - bipolar transistor, 20-11-20-12
    - calculation, 20-7
    - Cramer's rule and circuit models, 20-10-20-11
    - hybrid parameters, 20-8-20-9
    - interconnections, 20-13-20-14
    - port voltages and current, 20-5
    - transmission parameters, 20-6, 20-14-20-15
    - $y$  parameters, 20-6-20-8
    - $z$  parameters, 20-6
  - Two-variable polynomial
    - 1-D complex plane, 9-3
    - 2-D biplane, 9-4
    - nonessential singularities second kind (NSSK), 9-4
- U**
- Unilateral Laplace transforms
    - direct computation, 3-11-3-15
    - operational properties, 3-18-3-22
- V**
- Variable resistor
    - electric circuit, 11-7, 11-8
    - tapers, 11-9
    - types, 11-7-11-9
  - Vector spaces over fields
    - field  $F$ , properties, 1-2
    - $F$ -vector space, 1-2-1-3
    - $n$ -dimensional vector space, 1-3-1-4
  - Very strict Hurwitz polynomial (VSHP), 9-6
  - Voltage-controlled current source (VCCS)
    - circuit implementation, 14-2-14-3
    - circuit schematic symbol, 18-3
    - equivalent circuit, MOSFET, 14-1-14-2
    - SPICE format, 14-2, 14-4
  - Voltage-controlled voltage source (VCCVS), 14-3
    - circuit schematic symbol, 18-1-18-3
    - dynamic model, op-amp, 13-9, 13-10
    - SPICE format and circuit implementation, 14-4
  - Voltage-dependent resistor (VDR), 11-9
  - Voltage inversion negative impedance converter (VNIC), 14-11
  - Voltage-mode op-amps
    - closed-loop frequency response
      - closed-loop small-signal bandwidth, 16-28
      - crossover frequency, 16-29
      - feedback factor, 16-27
    - closed-loop transient response, 16-30-16-32
    - current-mode op amps, 16-32-16-34
    - open-loop voltage gain, 16-26
    - SPICE stimulation, 16-32
  - 2-V very strict Hurwitz polynomial (VSHP), 9-10-9-11
- W**
- Walsh-Hadamard transform (WHT), 4-20-4-21
  - Wavelet transform (WT) technique
    - basis functions, 6-10
    - digital filter banks
      - basis function, 6-29-6-30
      - half-band filter, 6-27
      - paraunitary filter banks, parametrization, 6-27
      - paraunitary properties, 6-25-6-27
      - polyphase representation, 6-24-6-25
      - subband construction, 6-22-6-24
      - tree-structured system, 6-28-6-29
      - two-channel filter bank, 6-22
    - filter banks
      - synthesis and reconstruction, 6-13-6-14
      - time-frequency representation, 6-13
      - wavelet function design, 6-14-6-15
    - Fourier basis, 6-15
    - Haar wavelet basis, 6-11-6-12
    - Hilbert space frame
      - arbitrary vector representation, 6-44
      - definition, 6-44
      - dual frame and sequence, 6-47
      - frame operator, 6-46
      - Riesz basis, 6-44-6-45
      - tight frame, 6-46
    - ideal bandpass wavelet
      - Fourier transform, 6-5-6-6
      - frequency axis splitting, 6-6-6-7
      - impulse response, 6-8
      - vs. low-pass, 6-5-6-6
    - $L^1$  and  $L^2$  signal space
      - convolution integral, 6-36-6-37
      - Lebesgue integrals, 6-31-6-32
      - $L^p$  signal, 6-32-6-34
    - $L^2$  functions, 6-8-6-10
    - multiresolution and wavelets
      - continuous time filter banks, 6-59-6-60
      - frequency domain, 6-51
      - ideal filter, 6-51-6-52
      - paraunitary filter banks, 6-56-6-58
      - time domain, 6-50
    - notations and acronyms, 6-3
    - octave-band splitting scheme, 6-8, 6-9
    - orthogonal projections, 6-10
    - orthonormal wavelet, 6-71-6-72
    - short-time Fourier transform
      - definition, 6-16-6-17
      - filter impulse response, 6-17
      - Gabor window, time-frequency resolution, 6-18-6-19
      - invertibility, 6-47-6-48
      - limitations, 6-30
      - orthonormality, 6-48-6-49

- shifted filters, analysis bank,
    - 6-18
  - time–frequency localization,
    - 6-49–6-50
  - wavelet regularity
    - ninth-order FIR filter,
      - 6-73–6-74
    - smoothness and Hölder regularity index, 6-74
  - time-domain decay
    - and regularity,
      - 6-77–6-78
    - two-scale dilation equation,
      - 6-72–6-73
  - wavelet transforms
    - coefficient computation,
      - 6-10–6-11
    - CWT and DWT, 6-15
  - definition, 6-11
  - frequency response, 6-16
  - properties, 6-12–6-13
  - vs. short-time Fourier transform, 6-19–6-22
- Wideband amplifiers
- composite stages, 15-27–15-28
  - feedback cascades,
    - 15-28–15-29