
Contents

PREFACE

ix

CHAPTER ONE

FUNDAMENTALS OF CONTROL 1

- 1-1 Meaning of Control 1
- 1-2 Manual Control 1
- 1-3 Semiautomatic Control 2
- 1-4 Automatic Control 3
- 1-5 Basic Concepts of Automatic Motor Control 4

CHAPTER TWO

A BRIEF REVIEW OF MOTORS 10

- 2-1 Choosing Motors 10
- 2-2 Construction of AC Motors 10
- 2-3 Electrical and Mechanical Characteristics of Motors Applications of Single-Phase Motors 12
14
- 2-5 Induction Motors 20
- 2-6 Reversing Polyphase Motor 21
- 2-7 Different Classes of Polyphase Motors 22
- 2-8 Multispeed Polyphase Motors 22
- 2-9 Applications and Connections for Two-Speed Motors 23
- 2-10 Wound-Rotor Motors 23
- 2-11 Synchronous Motors 25
- 2-12 Direct Current Motors 25
- 2-13 Working Fields and Corrective Fields 28
Dynamic Braking 28

CHAPTER THREE

CONTROL OF MOTOR STARTING 32

- 3-1 Motor Starting 32
- 3-2 Acceleration Control 32
- 3-3 Starting Wound-Rotor Motors 32
- 3-4 Starting Synchronous Motors 34
- 3-5 Selection of Starting Controllers 36
- 3-6 Overload Protection 37
- 3-7 Short-Circuit Protection 38
- 3-8 Limit Protection 38
- 3-9 Interlocking Protection 38
- 3-10 Speed-Control 39
- 3-11 Undervoltage Protection and Release 39
- 3-12 Phase-Failure Protection 39
- 3-13 Reverse-Phase Protection 40
- 3-14 Incomplete-Sequence Protection 40
- 3-15 Stopping the Motor 40
- 3-16 Starting DC Motors 41
- 3-17 Speed Control of DC Motors 41

CHAPTER FOUR

CONTROL COMPONENTS 44

- 4-1 Switches and Breakers 44
- 4-2 Contactors 44
- 4-3 Relays 45
- 4-4 Motor Starters 49
- 4-5 Manual Motor Starters 49
- 4-6 Automatic Motor Starters 50
- 4-7 Full-Voltage Starters 51
- 4-8 Reduced-Voltage Starters 51

	Speed-Control Starters	53	7-3	Sequence-Control Circuits	81
4-10	Combination Starters	54	7-4	Forward and Reverse Motor Control Circuit	82
4-11	Reversing Starters	54	7-5	Motor Control Circuit with Limit Switches	83
4-12	Wound-Rotor Motor Starters	56	7-6	Jogging Control	84
4-13	Synchronous Motor Starters	56	7-7	Automatic Plugging Control	85
4-14	Series Motor Starters	57	7-8	Three-Speed Motor Control	85
4-15	Direct-Current Shunt and Compound Motor Starters	58	7-9	Sequence-Speed Control	86
	Direct-Current Reversing Starters	58	7-10	Acceleration Control	87
	Automatic DC Controllers	59	7-11	Preselected Speed Control	89
			7-12	Chilled-Water Air-Conditioning System Control	91
CHAPTER FIVE					
PILOT DEVICES		61	CHAPTER EIGHT		
5-1	Descriptions of Pilot Devices	61	ANALYSIS OF CONTROL CIRCUITS		
5-2	Float Switches	61	8-1	Basic Procedures	96
5-3	Pressure Switches	62	8-2	Forward and Reverse Control	96
5-4	Limit Switches	63	8-3	Start, Stop, and Jog Operation	97
5-5	Flow Switches	64	8-4	Dynamic Braking	98
5-6	Thermostats	64	8-5	Wye-Delta Controller	99
5-7	Pushbutton Stations	66	8-6	Primary-Resistance Reduced-Voltage Starter	100
5-8	Plugging Switches	66	8-7	Lockout Circuit	102
5-9	Time Clocks	67	8-8	Direct-Current Control Circuits	102
CHAPTER SIX					
CONTROL-CIRCUIT DIAGRAMS		69	8-9	Accelerating Contactors	104
6-1	Symbols	69	8-10	Dynamic-Braking Contactor	107
6-2	Diagrams	71	8-11	Reversing Contactors	109
6-3	Wiring Diagrams	71	8-12	Antiplugging Relay	110
6-4	Schematic Diagram	72	8-13	Plugging Relay	110
6-5	Developing a Ladder Program	73	CHAPTER NINE		
6-6	Adding Circuit Elements	75	MAINTAINING CONTROL EQUIPMENT		
CHAPTER SEVEN					
DEVELOPMENT OF CONTROL CIRCUITS		78	9-1	General Procedure	114
7-1	Types of Control Circuits	78	9-2	Maintenance of Motor Starters	115
7-2	Expanding an Existing Circuit	78	9-3	Causes of Trouble	115
			9-4	Maintenance of Relays	115
			9-5	Maintenance of Pilot Devices	116

Maintenance of Brakes and Clutches	116	12-12 Silicon-Controlled Switch	140
		12-13 Gate Turn-Off Switch	141
		12-14 Triac	142
		12-15 Diacs	143
		12-16 Photodiode and Light-Emitting Diode	144
		12-17 Darlington Amplifier	144
		12-18 Programmable Unijunction Transistor	144
		12-19 SUS, SBS, and ASBS	145
		12-20 Solid-State Motor Control with Time-Delay Turn-Off	145
		12-21 Solid-State Motor Control with Overload Protection	146
		12-22 Solid-State AC Motor Speed Control (FHP Parajust)	147
		12-23 Soft Starts for Polyphase Motors with Solid-State Motor Control	148
		12-24 Super Start Solid-State Controller	148
		12-25 Solid-State Motor Control by Westinghouse	150
		12-26 Solid-State Motor Control by General Electric	153
		12-27 Regulator	154
		12-28 SCR Firing Circuit	155
CHAPTER TEN		CHAPTER THIRTEEN	
TROUBLESHOOTING CONTROL CIRCUITS		BASIC CONCEPTS OF STATIC-AND-LOGIC CONTROL	
	118		160
10-1 General Procedure	18	13-1 Basic Concepts of Static-and-Logic Control	160
10-2 Troubleshooting Control Components	120	13-2 Essentials of Static-and-Logic Control	161
Step-by-Step Procedure	120	13-3 Development of Logic Circuits	163
		13-4 Switching Logic and Boolean Algebra	164
		13-5 Logic Polarity	165
		13-6 Boolean Algebra and Circuit Simplification	166
		13-7 Fundamental Laws and Axioms of Boolean Algebra	167
CHAPTER ELEVEN			
MOTOR CONTROL CENTERS			
	122		
11-1 History of Motor Control Centers	122		
11-2 Motor Control Center Starters	122		
11-3 Power Distribution	123		
11-4 Classes of Control Centers	124		
11-5 Some Common and Important Terms	124		
11-6 Control Diagrams	125		
CHAPTER TWELVE			
SOLID-STATE MOTOR CONTROL			
	128		
12-1 Introduction to Solid-State Motor Control	128		
12-2 Basic Semiconductor Theory	129		
12-3 Diodes and Rectifiers	130		
12-4 Characteristic Curves	131		
12-5 Zener Diodes	131		
12-6 Thyrectors	132		
12-7 Tunnel Diodes	133		
12-8 NPN and PNP Transistors	134		
12-9 Unijunction Transistors	137		
12-10 Silicon-Controlled Rectifiers	137		
12-11 Light-Activated Silicon-Controlled Rectifier	140		

15-10	Shift Register	243	Applications in Process	
15-11	Logic Functions and Auxiliary Devices	246	Control	287
15-12	Developing Schematic Diagrams and Wiring Charts	246	16-6 Theory and Applications of Programmable Controllers	287
5-13	Summary of Allen Bradley Solid-State Logic Control	246	16-7 Eagle Signal EPTAK 200 Programmable Controller	288
15-14	Cutler-Hammer LSL Logic	249	16-8 Modicon Micro 84 and 584 Programmable Controllers	291
15-15	Designing an LSL Logic System	251	16-9 The TI 510 Programmable Controller	294
15-16	Master Control for LSL Logic Systems	255	16-10 Programming the TI 510 Programmable Controller	294
15-17	Implementing Internal Sequencing with LSL	257	16-11 The PC 700 and PC 900—Westinghouse Programmable Controllers	303
15-18	Input Circuits for LSL Logic Systems	258	16-12 Westinghouse CRT Program Loader NLPL 780	305
15-19	Output Circuits for LSL Logic Systems	259	16-13 The Min Loader Provides CRT-Type Programming and Monitoring	305
15-20	Power Circuits in LSL Logic Systems	260	16-14 Using Westinghouse Mini Loader NLPL 789	308
5-21	Summary of LSL Logic Applications	260	16-15 CRT Programmers and Their Applications in Programming, Editing, Monitoring, and Diagnostic Operations	312
5-22	Square D NORPAK Logic Control Systems	261	16-16 Ladder Diagram Programming of the Programmable Controller	312
5-23	Installation, Maintenance, and Troubleshooting Techniques	278	16-17 Example of Allen Bradley Programming Control Programming	313
15-24	Electrical Noise and Its Elimination	281		
15-25	Relay Conversions	282		

CHAPTER SIXTEEN**PROGRAMMABLE CONTROLLERS 285**

16-1	History of Programmable Controllers	285
16-2	Features of Programmable Controllers	285
16-3	Difference Between Programmable Controllers and Computers	286
16-4	Programming Methods for Programmable Controllers	286
16-5	Smart I/Os and Their	

CHAPTER SEVENTEEN**MICROPROCESSORS AND PROGRAMMABLE LOGIC FOR MOTOR CONTROL 319**

7-	Description of a Microprocessor	319
17-2	Microprocessors Versus Microcomputers	320
17-3	Microprocessor Programs	320

	Microprocessor Control Section	321	17-14 State Machine Control for Microprocessors	334
17-5	The Arithmetic/Logic Unit	322	7-15 Programmable Logic Devices	334
17-6	The Programming Process	322		
17-7	Algorithms and Flowcharts	322		
17-8	Microprocessor Applications	323	CHAPTER EIGHTEEN	
17-9	Binary and Hexadecimal Numbers	324	INDUSTRY OUTLOOK	340
17-10	Stepping Relays and Rotary Drum Switches	327	18-1 Numerical Control	340
	Stepping Relay Illustrative Example	328	18-2 How Numerical Control is Used in Industry	340
	Hex Numbers as Instructions for Microprocessors	331	18-3 Skills Needed by Industrial Technicians	341
	SDK-85 Microprocessor Board	334	INDEX	345