Ref.539.2 HOE

Table of Contents

Foreword xi
Preface xii
Acknowledgements xvi

PART 1 TWO-DIMENSIONAL TLM THEORY

Chapter 1 The Theoretical Foundations of the TLM Method 1

1.1 Introduction 1
1.2 Historical Background 2
1.3 Huygens' Principle in Discrete Form 3

Chapter 2 Wave Propagation in Two-Dimensional Shunt and Series Connected TLM Networks 6

2.1 Introduction 6
2.2 Scattering of Voltage Impulses at Shunt Nodes 7
2.3 Wave Properties of Infinitesimally Fine Shunt Networks 10
2.4 Wave Properties of Series-Connected TLM Networks 13

Chapter 3 Modelling of Linear Media 15

3.1 Introduction 15
3.2 Modelling of Free Space 15
3.3 Modelling of Lossy Homogeneous Media 18
3.4 Modelling of Lossy Inhomogeneous Media 22
3.4.1 Introduction of Shunt Stubs 22
3.4.2 Impulse Scattering at Stub-Loaded Shunt Nodes 23
3.4.3 Wave Properties of Stub-Loaded Shunt Networks 24
3.4.4 Introduction of Series Stubs 27
3.4.5 Impulse Scattering at Stub-Loaded Series Nodes 28
3.4.6 Wave Properties of Stub-Loaded Series Networks 29
3.4.7 Dielectric Interface Conditions 30

ห้องสมุดกลางวิทยาศาสตร์บริการ

Chapter 4 Modelling of Boundaries 34

4.1 Introduction 34
4.2 Modelling of Boundaries by a Real Impulse Reflection Coefficient 35
4.2.1 Lossless Non-Dispersive Boundaries 36
4.2.2 Lossy Boundaries 38
4.2.2.1 Absorbing Boundary for TEM Waves 38
4.2.2.2 Narrowband Matched Load for TE-Waves 40
4.2.2.3 Lossy Conducting Walls 40
4.3 Modelling of Boundaries by a Johns Matrix 41
4.3.1 The Discrete Time Domain Green's Function or "Johns Matrix" 41
4.3.2 The Discrete Green's Function for Node Voltages 42
4.3.3 The Discrete Green's Function for TLM Impulses 44
4.3.4 Response of a TLM Substructure to Arbitrary Excitation 46
4.3.5 Physical Interpretation of the Johns Matrix 49
4.3.6 Examples of Johns Matrix Boundaries 50
4.3.6.1 Interface Between TLM Substructures 50
4.3.6.2 Wideband Absorbing Boundaries for Non-TEM Waves 52
4.3.6.3 Frequency Dispersive Reactive Boundary in the Time Domain 54

Chapter 5 Modelling of Nonlinear Materials and Devices 57

5.1 Introduction 57
5.2 Modelling of Varactor Diodes with Losses 58
5.3 Modelling of Nonlinear Active Diodes 63
5.3.1 Principle of General Lumped Element Modelling in TLM 63
5.3.2 Modelling of an Active Diode 67
5.3.3 Modelling of the Nonlinear Negative Conductance 69

Chapter 6 Excitation and Response of a TLM Network 71

6.1 Introduction 71
6.2 Impulsive Excitation of a TLM Network 71
6.3 Arbitrary Excitation in Space and Time 75
6.4 Modelling of Calibrated Impulse Voltage Sources 76
6.5 Computation of Fields and Field Distributions 77
6.6 Computation of Impedances and Power Flow 79
6.7 Extraction of Scattering Parameters from the TLM Impulse Response 80
6.8 Reversal of Electromagnetic Processes in Time 82

Chapter 7 Errors and Their Correction 86

7.1 Introduction 86
7.2 Truncation Error 86
7.3 Velocity Error 88
7.3.1 Dispersion Characteristics of Two-Dimensional TLM Networks 89
7.3.1.1 Dispersion Characteristics of Lossless Networks without Stubs 89
7.3.1.2 Dispersion Characteristics of Lossy Networks without Stubs 93
7.3.1.3 Dispersion Characteristics of Stub-Loaded Networks 93
7.3.2 Correction of the Velocity Error 98
7.4 Coarseness Error 98

Chapter 8 Discussion and Conclusion 100

References 102

PART 2 OPERATING MANUAL AND TUTORIAL

Chapter 9 Operating Manual for the Two-Dimensional Electromagnetic Wave Simulator 106

9.1 Introduction 106
9.1.1 General Features of the Simulator 106
9.1.2 Recommended Hardware 107
9.1.3 Getting Started 108
9.1.4 Files Generated by the Programme 2D-TLM 108
9.2 An Overview of the Menu System of 2D-TLM 109
9.2.1 Starting the Programme 109
9.2.2 The System Menu 110
9.2.3 The File Menu 112
9.2.4 The Mesh Menu 114
9.2.5 The Simulate Menu 119
9.2.6 The Input Menu 122
9.2.7 The Plot Menu 123
9.2.8 The Graph Menu 126
9.2.9 The 3D Graphic Menu 127
9.3 Final Remarks and Warning 129

ห้องสมุดกรมวิทยาศาสตร์บริการ

Chapter 10 A Simulation Tutorial 130

10.1 Introduction 130
10.2 Simulations 131
10.2.1 Analysis of a Microstrip Lowpass Filter 131
10.2.2 Generation of the Johns Matrix for a Wideband Absorbing Boundary in Rectangular Waveguide 134
10.2.3 Analysis of a Rectangular Waveguide Bandpass Filter 136
10.2.4 Generation of a Johns Matrix for a Short-Circuited Rectangular Waveguide Stub 137
10.2.5 The Field Response of a Short Circuited Waveguide and its Johns Matrix Twin 137
10.2.6 Use Your Own Source Function 138
10.2.7 A Simple Varactor Diode Frequency Multiplier 140
10.2.8 A Simple Diode Oscillator 141

PART 3 VISUAL ELECTROMAGNETICS LABORATORY EXPERIMENTS: A Series of Examples

Chapter 11 Visual Electromagnetics Laboratory Experiments 144

Preliminary Remarks 144

11.1 **Experiment 1:** Wave Propagation on TEM Transmission Lines 145
11.1.1 Propagation of a Gaussian Impulse along a Lossless Line 146
11.1.2 Propagation of a Sinusoidal Wave along a Lossless Line 146
11.1.3 Reflection of a Gaussian Impulse by a Short-Circuit 147
11.1.4 Reflection of a Gaussian Impulse by an Open Circuit 147
11.1.5 Partial Reflection of a Gaussian Impulse by a Resistive Load 147
11.1.6 Reflection of a Sine Wave by a Short-Circuit 148
11.1.7 Reflection of a Sine Wave by an Open Circuit 148
11.1.8 Partial Reflection of a Sine Wave by a Resistive Load 149
11.1.9 Propagation of a Gaussian Impulse along a Lossy Line 149
11.1.10 Propagation of a Sine Wave along a Lossy Line 149
11.1.11 Scattering of a Gaussian Impulse at a Dielectric Discontinuity 149
11.1.12 Scattering of a Sine Wave at a Dielectric Discontinuity 150
11.1.13 Additional Experimentation 150

11.2 **Experiment 2:** Wave Propagation in Rectangular Waveguides 152

11.2.1 Propagation of a Sinusoidal TE_{10} Wave along a Lossless Guide 153
11.2.2 Reflection of a Sinusoidal TE_{10} Wave by a Short and an Open Circuit 154
11.2.3 Partial Reflection of a Sinusoidal TE_{10} Wave by a Resistive Load 155
11.2.4 Excitation of a Rectangular Waveguide by a Gaussian Impulse 155
11.2.5 Propagation of a Sinusoidal TE_{10} Wave in a Lossy Waveguide 156

11.3 **Experiment 3:** Mode Fields in Rectangular Waveguides 157

11.3.1 Simulation of the Mode Fields 158
11.3.2 Further Experimentation 158

11.4 **Experiment 4:** Scattering at a Discontinuity in a Rectangular Waveguide 159

11.4.1 Scattering Parameters of an Inductive Iris 160
11.4.2 Field Behaviour at the Discontinuity 160
11.4.3 Further Experimentation 160

11.5 **Experiment 5:** Scattering at a Waveguide T-Junction 161

11.5.1 Scattering Parameters of the T-Junction 162
11.5.2 Field Behaviour at the T-Junction 162
11.5.3 Further Experimentation 162

11.6 **Experiment 6:** Study of a Hybrid Branchline Coupler 163

11.6.1 Scattering Parameters of the Branchline Coupler 164
11.6.2 Field Behaviour in the Branchline Coupler 164
11.6.3 Further Experimentation 164

11.7 **Experiment 7:** Diffraction of a Plane Wave by a Small Aperture 165

11.7.1 Diffraction of the Incident Field by the Aperture 165
11.7.2 Further Experimentation 166

11.8 **Experiment 8:** Diffraction of a Plane Wave by a Knife Edge 167

11.8.1 Diffraction of the Incident Field by the Knife Edge 167
11.8.2 Further Experimentation 168

ห้องสมุดกรมวิทยาศาสตร์

11.9 **Experiment 9:** Scattering of a Plane Wave by a Dielectric Cylinder of Square Cross-Section 169

11.9.1 Scattering of a Wave with Polarization Parallel to the Cylinder Axis 170

11.9.2 Scattering of a Wave with Polarization Perpendicular to the Cylinder Axis 170

11.9.3 Further Experimentation 170

11.10 **Experiment 10:** Scattering of a Plane Wave by a Helicopter 171

11.10.1 Scattering of a Wave by the Helicopter 171

11.10.2 Further Experimentation 172

11.11 **Experiment 11:** Parametric Frequency Halving using Varactor Diodes 173

11.11.1 Visualization of the Frequency Halving Process 174

11.11.2 Visualization of the Field Behaviour in the Halver 174

11.11.3 Further Experimentation 174

11.12 **Experiment 12:** Microwave Oscillator with Negative Conductance Diode 175

11.12.1 Visualization of the Start of Oscillations 176

11.12.2 Visualization of the Field in the Oscillator 176

11.12.3 Visualization of the Output Spectrum of the Oscillator 176

11.12.4 Further Experimentation 176

Warning 177

Index 178