

CONTENTS

	Page
Chapter 1. What Machines and Transformers Have in common	
1.1 Purposes of Electrical Machines and Transformers	1
1.2 Mechanical Torque and Power	3
1.3 The Role of the Magnetic Field	5
1.4 Types of Machines	7
1.5 Machine Terminology	8
1.6 Magnetic Poles in Machines	16
1.7 Torque Development in the Three Basic Machines	20
1.8 “Losses” and “Efficiency”	23
1.9 Maximum Efficiency	26
1.10 The Nameplate	28
1.11 Regulation	29
Problems	31
Chapter 2. Synchronous Machines	
2.1 Synchronous Machine Characteristics	35
2.2 Construction of a Synchronous Machine	36
2.3 Cylindrical-Rotor Theory Versus Salient-Pole Theory	49
2.4 The Magnetomotive-Force Field of the Rotor	50
2.5 The Rotating MMF of the Stator Armature Winding	54
2.6 Air Gap Magnetic Field and the Flux per Pole	64
2.7 The Voltage Induced in the Armature Winding of a Synchronous Machine	70
2.8 The Leakage Impedance and Equivalent Circuit	87
2.9 The Circuit Model of the Synchronous Machine	92
2.10 Relative Magnitudes of Synchronous-Machine Impedances: The Per-Unit System	99
2.11 Power and Torque as Related to Power Angle, δ	102
2.12 Damping and Synchronous Motor Starting	107
2.13 How Field Current Changes Are Reflected in the Circuit Model	108
2.14 Operation as a Motor	110
2.15 Operation as a Synchronous Condenser	118
2.16 The Synchronous Machine as a Generator	119
2.17 Measuring x_d	124
2.18 The Short – Circuit Ratio	131
2.19 Calculating Excitation Requirements for Given Operating Conditions	133
2.20 The Capability Curve	144
2.21 Short - Circuit Current Transients in Synchronous Alternators	148
Problems	152
Chapter 3. Transformers	
3.1 Why Transformers Are Essential to Power Systems	159
3.2 Types of Power – System Transformers	160
3.3 Elements of a Transformer	161
3.4 Faraday’s Law and Lenz’ Law	167
3.5 Magnetic Fluxes of a Transformer	169
3.6 Details of Transformer Operation	170
3.7 The Ideal Transformer	179
3.8 A Circuit Model of the Iron-Core Transformer	182
3.9 The Approximate Transformer Circuit Models	194
3.10 Relative Magnitudes of the Circuit – Model Constants : The Per-Unit System	196
3.11 How to Find the Primary Voltage Necessary to produce a Desired Secondary Voltage	202

3.12	Transformer Voltage Regulation	204
3.13	Transforming Three-Phase	209
3.14	Three-Phase Transformation with Two Transformers	216
3.15	Computing Transformer Efficiency	222
3.16	Measuring Transformer Quantities	225
3.17	Measurements on Three-Phase Transformers	229
3.18	Autotransformers	233
3.19	Instrument Transformers	238
	Problems	240
Chapter 4. Induction or “Asynchronous” Machines		
4.1	History and Application of Induction Machines	245
4.2	Construction of Induction Machines	247
4.3	How the Induction Motor Works	250
4.4	The Concept of Slip	252
4.5	The Frequency of Rotor Voltages and Currents	253
4.6	The Induction Motor Under Load	254
4.7	Circuit Model of the Induction Machine	255
4.8	Losses, Power Flow, and Efficiency of Induction Motors	266
4.9	Air-Gap Power : The Magic Quantity	268
4.10	Separation of Mechanical Load from Rotor Copper Loss in the Circuit Model	271
4.11	Performance Calculation Using the Circuit Model	272
4.12	Torque – Speed Characteristics of Induction Machines	276
4.13	Some Useful Exact and Approximate Relationships	282
4.14	Control of Performance Characteristics by Rotor Design	284
4.15	Tests to Determine Circuit – Model Impedances	291
4.16	Starting Induction Motors	301
4.17	Speed Control of Induction Motors	305
	Problems	326
Chapter 5. Direct-Current Machines		
5.1	The Importance of d-c Machines	331
5.2	Construction of d-c Machines	332
5.3	How d-c Machines Work	335
5.4	The Generated Voltage of a d-c Machine	339
5.5	Circuit Model of a d-c Machine	343
5.6	Developed Torque	346
5.7	Field Excitation, Wound-Pole Machines	349
5.8	Finding $K_a\phi$	352
5.9	Speed Control of Shunt and Permanent-Magnet Motors	359
5.10	Per-Unit Values of d-c Machine Resistances and Losses	367
5.11	D-c Motor Starting and Dynamic Braking	372
5.12	Armature Reaction and Commutation	381
5.13	Characteristics of Series and Compound d-c Motors	391
5.14	Permanent Magnet d-c (PMDC) Machines	393
5.15	Self-Excited d-c Generators	402
5.16	Armature Windings for Commutator Machines	413
5.17	Metadynes	418
	Problems	425
Chapter 6. Single – Phase Machines		
6.1	Why Single-Phase Motors Are Different	431
6.2	The Universal Motor	432
6.3	The Shaded-Pole Motor	434
6.4	Single-Phase Induction Motors-Introduction	439
6.5	The Split-Phase Motor	443
6.6	Capacitor Motors	445
6.7	Repulsion Motors	449
6.8	The Circuit Model of Single-Phase Induction Motors	451

6.9 Using the Single-Phase, Induction-Motor Model 457

Index 551