
Contents

Foreword to the First Edition	xii
Preface to the Revised Edition	xlii
Preface to the First Edition	xv
Acknowledgments	xvii

Physical Background Information	1
1.1 Some Basic Electrical Concepts	1
Electric Current	1
Electric Fields	2
Electric Power	4
Electric Energy	4
Resistance	5
Current Flow in Metals	5
Johnson Noise	7
Noise Current	8
Electromigration	9
Insulators and Semiconductors	9
Energy-Band Theory	10
1.2 The Solid State of Matter	13
An Atomistic View	14
Heat Conduction	16
The Material Silicon	17
1.3 Impurity Doping	18
Impurity Types	19
1.4 Diffusion of Materials	20
Gas-Phase Diffusion	21
Solid-State Diffusion and Ion Implantation	21
1.5 Effects of Impurity Doping	22
N-Type Doping and the Electron	23
P-Type Doping and the "Hole"	25
Majority and Minority Charge Carriers	25
2. The Semiconductor Diode: The Basis of the Bipolar Transistor	
2.1 Why Varactors Are More Complex Than a Capacitor	30
Uses for Varactors	32
2.2 Leakage Currents and the Reverse-Biased Diode	33
Temperature Dependence of Leakage Current	35
Nonideal Leakage Currents	35
2.3 Reverse-Voltage Limitations	35
Diodes in Breakdown	36
Avalanche Breakdown	36

	Zener Breakdown	40
	Thickness-Limited Breakdown	42
2.4	Understanding Diodes	42
	Forward-Biasing	42
	Depletion and Diffusion Capacitance	45
	High-Conductance Diodes	45
	Backward Diodes	46
	Quantum-Mechanical Tunneling and the Tunnel Diode	46
	P-i-N and Step-Recovery Diodes	48
	Schottky Diodes	50
	The Ideal-Diode Equation	51
	On Resistance of a Diode	53
2.5	Optoelectronic Diodes	55
	Photodiode Light Detectors	55
	Light-Emitting Diodes	57
3.	An Intuitive Description of Bipolar Transistor Operation	59
3.1	Transistor Basics	59
	Transconductance of a Transistor	60
	Internal Transistor Action	62
	Factors Providing Undesirable Base Currents	64
	Reasons for Output Impedance: Early's Effect and Other Concepts	66
	A Simple Circuit Model for the Transistor	68
	Effects of Biasing Conditions on Output Impedance	70
	The Cascode Connection	73
3.2	Super- β Transistors	73
3.3	Large-Signal Effects	74
	Kirk Effect or Base Stretching	74
	Emitter Efficiency	75
	Saturation	75
	Gold-Doping and Recombination	77
	The Baker Clamp	78
	A Schottky Diode Clamp	78
3.4	Some Unusual Transistors for High Frequency Applications	78
	Heterojunction Bipolar Transistors	78
	Hot Electron Transistors	80
4.	How Transistors Are Made: A Short History of Manufacturing Technologies	81
4.1	Germanium-Alloy Transistors	81
	Base-Width Control	82
4.2	Discrete-Planar, Epitaxial, Passivated-Silicon Transistors	83
	Oxide Benefits with Silicon	83
	Epitaxial Layers	83
	Oxide Masking	84
	Undesired Emitter Pipes	86
	Providing Contacts to the Transistor	87
	A Completed Transistor	87
5.	Bipolar Integrated Circuits: The Whole Thing on One Chip	89
5.1	Some Basic Factors	89
	Linear versus Digital Circuits	89
	Isolating the Transistors	90
	Fabricating NPN Transistors	91
	The Current Mirror and V_{BE} versus I_C Relationships	92
	Emitter-Area Scaling	94

	The Negative Temperature Coefficient of V_{BE} and the Positive Temperature Coefficient of ΔV_{BE}	95
5.2	The Useful Lateral PNP Transistor in Linear ICs	99
	Current Scaling in Multicollector Lateral PNPs	100
	Current Reduction with Reinjector Lateral PNPs	101
5.3	Some Additional PNP Transistors Used in Linear ICs	102
	The Vertical PNP Transistor	103
	A Compatible PNP Process	104
5.4	T²L, the Popular Bipolar-Logic Family	105
5.5	I²L, a Bipolar-Logic Technique	107
5.6	Detrimental Effects of Parasitic Diodes and Transistors in IC Products	109
	Epi Tubs Cause Problems	110

6. Junction Field-Effect Transistors

6.1	The Current I_{DSS}	115
6.2	Pinching Off the Channel	115
6.3	V_{GS} Control and the Pinchoff Voltage	116
6.4	The Bi-FETs	117
	The Trimistor	118
6.5	Metal-Semiconductor FETs (MESFETs) and the GASFETs	121

7. Metal-Oxide Semiconductor Field-Effect Transistors (MOSFETs)

7.1	The P-Channel MOSFET (PMOS)	125
	Inverting the Channel Region	126
	MOS Intuition	127
	Conditions at the Source End	130
	Conditions at the Drain End	131
	Fixed Charge in the Oxide, Fast-Surface States, and Ionic Contamination	132
	Effects of Gate Material on V_{TH}	133
	Increasing V_{TH} through Source-Body Reverse-Biasing	134
	Effects of Increases in V_{DS}	135
	The Saturation Region	135
	An Operating MOSFET	136
	A PMOS Inverter	139
	Depletion Loads	139
	Improvements with Silicon Gates	140
7.2	N-Channel Silicon-Gate MOSFETs	142
	Uses for Polysilicon Layers and Metal Silicides	142
	Fabricating NMOS Transistors	143
7.3	NMOS Improves Microprocessors	145
	NMOS Logic Circuits	146
7.4	Static RAM (SRAM)	149
7.5	The Complementary MOSFET (CMOS)	150
	Parasitic NPN Bipolar Transistors in CMOS	152
	The Semiconductor-Controlled Rectifier (SCR) in CMOS	152
	The Transmission Gate	153
	Using CMOS for Linear Functions	154
	Using CMOS for A/D Converters	161
	Silicon on Sapphire	175
7.6	Double-Diffused Metal-Oxide-Semiconductor (DMOS) Transistors	176
7.7	Vertical Metal-Oxide-Semiconductor (VMOS) Field-Effect Transistors	178
7.8	Charge-Transfer Devices (CTDs)	179
	Bucket-Brigade Devices (BBDs)	179
	Charge-Coupled Devices (CCD)	181
7.9	The Evolution of MOSFET Dynamic Random-Access Memory (DRAM)	182
	Simplifying the DRAM Cell	182
	16-kb Dynamic RAM	184

x Contents

Sensing the Stored Bit	187
α -Particles and Soft Errors	188
High Density Dynamic RAM	190
7.10 Nonvolatile Semiconductor Memory	191
UV Erasable Programmable ROMs (EPROMs)	191
Electrically Erasable PROMs (E ² PROMs)	193
7.11 A Look into the Future	194
Bibliography	197
Index	199