

# CONTENTS

<b>PREFACE</b>	<b>xi</b>
<b>Chapter 1 MEASUREMENT AND ERROR</b>	<b>1</b>
1-1 <i>Definitions</i>	
1-2 <i>Accuracy and Precision</i>	2
1-3 <i>Significant Figures</i>	3
1-4 <i>Types of Error</i>	6
1-5 <i>Statistical Analysis</i>	10
1-6 <i>Probability of Errors</i>	12
1-7 <i>Limiting Errors</i>	16
<i>Questions</i>	18
<i>Problems</i>	18
<b>Chapter 2 SYSTEMS OF UNITS OF MEASUREMENT</b>	<b>20</b>
2-1 <i>Fundamental and Derived Units</i>	20
2-2 <i>Systems of Units</i>	21
2-3 <i>Electric and Magnetic Units</i>	23
2-4 <i>International System of Units</i>	27
2-5 <i>Other Systems of Units</i>	27
2-6 <i>Conversion of Units</i>	30
<i>Problems</i>	30

<b>Chapter 3</b>	<b>STANDARDS OF MEASUREMENT</b>	<b>34</b>
3-1	<i>Classification of Standards</i>	34
3-2	<i>Standards for Mass, Length, and Volume</i>	36
3-3	<i>Time and Frequency Standards</i>	37
3-4	<i>Electrical Standards</i>	39
3-5	<i>Standards of Temperature and Luminous Intensity</i>	46
3-6	<i>IEEE Standards</i>	47
	<i>Questions and Problems</i>	48
<b>Chapter 4</b>	<b>DIRECT-CURRENT INDICATING INSTRUMENTS</b>	<b>50</b>
4-1	<i>Suspension Galvanometer</i>	50
4-2	<i>Torque and Deflection of the Galvanometer</i>	51
4-3	<i>Permanent-Magnet Moving-Coil Mechanism</i>	55
4-4	<i>DC Ammeters</i>	61
4-5	<i>DC Voltmeters</i>	65
4-6	<i>Voltmeter Sensitivity</i>	68
4-7	<i>Voltmeter-Ammeter Method of Measuring Resistance</i>	72
4-8	<i>Series-Type Ohmmeter</i>	74
4-9	<i>Shunt-Type Ohmmeter</i>	78
4-10	<i>Multimeter or VOM</i>	80
4-11	<i>Calibration of DC Instruments</i>	84
4-12	<i>Alternating-Current Indicating Instruments</i>	85
4-13	<i>Thermoinstruments</i>	94
4-14	<i>Electrodynamometers in Power Measurements</i>	97
4-15	<i>Watt-hour Meter</i>	99
4-16	<i>Power-Factor Meter</i>	101
4-17	<i>Instrument Transformers</i>	103
	<i>Problems</i>	108
<b>Chapter 5</b>	<b>BRIDGES AND THEIR APPLICATION</b>	<b>110</b>
5-1	<i>Introduction</i>	110
5-2	<i>Wheatstone Bridge</i>	110
5-3	<i>Kelvin Bridge</i>	117
5-4	<i>Guarded Wheatstone Bridge</i>	122
5-5	<i>AC Bridges and Their Application</i>	125
5-6	<i>Comparison Bridges</i>	129
5-7	<i>Maxwell Bridge</i>	132
5-8	<i>Hay Bridge</i>	134
5-9	<i>Schering Bridge</i>	136
5-10	<i>Unbalance Conditions</i>	138

5-11	<i>Wien Bridge</i>	141
5-12	<i>Wagner Ground Connection</i>	142
5-13	<i>Potentiometer</i>	144
	<i>Problems</i>	145
<b>Chapter 6 ELECTRONIC INSTRUMENTS FOR MEASURING BASIC PARAMETERS</b>		<b>147</b>
6-1	<i>Amplified DC Meter</i>	148
6-2	<i>AC Voltmeter Using Rectifiers</i>	151
6-3	<i>True RMS-Responding Voltmeter</i>	155
6-4	<i>Electronic Multimeter</i>	156
6-5	<i>Considerations in Choosing an Analog Voltmeter</i>	161
6-6	<i>Differential Voltmeters</i>	163
6-7	<i>Digital Voltmeters</i>	169
6-8	<i>Component Measuring Instruments</i>	178
6-9	<i>Q Meter</i>	186
6-10	<i>Vector Impedance Meter</i>	195
6-11	<i>Vector Voltmeter</i>	199
6-12	<i>RF Power and Voltage Measurement</i>	203
	<i>Problems</i>	206
<b>Chapter 7 OSCILLOSCOPES</b>		<b>207</b>
7-1	<i>Introduction</i>	207
7-2	<i>Oscilloscope Block Diagram</i>	208
7-3	<i>Cathode Ray Tube</i>	210
7-4	<i>CRT Circuits</i>	223
7-5	<i>Vertical Deflection System</i>	224
7-6	<i>Delay Line</i>	230
7-7	<i>Multiple Trace</i>	233
7-8	<i>Horizontal Deflection System</i>	235
7-9	<i>Oscilloscope Probes and Transducers</i>	239
7-10	<i>Oscilloscope Techniques</i>	242
7-11	<i>Special Oscilloscopes</i>	248
	<i>Problems</i>	258
<b>Chapter 8 SIGNAL GENERATION</b>		<b>259</b>
8-1	<i>The Sine-Wave Generator</i>	259
8-2	<i>Frequency Synthesized Signal Generator</i>	270
8-3	<i>Frequency Divider Generator</i>	274
8-4	<i>Signal Generator Modulation</i>	277
8-5	<i>Sweep-Frequency Generator</i>	277

8-6	<i>Pulse and Square-Wave Generators</i>	282
8-7	<i>Function Generator</i>	291
8-8	<i>Audiofrequency Signal Generation</i>	293
	<i>Problems</i>	295
<b>Chapter 9</b>	<b>SIGNAL ANALYSIS</b>	<b>296</b>
9-1	<i>Wave Analyzers</i>	296
9-2	<i>Harmonic Distortion Analyzers</i>	300
9-3	<i>Spectrum Analysis</i>	306
	<i>Problems</i>	324
<b>Chapter 10</b>	<b>FREQUENCY COUNTERS AND TIME-INTERVAL MEASUREMENTS</b>	<b>325</b>
10-1	<i>Simple Frequency Counter</i>	325
10-2	<i>Measurement Errors</i>	337
10-3	<i>Extending the Frequency Range of the Counter</i>	341
10-4	<i>Automatic and Computing Counters</i>	345
	<i>Problems</i>	347
<b>Chapter 11</b>	<b>TRANSDUCERS AS INPUT ELEMENTS TO INSTRUMENTATION SYSTEMS</b>	<b>348</b>
11-1	<i>Classification of Transducers</i>	348
11-2	<i>Selecting a Transducer</i>	349
11-3	<i>Strain Gages</i>	353
11-4	<i>Displacement Transducers</i>	359
11-5	<i>Temperature Measurements</i>	369
11-6	<i>Photosensitive Devices</i>	384
	<i>Problems</i>	384
<b>Chapter 12</b>	<b>ANALOG AND DIGITAL DATA ACQUISITION SYSTEMS</b>	<b>392</b>
12-1	<i>Instrumentation Systems</i>	392
12-2	<i>Magnetic Tape Recorders</i>	394
12-3	<i>Self-Balancing Potentiometer</i>	403
12-4	<i>Digital-to-Analog Conversion</i>	407
12-5	<i>Analog-to-Digital Conversion</i>	409
12-6	<i>Multiplexing</i>	421
12-7	<i>Spatial Encoders</i>	424

<b>Chapter 13</b>	<b>COMPUTER-CONTROLLED TEST SYSTEMS</b>	<b>429</b>
13-1	<i>Testing an Audio Amplifier</i>	429
13-2	<i>Testing a Radio Receiver</i>	431
13-3	<i>Instruments Used in Computer-Controlled Instrumentation</i>	435
13-4	<i>IEEE 488 Electrical Interface</i>	443
13-5	<i>Digital Control Description</i>	445
13-6	<i>Example of Signal Timing in a Microprocessor-Based Measurement</i>	446
	<i>Questions</i>	447
<b>APPENDIX</b>		<b>449</b>
	<i>Abbreviations, Symbols, and Prefixes</i>	450
	<i>Decibel Conversion Tables</i>	452
	<i>Table 1: Conversion of Decibels to Power and Voltage (or Current) Ratios</i>	
	<i>Table 2: Conversion of Voltage (or Current) and Power Ratios to Decibels</i>	
<b>SELECTED ANSWERS</b>		
<b>INDEX</b>		