

Contents

<i>Preface to Second Edition</i>	<i>ix</i>
<i>Preface to First Edition</i>	<i>xi</i>
1. Basic Theory	
1.1. <i>Introduction</i>	-
1.2. <i>Energy Bands in Solids</i>	1
1.3. <i>The Fermi Energy Level</i>	4
1.4. <i>Extrinsic Semiconductors</i>	4
1.5. <i>The p-n Junction</i>	6
1.5.1. <i>The Bipolar Junction Transistor</i>	8
1.6. <i>The Metal-Semiconductor Junction</i>	11
1.7. <i>The Metal-Insulator-Semiconductor (MIS) Junction</i>	13
1.7.1. <i>The Metal-Insulator-Semiconductor Transistor</i>	15
1.8. <i>Effective Mass of a Carrier</i>	15
1.9. <i>Carrier Mobilities</i>	17
1.10. <i>Crystalline Structure</i>	19
2. Processing of Silicon Devices and Circuits	
2.1. <i>Introduction</i>	24
2.2. <i>Preparation of Artwork</i>	24
2.3. <i>Photo-sensitive Resists</i>	27
2.4. <i>Masking and Diffusion</i>	29
2.4.1. <i>Gold Diffusion</i>	31
2.5. <i>Metallization</i>	31
2.6. <i>Epitaxial Growth</i>	33
2.7. <i>Alloyed Junctions</i>	34
2.8. <i>Summary</i>	35
3. Silicon Planar Devices and Integrated Circuits	
3.1. <i>Introduction</i>	36
3.2. <i>The Bipolar Planar Transistor</i>	36
3.3. <i>The Planar Diode</i>	39
3.4. <i>The Silicon Integrated Circuit</i>	41

vi *Contents*

4. Bipolar Logic Circuits

4.1. <i>Introduction</i>	53
4.2. <i>Basic Logic Functions</i>	54
4.3. <i>Performance Specifications</i>	56
4.4. <i>Logic Circuits</i>	59
4.5. <i>Comparison of Logic Gates</i>	67
4.6. <i>Schottky TTL</i>	68
4.7. <i>Merged Transistor Logic</i>	68

5. Differential Amplifiers

5.1. <i>Introduction</i>	74
5.2. <i>The Differential Amplifier</i>	74
5.3. <i>The Integrated Operational Amplifier</i>	79

6. Metal–Insulator–Semiconductor Devices

6.1. <i>Introduction</i>	86
6.2. <i>The Basic MOST Mechanism</i>	87
6.3. <i>MOST Symbols. Substrate Bias</i>	94
6.4. <i>Threshold Voltage</i>	96
6.5. <i>The Polysilicon Gate</i>	96
6.6. <i>N-Channel Devices</i>	100
6.7. <i>Complementary Metal–Oxide–Semiconductor (CMOS) Devices</i>	100
6.8. <i>Silicon on Sapphire (SOS)</i>	102
6.9. <i>Other Developments</i>	102
6.10. <i>Equations for the MOST</i>	104
6.11. <i>The MOST as a Resistor</i>	107
6.12. <i>Input Impedance of a MOST</i>	109
6.13. <i>Charge Coupled Devices (CCDs)</i>	109

7. MOS Circuits

7.1. <i>Introduction</i>	114
7.2. <i>The Basic Inverter (or Negate) Circuit</i>	116
7.3. <i>The Basic NOR Gate</i>	120
7.4. <i>The Basic NAND Gate</i>	121
7.5. <i>Comparison of Areas Required for the Basic NAND and NOR Gates</i>	122
7.6. <i>NAND–NOR Gate</i>	123
7.7. <i>Small-signal Analog Amplifier</i>	123
7.8. <i>Large-signal Analog Amplifier</i>	127
7.9. <i>MOSTs as Frequency Doublers</i>	128
7.10. <i>CCD Applications</i>	129
7.11. <i>The CMOS Inverter</i>	132

8. Thin-film Circuits

8.1. <i>Introduction</i>	134
8.2. <i>Thin-film Deposition Methods</i>	134
8.3. <i>Masking and Pattern-making Methods</i>	138
8.4. <i>Thin-film Resistors</i>	142
8.5. <i>Thin-film Capacitors</i>	144
8.6. <i>The Thin-film Transistor</i>	148

9. Thick-film Circuits

9.1. <i>Introduction</i>	149
9.2. <i>The Silk-screen Process</i>	149
9.3. <i>Resistors</i>	152
9.4. <i>Capacitors</i>	152
9.5. <i>Conductor Patterns and Substrates</i>	153

10. Hybrid Circuits

10.1. <i>Introduction</i>	154
10.2. <i>Hybrid Assembly on a Chip</i>	155
10.3. <i>Hybrid Bonding Methods and Circuits</i>	155

11. Microwave Applications of Microelectronics

11.1. <i>Introduction</i>	162
11.2. <i>Passive Components and Microstrip Transmission Lines</i>	162
11.3. <i>Microwave Solid-state Power Sources</i>	168
11.4. <i>High Frequency Transistors</i>	175
11.5. <i>Metal-Semiconductor Junction Devices</i>	177
11.5.1. <i>The Schottky Barrier Diode</i>	177
11.5.2. <i>Gallium Arsenide Field Effect Transistors</i>	178

12. Semiconductor Memories

12.1. <i>Introduction</i>	183
12.2. <i>Some Commonly Used Terms</i>	183
12.3. <i>Read Only Memories (ROMs)</i>	184
12.4. <i>Random Access Memories (RAMs)</i>	188
12.5. <i>Non-volatile Semiconductor Memories (NVSMs)</i>	196
12.6. <i>Shift Registers</i>	202

Appendix. Commonly Used Abbreviations	212
--	-----

Index	214
--------------	-----