

Contents

(Key subjects are shown in bold type)

1	THE END AND THE MEANS	1
	1, Purpose of a laboratory-2, The question of equipment-3, Selecting for minimum cost-4, True economy-5, Making one's own apparatus	
2	PREMISES AND LAYOUT	8
	1, Choice of premises-2, Heating and lighting-3, Interference-4, The amateur's laboratory-5, Storage-6, Layout-7, Mounting of apparatus-8, Benches and wiring-9, Soldering-10, Earthing-11, Connectors	
3	FUNDAMENTAL PRINCIPLES OF MEASUREMENT	23
	1, Measurement <i>v.</i> guesswork-2, False assumptions-3, Direct observation or instrument readings?-4, Subjective methods-5, Disentangling the conclusions-6, Accuracy and precision-7, Basic methods: trial-8, Substitution-9, Difference measurements-10, Null methods-11, The quest for accuracy-12, Personal errors-13, Disturbing effects of instruments-14, Reproducing working conditions	
4	SOURCES OF POWER AND SIGNALS	36
	1, 'Signals'-2, Mains power-3, Voltage stabilizers : reference devices-4, Simple stabilizers-5, Stabilizers with feedback control-6, Switching stabilizers-7, Power supply protection-8, Batteries-9, D.C. voltage raisers-10, Current stabilizers-11, Stabilization of a.c.-12, Power supply literature-13, Signal sources: the gramophone-14, Oscillators : general requirements-15, Reduction of harmonics by <i>LC</i> circuit-16, Valves and transistors compared-17, Feedback <i>LC</i> oscillators-18, Electron-coupled oscillators-19, Negative-resistance or two-terminal oscillators-20, Amplifier two-terminal <i>LC</i> oscillators-21, V.h.f. oscillators-22, <i>RC</i> oscillators-23, Amplitude stabilization-24, Automatic amplitude control-25, The	

CONTENTS

beat-frequency source—26, Commercial a.f. and ultrasonic sources—27, Constructional a.f. sources—28, R.f. sources—29, Standard-signal generators—30, Necessity for thorough screening—31, The attenuator—32, The dummy aerial—33, Frequency control—34, Amplitude modulation—35, Swept frequency generation ('wobulation')—36, Commercial r.f. signal generators—37, Special waveform generators—38, Square-wave and pulse generators—39, Ramp generators—40, 'Noise' generators

5 INDICATORS

105

1, Basic types of meter—2, Characteristics of meter types—3, Accuracy of meters—4, Multi-range meters—5, Overload protection—6, Wattmeters—7, Output power meters—8, R.f. wattmeters—9, Ohmmeters—10, Vibration galvanometers—11, Amplifier-aided meters: introduction—12, D.v. amplifiers: resistance converters—13, Stabilization of d.v. amplifiers—14, Chopper-type amplifiers—15, Meter rectifiers—16, The diode voltmeter—17, Peak-to-peak and r.m.s. meters—18, Simple a.c. valve voltmeters—19, Diode-plus-amplifier voltmeters—20, Amplifier-plus-diode a.v. voltmeters—21, Electronic multimeters and ohmmeters—22, Clip-around meters—23, Selective meters—24, Recording meters—25, Digital meters—26, Cathode-ray tubes: advantages—27, Characteristics of oscilloscope c.r. tubes—28, Multiple-beam tubes—29, Relationship between signal and trace—30, Power supplies—31, Deflection amplifiers—32, Input arrangements—33, Voltage measurement—34, Time bases—35, Synchronization—36, Trace expansion—37, Time measurement—38, The polar time base—39, The frequency base—40, Multiple trace displays—41, Photographing oscillograms—42, Inexpensive electronic indicators—43, Audible indicators

6 STANDARDS

192

1, Purpose and basis of standards—2, Residuals—3, Standards of resistance—4, Non-reactive winding—5, Adjustment of resistors—6, Standards of capacitance—7, Variable standard capacitors—8, Fixed capacitors—9, Standards of inductance—10, Inductometers—11, Fixed inductors—12, Standards of voltage—13, Standards of frequency—14, Quartz crystal oscillators—15, Extending frequency range—16, Passive frequency standards—17, Standards of wavelength—18, Standards of amplification: attenuators—19, The potential divider—20, Loaded attenuators—21, Ladder attenuators—22, Other attenuators

7 COMPOSITE APPARATUS

238

1, What this chapter includes—2, Bridges in general—3, Components of bridges—4, A general-purpose bridge—5, Stray admittances—6, Screening—7, The Wagner earth—8, Symmetrical bridges—9, Common input-output bridges—10, Transformer ratio arms—11, Resistance and capacitance bridges—12, Inductance bridges—13, Classification of four-terminal bridges—14, Commercial bridges—15,

Construction of a mains-frequency bridge-16, Construction of an inductance bridge-17, R.f. bridges-18, Influence of source frequency-19, Frequency bridges and meters-20, **Digital frequency and time meters**-21, Phase meters-22, *Q* meters

8 CHOICE AND CARE OF EQUIPMENT 279

1, General policy in choosing equipment-2, A short list-3, Devising special apparatus-4, Preparation for an experiment-5, Importance of handiness of instruments-6, Layout of apparatus-7, Need for observing restrictions-8, Personal risks-9, Avoiding damage to instruments-10, Maintenance: contacts-11, Calibrations-12, Experimental circuit wiring-13, Prototype circuit testing

9 MEASUREMENT OF CIRCUIT PARAMETERS 298

(A) MEASUREMENT AT ZERO AND AUDIO FREQUENCIES

1, **Resistance**: medium values-2, The Wheatstone bridge-3, Avoiding error in bridge measurements-4, Low resistance-5, Very high resistance-6, Capacitor leakage-7, Guard-ring technique-8, Resistivity of liquids-9, **Capacitance**: measurement by voltmeter-10, Cathode-ray-tube method-11, Bridge methods for capacitance-12, The pF range-13, Testing dielectric materials-14, Larger capacitances-15, Electrolytic capacitors-16, Direct capacitance ('in situ')-17, Direct-reading capacitance meters-18, **Inductance**: difficulties of measurement-19, The three-voltages method-20, Capacitance-comparison method-21, Bridge methods for inductance-22, High inductance by Dye's shunt method-23, Mutual inductance-24, Impedance

(B) MEASUREMENT AT RADIO FREQUENCIES

25, R.f. methods classified-26, **Measurements by *Q* meter**-27, 'Loose-coupled' measurements-28, Capacitance variation-29, Frequency variation-30, Resistance variation-31, **Measurements by oscillator**-32, Measurement of small capacitances-33, Gang-capacitor matching.

(C) MEASUREMENTS ON ACTIVE DEVICES

34, Purposes of tests-35, General precautions-36, D.c. tests-37, Low-frequency tests-38, High-frequency tests-39, Curve tracers-40, Switching tests-41, Special devices

10 SIGNAL MEASUREMENTS 371

1, Disturbing effects of meters-2, Potentiometer measurements-3, Other no-current voltage measurements-4, Small voltages and

CONTENTS

currents-5, Effects of waveform on meter readings-6, Measurement of power-7, Phase difference-8, Waveform examination-9, **Frequency measurement**-10, Frequency comparison by cathode-ray tube-11, Use of auxiliary oscillator-12, Frequency comparison by tuning indicator-13, Aural comparison-14, Calibrating an r.f. signal generator-15, Syntonizing passive tuned circuits-16, Wow and flutter-17, Magnetic flux

11 MEASUREMENT OF EQUIPMENT CHARACTERISTICS

398

1, Response measurements: standard terms-2, **A.f. amplifiers**: measurement of gain-3, Attenuation or loss-4, Sensitivity-5, Frequency characteristics-6, **Output/input characteristics**: overload point-7, Load-resistance characteristics-8, Observation or non-linearity by c.r. tube-9, Basis of non-linearity measurements-10, Calculation of harmonics-11, Measurement of harmonics-12, Measurement of intermodulation-13, Measurement of hum-14, Measurement of noise-15, Input and output impedances-16, Stability tests-17, Square-wave tests-18, **A.f. transformers**-19, Loudspeakers-20, Gramophone pickups-21, **V.f. amplifiers**-22, **R.f. amplifiers**: gain-23, R.f. non-linearity distortion-24, **Detectors**-25, Frequency changers-26, Power units-27, **Receivers**: scope of tests-28, Standard conditions for receiver tests-29, Sensitivity-30, Signal/noise ratio-31, Noise factor-32, **Selectivity**-33, Two-signal tests-34, R.f. modulation hum-35, Continuous selectivity-curve tracing-36, Spurious responses-37, Automatic gain control-38, Overall distortion-39, Tuning drift-40, Vision-channel testing-41, **F.m. receivers**-42, The discriminator-43, Derivative tests-44, Sensitivity-45, Signal/noise ratio-46, Distortion-47, **Transmission lines** (r.f. cables)-48, Return-loss bridges-49, Time-domain reflectometry

12 DEALING WITH RESULTS

475

1, Rearranging formulae-2, What may be neglected-3, Deceptive formulae-4, Aids to calculation-5, **False accuracy**-6, Eliminating errors-7, Tabular working-8, Interpretation of results-9, **Laws**-10, Establishing laws-11, Need for caution-12, Recording results-13, Filing information-14, Communicating results

13 FOR REFERENCE

494

1, Units-2, Symbols, abbreviations and unit equivalents-3, Ohm's law-4, Kirchhoff's laws-5, Resistance-6, Capacitance-7, Properties of insulants and dielectrics-8, Electromagnetism-9, Transformers-10, Inductance-11, Alternating quantities-12, Calculation of impedances-13, **Duals**-14, λ - Δ or T- Π transformation-15, Frequency cut-off curves-16, Resonance-17, Q -18, Tuning curves-19, Miller effect-20, Negative feedback-21, Operational amplifiers-22, Valve equivalent generator-23, Transistor equivalent generator-24, Thevenin's theorem-25, Attenuators-26, Smoothing and

CONTENTS

decoupling filters—27, Matched-termination filters—28, Transmission lines—29, Aerials—30, Cathode-ray deflection—31, Light—32, Sound—33, Noise—34, Mathematical formulae—35, Decibels (and nepers)—36, Musical intervals and frequencies—37, Frequency allocations—38, Standard frequency signals—39, Test disk and tape records—40, Colour codes—41, Wire tables

INDEX

594