

CONTENTS

		Page
Chapter 1	Introduction	
1.1	Basic concepts	1
1.2	The structure of matter	1
1.3	Electric current	3
1.4	The SI system of units	4
1.5	Multiples of units	5
1.6	The basic units	5
1.7	Derived units	6
1.8	Weight	7
1.9	Rotary motion	8
1.10	Examples	9
1.11	Summary	11
	Problems 1	12
Chapter2	The electric circuit	
2.1	Voltage, current, and resistance	13
2.2	Resistors in series	14
2.3	The potential divider	16
2.4	Resistors in parallel	16
2.5	Current division in parallel paths	19
2.6	Sources	20
2.7	Resistivity and calculation of resistance	23
2.8	Change of resistance with temperature	24
2.9	Power and energy	26
2.10	Circuit reduction	29
2.11	Kirchhoff's laws	32
2.12	The superposition theorem	37
2.13	Thevenin's theorem	39
2.14	Maximum power transfer	40
2.15	Summary	42
	Problems 2	45
Chapter3	Electromagnetism	
3.1	Magnetic fields, flux, and flux density	52
3.2	Force on a conductor in a magnetic field	57
3.3	Magnetic field strength H and its relation to B	59
3.4	The calculation of H	59
3.5	Force between two long parallel conductors carrying current	61
3.6	The magnetization of iron	63
3.7	The magnetic circuit	66
3.8	Induced e.m.f.	71
3.9	Flux cutting	73
3.10	Fleming's right hand rule	74
3.11	Self inductance	75
3.12	Calculation of self inductance	77
3.13	Energy stored in an inductance	78
3.14	Mutual inductance	79
3.15	The transformer principle	81
3.16	A note on dimensions	81
3.17	Hysteresis	81
3.18	Eddy current loss	84
3.19	Summary	84

	Problems 3	87
Chapter4	Electric field; capacitors and capacitance	
4.1	Electric charges	95
4.2	Coulomb's law	95
4.3	Electric fields; field intensity or electric force	95
4.4	Capacitance; capacitors	98
4.5	Relationship between electric force and potential gradient	101
4.6	Electric flux density D	102
4.7	Relationship between D and E; permittivity	103
4.8	Capacitance between parallel plates	104
4.9	A definition of relative permittivity	106
4.10	Capacitors in parallel	106
4.11	Calculation of capacitance of multi-plate capacitors	107
4.12	Capacitors in series	107
4.13	Energy stored in a capacitor	108
4.14	Construction of capacitors	109
4.15	Summary	111
	Problems 4	112
Chapter5	Transient effects in d.c. circuits	
5.1	Transient and steady-state conditions	116
5.2	Charge of a capacitor	116
5.3	Discharge of a capacitor	119
5.4	Growth and decay of current in an inductive circuit	121
5.5	Plotting charge and discharge curves	123
5.6	A note on dimensions	124
5.7	Summary	125
	Problems 5	125
Chapter 6	Alternating currents	
6.1	Alternating currents and voltages	128
6.2	Production of an alternating e.m.f.	130
6.3	Average value of an alternating quantity	133
6.4	Root mean square (r.m.s.) value of a current	135
6.5	Form factor and peak factor	137
6.6	The sine wave	138
6.7	Average and r.m.s. values of a sine wave	140
6.8	Representation of an alternating quantity	142
6.9	Summary	147
	Problems 6	148
Chapter7	Single-phase alternating current theory	
7.1	Circuit containing resistance only	153
7.2	Circuit containing inductance only	154
7.3	Circuit containing capacitance only	156
7.4	Inductance and resistance in series	158
7.5	Capacitance and resistance in series	161
7.6	Impedance has two parts	164
7.7	More about phasor diagrams	164
7.8	Impedances in series	166
7.9	Power and power factor	170
7.10	Power, apparent power, and reactive power	173
7.11	Series resonance	174
7.12	Phasor diagrams for parallel circuits	178
7.13	Admittance, conductance, and susceptance	179
7.14	Equivalence of series and parallel representation	181
7.15	Admittances in parallel	183
7.16	Parallel resonance	184
7.17	Electricity supply	186

7.18	Summary	190
	Problems 7	193
Chapter 8	Three-phase alternating current theory	
8.1	Polyphase generation	202
8.2	Three-phase, four-wire systems	204
8.3	Three-wire systems	208
8.4	Reasons for the adoption of three-phase systems	213
8.5	Summary	214
	Problems 8	215
Chapter 9	The single-phase transformer	
9.1	Transformer construction	218
9.2	Principle of operation	220
9.3	Transformer e.m.f. equation	222
9.4	Phasor diagrams	223
9.5	Impedance matching	226
9.6	Transformer losses and efficiency	227
9.7	Leakage reactance	228
9.8	Transformer testing	229
9.9	Auto-transformers	232
9.10	Summary	233
	Problems 9	233
Chapter 10	Electrical machines	
10.1	Machines	237
10.2	Single-excited machines	237
10.3	Double-excited machines	240
10.4	Windings	242
10.5	Multi-polar machines	247
10.6	Some types of machine	249
10.7	Energy balance and efficiency	251
10.8	Steady-state theory of the d.c. machine	253
10.9	D.C. motors	256
10.10	D.C. generators	261
10.11	Swinburne test for d.c. machines	263
10.12	The three-phase induction motor	265
10.13	Summary	267
	Problems 10	269
Chapter 11	Electronics	
11.1	More about the structure of matter	272
11.2	Pure semiconductors	274
11.3	Impurity semiconductors	276
11.4	The p-n junction	278
11.5	The bipolar transistor	284
11.6	The common-base amplifier	286
11.7	The common-emitter amplifier	288
11.8	Static characteristics of a transistor	289
11.9	The d.c. load line	290
11.10	The transistor as a switch	292
11.11	Transistor construction	293
11.12	Unipolar transistors	295
11.13	Thermionic emission	297
11.14	The vacuum diode	298
11.15	The vacuum triode	300
11.16	Static characteristics of a triode valve	301
11.17	The triode valve as an amplifier	302
11.18	The cathode ray tube	303
11.19	Rectifier connections	306

11.20	Summary	306
	Problems 11	309
Chapter 12	Measurement	
12.1	The moving-coil instrument	314
12.2	Measuring current with a moving-coil instrument	317
12.3	Measuring voltage with a moving-coil instrument	318
12.4	Measuring resistance with a voltmeter and ammeter	319
12.5	Measuring resistance using the Wheatstone bridge	321
12.6	Measurement of resistance with an ohmmeter	322
12.7	The potentiometer	324
12.8	Using the potentiometer to measure higher voltages	327
12.9	Using the potentiometer to measure current	328
12.10	Using the potentiometer	328
12.11	Measurement of alternating current	329
12.12	The moving-iron instrument	329
12.13	The rectifier moving-coil instrument	333
12.14	Thermal instruments	333
12.15	Extension of range of a.c. instruments	334
12.16	The dynamometer instrument and its use as a wattmeter	335
12.17	Measurement of power on three-phase circuits	338
12.18	Measuring power factor of a three-phase balanced load	340
12.19	Measurements using the cathode-ray oscilloscope	342
12.20	Electronic voltmeters	344
12.21	The fluxmeter	345
12.22	Summary	346
	Problems	347
Index		377